

### 3. Behavioral Design Assignments

Due Jun 2 at 11:59pm Points 100 Questions 3 Time Limit None

#### Instructions

The main objective of the assignment is to practice and implement different methods for describing combinational logic in Verilog:

1. In this set of assignments, we will practice how to use the assign operator to define the logical expression for an output. In the structural design with basic primitive logic gates assignment, we instantiated AND, OR, NOT, and XOR gates and used interconnecting wires to implement the switching logic. Using the assign operator allows us to describe the hardware in a more compact code. This is implemented in question 1 converting a BCD to Xcess3 code. This example also introduces you to the Xcess code and covers an overview of the advantages of this code.
2. The assignment also covers the implementation of case structures to implement a hardware design while bypassing the K-map step for finding the SOP (Sum of Products) expressions. Question 2 introduces the students to the 2421 code and uses the case structure to implement the conversion.
3. Displaying 4-bit binary input on two seven-segment-displays covering numbers from 0 to 15. This design requires the implementation of comparators, multiplexers (using the conditional assignment) to have the correct numbers displayed.

For each design, you will create a testbench to verify the correct functionality of the design.

This is a group assignment (groups of 2 students). Each group will submit one document listing the contribution of each member.

**Objective:** Behavioral Models in Verilog - Designing combinational circuits that can perform binary-to-decimal number conversion.

#### Part (1): Seven Segment Display (Book example page 170 & 171)

We wish to display on 7-segment display the values set by 4 input switches. Your circuit should be able to display the digits from 0 to 9 and should treat the values 1010 to 1111 as BLANK display (all OFF). The LEDs for the 7-segment display are all active low (common anode), which means that the LED would turn ON when its assigned bit value is a logic '0'.

Create a design that assigns the correct output bits to the 7-segments based on the 4-bit input value. Use parameters for the 10 different decimal digits (0 to 9) and the BLANK case.

```
//
parameter      BLANK      = 7'b111_1111;
parameter      ZERO       = 7'b000_0001;
```

 


FIGURE 5-14 A seven-segment LED display.

#### Division of Responsibility

Assignment	Map/ Equations/ Code	TestBench
1	Kalin	Jammeh
2	Kalin	Jammeh
3 Part 1	Kalin	Jammeh
3 Part 2	Kalin	Jammeh

#### Module code

// Name: Ron Kalin, Date: 5-31-24, Design: Lesson 3A3P1: 7-segment display

// Group: Ron Kalin/Lamin Jammeh

// 7-segment display

Date: June 01, 2024


Seven\_Seg\_Display.v

Project: Seven\_Seg\_Display

```
1 // Name: Ron Kalin, Date: 5-31-24, Design: Lesson 3A3P1: 7-segment display
2 // Group: Ron Kalin/Lamin Jammeh
3 // 7-segment display
4 module Seven_Seg_Display ( output reg [6:0] Display, //output is the display abc_defg
5                             input [3:0] BCD); //input BCD
6 //
7 parameter      BLANK      = 7'b111_1111; //blank
8 parameter      ZERO       = 7'b000_0001; //h01 hexadecimal 1st 3-digits = 0 = 000
9 parameter      ONE        = 7'b100_1111; //h4F hexadecimal 2nd 4-digits = F = 1111
10 parameter     TWO        = 7'b001_0010; //h12
11 parameter     THREE      = 7'b000_0110; //h06
12 parameter     FOUR       = 7'b100_1100; //h4c
13 parameter     FIVE       = 7'b010_0100; //h24
14 parameter     SIX        = 7'b010_0000; //h20
15 parameter     SEVEN      = 7'b000_1111; //h0f
16 parameter     EIGHT      = 7'b000_0000; //h00
17 parameter     NINE       = 7'b000_0100; //h04
18 always @ (BCD)
19     case (BCD) //BCD is
20         0: Display = ZERO;
21         1: Display = ONE;
22         2: Display = TWO;
23         3: Display = THREE;
24         4: Display = FOUR;
25         5: Display = FIVE;
26         6: Display = SIX;
27         7: Display = SEVEN;
28         8: Display = EIGHT;
29         9: Display = NINE;
30         default: Display = BLANK;
31     endcase
32 endmodule
33
```



FIGURE 5-14 A seven-segment LED display.

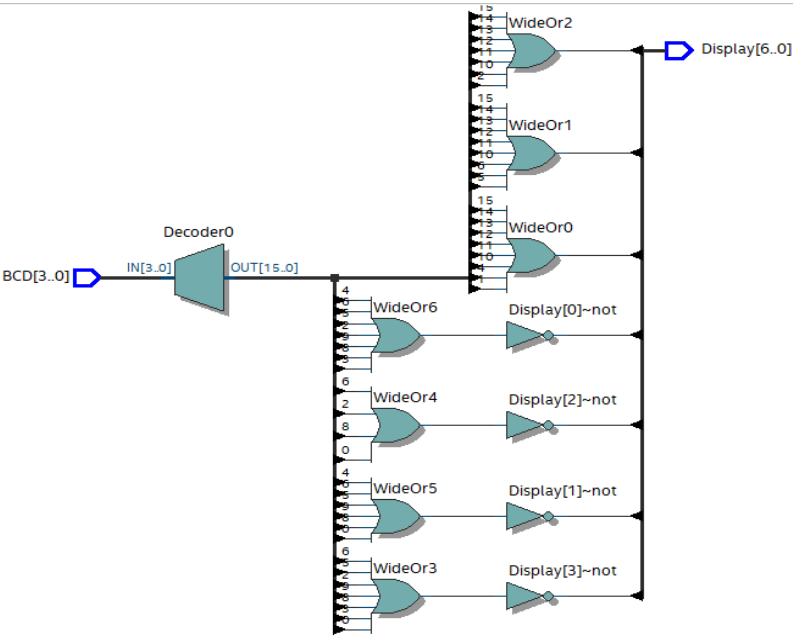

// 5/31/24 testbench 7-segment display

te: June 02, 2024

Seven\_Seg\_Display\_tb.v

Project: Seven\_Seg\_Display

```
1  /*-----*/
2  Name Lamin Jammeh
3  Class: EE417 Summer 2024
4  Lesson 03 HW Question 3 Part1
5  Group: Ron Kalin/ Lamin Jammeh
6  Main design was done by Ron Kalin
7  TestBench was done by Lamin Jammeh
8  -----*/
9
10 //Step1 define a name for the test-bench
11 module Seven_Seg_Display_tb ;
12
13 //Step2 define the inputs as registers and outputs as wires
14 reg [3:0] BCD;
15 wire [6:0] Display;
16
17 //Step3 define the Unit under test UUT with all inputs and outputs
18 Seven_Seg_Display UUT (
19     .Display(Display),
20     .BCD(BCD)
21 );
22
23 //Step4 open an initial block and define all the possible input combination for the BCD
24 //from 0-15 using 4bits
25 initial
26 begin
27     BCD = 4'b_0000; //0
28     #100 BCD = 4'b_0001; //1
29     #100 BCD = 4'b_0010; //2
30     #100 BCD = 4'b_0011; //3
31     #100 BCD = 4'b_0100; //4
32     #100 BCD = 4'b_0101; //5
33     #100 BCD = 4'b_0110; //6
34     #100 BCD = 4'b_0111; //7
35     #100 BCD = 4'b_1000; //8
36     #100 BCD = 4'b_1001; //9
37     //Needs a second circuit to show the tenth digits
38     #100 BCD = 4'b_1010; //10
39     #100 BCD = 4'b_1011; //11
40     #100 BCD = 4'b_1100; //12
41     #100 BCD = 4'b_1101; //13
42     #100 BCD = 4'b_1110; //14
43     #100 BCD = 4'b_1111; //15
44     #100;
45 end
46 //Display the results
47 initial begin
48     $monitor("BCD = %b:   Decimal_Input = %d:   Display = %b:   Hex_Output =%h:", BCD,
49     BCD, Display, Display);
50 end
51 endmodule
```

# Simulation Results



```
# run -all
# BCD = 0000: Decimal_Input = 0: Display = 0000001: Hex_Output =01:
# BCD = 0001: Decimal_Input = 1: Display = 1001111: Hex_Output =4f:
# BCD = 0010: Decimal_Input = 2: Display = 0010010: Hex_Output =12:
# BCD = 0011: Decimal_Input = 3: Display = 0000110: Hex_Output =06:
# BCD = 0100: Decimal_Input = 4: Display = 1001100: Hex_Output =4c:
# BCD = 0101: Decimal_Input = 5: Display = 0100100: Hex_Output =24:
# BCD = 0110: Decimal_Input = 6: Display = 0100000: Hex_Output =20:
# BCD = 0111: Decimal_Input = 7: Display = 0001111: Hex_Output =0f:
# BCD = 1000: Decimal_Input = 8: Display = 0000000: Hex_Output =00:
# BCD = 1001: Decimal_Input = 9: Display = 0000100: Hex_Output =04:
# BCD = 1010: Decimal_Input = 10: Display = 1111111: Hex_Output =7f:
# BCD = 1011: Decimal_Input = 11: Display = 1111111: Hex_Output =7f:
# BCD = 1100: Decimal_Input = 12: Display = 1111111: Hex_Output =7f:
# BCD = 1101: Decimal_Input = 13: Display = 1111111: Hex_Output =7f:
# BCD = 1110: Decimal_Input = 14: Display = 1111111: Hex_Output =7f:
# BCD = 1111: Decimal_Input = 15: Display = 1111111: Hex_Output =7f:
```

Part 2: 7-segment display, 4-bit input word and output 2-decimal equivalent

Part (2): Binary-Coded Decimal

You are to design a circuit that converts a four-bit binary number  $V = v_3 v_2 v_1 v_0$  into its two-digit decimal equivalent  $D = d_1 d_0$ . Table 1 shows the required output values.

**Structural Design:**

It includes a comparator that checks when the value of  $V$  is greater than 9 and uses the output of this comparator in the control of the 7-segment displays. You can use the conditional and comparison operators

 


Table 1: Binary-to-decimal conversion values.

Figure 1: Partial design of the binary-to-decimal conversion circuit.

Notice that the circuit in Figure 1 includes a 4-bit wide 2-to-1 multiplexer. The purpose of this multiplexer is to drive digit  $d_0$  with the value of  $V$  when  $z = 0$ , and the value of  $A$  when  $z = 1$ . To design circuit A consider the following. For the input values  $V < 9$ , the circuit A does not matter, because the multiplexer in Figure 1 just selects  $V$  in these cases. But for the input values  $V > 9$ , the multiplexer will select  $A$ . Thus,  $A$  has to provide output values that properly implement Table 1 when  $V > 9$ . You need to design circuit A so that the input  $V = 1010$  gives an output  $A = 0000$ , the input  $V = 1011$  gives the output  $A = 0001$ , and the input  $V = 1111$  gives the output  $A = 0101$ . Design circuit A using a case structure.

Circuit A			
DecV	V	A	DecA
10	1010	0000	0
11	1011	0001	1
12	1100	0010	2
13	1101	0011	3
14	1110	0100	4
15	1111	0101	5

The top code module should instantiate the needed submodules with correct interconnections.

```

1 // Name: Ron Kalin, Date: 5-31-24, Design: Lesson3A3P2: 7-seg display 2 digits
2 // Group: Ron Kalin/Lamin Jammeh
3 module SevenSegDisplay2Digits (output [6:0] d1,d0, input [3:0] V);
4     wire [3:0] A;
5     wire [3:0] muxout;
6     wire [3:0] z;
7     wire gr;
8 //instantiate submodules, cannot use if statements to instantiate
9 comp4bit COMP9 (z, V, gr); //if V>9, gr=1, else gr=0
10 CircuitA CIRA (V, A); //input V output A, A=V if V<=9, else A=V-10
11 mux2to1_4bit MUX (V, A, gr, muxout); //z=0, select V, else select A
12 //assign z1 = (z==1) ? z : 4'b1111; //if gr=1 then z1=1, else z1=blank
13 Seven_Seg_Dis SEV1 (d1,z); //d1 output, z1 input (either 1 or 0), blank =4'b1111
14 Seven_Seg_Dis SEV0 (d0, muxout); //display data from MUX
15
16 endmodule
17
18 //4-bit comparator
19 module comp4bit(B, V, z);
20     input [3:0] V; // 4-bit inputs
21     output reg [3:0] B; // 4-bit output
22     output z;
23     //wire eq, ls;
24     //assign eq = (a == 9) ? 1 : 0; // Equal condition
25     assign z = (V > 9) ? 1 : 0; // Greater than condition
26     //assign ls = (a < 9) ? 1 : 0; // Less than condition
27     always @ (V)
28         if (V>9) begin
29             //V>9 so display 1
30             B=4'b0001;
31             //b=V;
32             end
33         else begin //V<9 so blank
34             B=4'b1111;
35             end
36 endmodule
37
38 //4-bit wide 2 to 1 multiplexer
39 module mux2to1_4bit(
40     input [3:0] data0, // 4-bit input data 0
41     input [3:0] data1, // 4-bit input data 1
42     input select, // Select signal (0 or 1), z
43     output reg [3:0] muxout); //4-bit output
44     always @ (data0, data1) //put input only in sensitivity list
45         if (select) //select = 1
46             muxout = data1; //data1 from circuit A
47         else
48             muxout = data0; //data from V
49 endmodule
50
51 //Circuit A
52 module CircuitA (
53     input [3:0] V, // Input V 4-bit word
54     output reg [3:0] A ); // output 4-bit word
55
56     always @ (V)
57         case (V)
58             4'b1010: A = 4'b0000; // 10 returns 0
59             4'b1011: A = 4'b0001; // 11 returns 1
60             4'b1100: A = 4'b0010; // 12 returns 2
61             4'b1101: A = 4'b0011; // 13 returns 3
62             4'b1110: A = 4'b0100; // 14 returns 4
63             4'b1111: A = 4'b0101; // 15 returns 5
64             default: A = 4'b1111; // Default unique value, detect invalid input
65         endcase
66 endmodule

```

---

```

67 // 7-segment display
68 module Seven_Seg_Dis ( output reg [6:0] Disp, input [3:0] BCD); //input BCD
69 // output Disp abc_defg (seven segments, not including dec. pt)
70

```

June 02, 2024


SevenSegDisplay2Digits.v

Project: SevenSegDisplay2Digits

```

71 parameter BLANK = 7'b111_1111; //blank
72 parameter ZERO = 7'b000_0001; //h01 hexadecimal 1st 3-digits = 0 = 000
73 parameter ONE = 7'b100_1111; //h4F hexadecimal 2nd 4-digits = F = 1111
74 parameter TWO = 7'b001_0010; //h12
75 parameter THREE = 7'b000_0110; //h06
76 parameter FOUR = 7'b100_1100; //h4c
77 parameter FIVE = 7'b010_0100; //h24
78 parameter SIX = 7'b010_0000; //h20
79 parameter SEVEN = 7'b000_1111; //h0f
80 parameter EIGHT = 7'b000_0000; //h00
81 parameter NINE = 7'b000_0100; //h04
82 always @ (BCD)
83 case (BCD) //BCD is decimal value
84 0: Disp = ZERO;
85 1: Disp = ONE;
86 2: Disp = TWO;
87 3: Disp = THREE;
88 4: Disp = FOUR;
89 5: Disp = FIVE;
90 6: Disp = SIX;
91 7: Disp = SEVEN;
92 8: Disp = EIGHT;
93 9: Disp = NINE;
94 default: Disp = BLANK;
95 endcase
96 endmodule
97

```

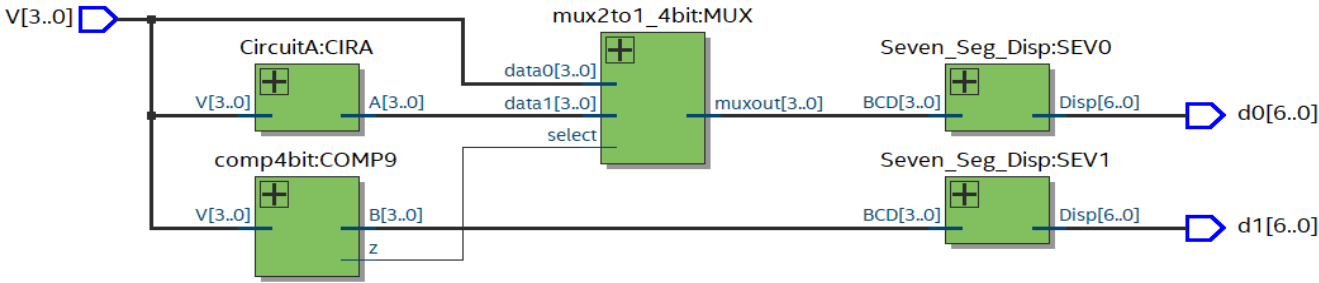



## Testbench

```
/*-----*/
Name Lamin Jammeh
Class: EE417 Summer 2024
Lesson 03 HW Question 3 Part1
Group: Ron Kalin/ Lamin Jammeh
Main design was done by Ron Kalin
TestBench was done by Lamin Jammeh
/*-----*/

//Step1 define a name for the test-bench
module SevenSegDisplay2Digits_tb;

//Step2 define the inputs as registers and outputs as wires
reg [3:0] v;
wire [6:0] d1, d0;


//Step3 define the unit under test UUT with all inputs and outputs
SevenSegDisplay2Digits uut (
    .d1(d1),
    .d0(d0),
    .v(v)
);

//Step4 open an initial block and define all the possible input combination for the BCD from 0-15 using 4bits
initial
begin
    v = 4'b0000; //0
    #100 v = 4'b0001; //1
    #100 v = 4'b0010; //2
    #100 v = 4'b0011; //3
    #100 v = 4'b0100; //4
    #100 v = 4'b0101; //5
    #100 v = 4'b0110; //6
    #100 v = 4'b0111; //7
    #100 v = 4'b1000; //8
    #100 v = 4'b1001; //9

    #100 v = 4'b1010; //10
    #100 v = 4'b1011; //11
    #100 v = 4'b1100; //12
    #100 v = 4'b1101; //13
    #100 v = 4'b1110; //14
    #100 v = 4'b1111; //15
    #100;
end

//Display the results
initial begin
    $display("-----output_display = --d1---_--d0---");
    $monitor("V = %b: Decimal_Input = %d: output_Display = %b_%b ", v, v, d1, d0);
end
endmodule
```

## Simulation

 

```
#
# add wave *
# view structure
# .main_pane.structure.interior.cs.body.struct
# view signals
# .main_pane.objects.interior.cs.body.tree
# run -all
#
# output_didplay = --d1---d0---
# V = 0000: Decimal_Input = 0: Output_Display = 1111111_00000001
# V = 0001: Decimal_Input = 1: Output_Display = 1111111_10011111
# V = 0010: Decimal_Input = 2: Output_Display = 1111111_00100101
# V = 0011: Decimal_Input = 3: Output_Display = 1111111_00001110
# V = 0100: Decimal_Input = 4: Output_Display = 1111111_10011100
# V = 0101: Decimal_Input = 5: Output_Display = 1111111_01001100
# V = 0110: Decimal_Input = 6: Output_Display = 1111111_01000000
# V = 0111: Decimal_Input = 7: Output_Display = 1111111_00011111
# V = 1000: Decimal_Input = 8: Output_Display = 1111111_00000000
# V = 1001: Decimal_Input = 9: Output_Display = 1111111_00001100
# V = 1010: Decimal_Input = 10: Output_Display = 1001111_00000001
# V = 1011: Decimal_Input = 11: Output_Display = 1001111_10011111
# V = 1100: Decimal_Input = 12: Output_Display = 1001111_00100101
# V = 1101: Decimal_Input = 13: Output_Display = 1001111_00001110
# V = 1110: Decimal_Input = 14: Output_Display = 1001111_10011100
# V = 1111: Decimal_Input = 15: Output_Display = 1001111_01001100
```

VSIM 2>