

Example Design: Random Counter using a Moore FSM:

```

/*-----
Random Counter:
-----
The counter if reset should display a count of 3'b001. If the reset is inactive
and the counter is enabled and the mode is 0, the counting sequence should be:
1 7 3 5 1 7 3 5 ... and so on.
If the counter is enabled and the mode is 1, the counting sequence should be:
1 5 3 7 1 5 3 7 ... and so on.
If the counter is not reset but the enable is not high, then the counter should
hold the last value it has reached.
This counter is synchronized by a clock. The reset and the enable are also
synchronized, meaning that their effect will only be applied at a positive clock edge.
The counter should be designed using a Moore FSM.
*/

```

```

module RandomCounter (count, clk, reset, enable, mode);

```

```

    output reg [2:0] count;
    input            clk, reset, enable, mode;

```

```

    reg [1:0] state, next_state;

```

```

    parameter ONE    = 2'b00;
    parameter SEVEN  = 2'b01;
    parameter THREE  = 2'b10;
    parameter FIVE   = 2'b11;

```

```

// Sequential logic:

```

```

always @ (posedge clk)
if (reset) state <= ONE;
else state <= next_state;

```

```

// Combinational logic to find the next_state based on the inputs and the current state:

```

```

always @ *
case (state)

```

```

    ONE :   if (enable & ~mode) next_state = SEVEN; // 1 7 3 5 1 7 3 5
           else if (enable & mode)  next_state = FIVE;  // 1 5 3 7 1 5 3 7
           else                    next_state = ONE;    // hold

```

```

    SEVEN : if (enable & ~mode) next_state = THREE; // 1 7 3 5 1 7 3 5
           else if (enable & mode)  next_state = ONE; // 1 5 3 7 1 5 3 7
           else                    next_state = SEVEN; // hold

```

```

    THREE : if (enable & ~mode) next_state = FIVE; // 1 7 3 5 1 7 3 5
           else if (enable & mode)  next_state = SEVEN; // 1 5 3 7 1 5 3 7
           else                    next_state = THREE; // hold

```

```

    FIVE :   if (enable & ~mode) next_state = ONE; // 1 7 3 5 1 7 3 5
           else if (enable & mode)  next_state = THREE; // 1 5 3 7 1 5 3 7
           else                    next_state = FIVE; // hold

```

```

    default: next_state = ONE; // assumed to be the starting and reset case.

```

```

endcase

```

```

// Combinational logic to determine the output based on the current state:

```

```

always @ (state)
case (state)

```

```

    ONE   : count = 3'b001;
    SEVEN : count = 3'b111;
    THREE : count = 3'b011;
    FIVE  : count = 3'b101;
    default: count = 3'b000; // invalid output

```

```

endcase


```

```

endmodule


```

• Moore FSM:

 


We can observe and verify the design used for the FSM by using the State Machine Viewer in Quartus:

 Tools -> Netlist viewer -> State Machine Viewer



 You can also access it by going to the **RTL viewer** and double clicking on the sequential logic finding the value of the next state and updating the state value.



```

module RandomCounter_TB ();

wire [2:0] count;
reg      reset, enable, mode;
reg      clk;

// internal probes to observe how the state is changing:
wire [1:0] state, next_state;

RandomCounter UUT (count, clk, reset, enable, mode);

// assigning the internal probes to test the internal registers of the UUT
assign state      = UUT.state;
assign next_state = UUT.next_state;

initial
begin
    clk = 1'b0;
    forever
    #5    clk = ~clk;
end


initial
begin
    reset = 1'b1;
    # 50 reset = 1'b0;
    #200 reset = 1'b1;
    #40  reset = 1'b0;
end

initial
begin
    mode = 1'b0;
    forever
    # 100 mode = ~mode;
end

initial
begin
    enable = 1'b0;
    forever
    begin
        # 30 enable = 1'b1;
        # 80 enable = 1'b0;
    end
end

endmodule

```

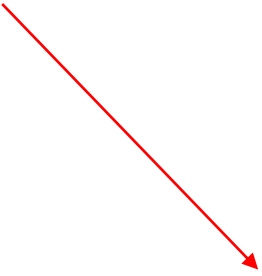

Observing internal signals within the UUT is sometimes very helpful in trouble shooting problems in the code and tracking any functional mistakes. You don't have to take the signal as an output, but rather assign an internal testing probe.

The simulation results:

