

Example Design: Sequence Detector – Mealy FSM – Video 2

```

/*-----
The module receives a single bit input x_in. Whenever x_in performs a sequence 101
the z_out flag is raised high indicating that 101 was detected. The sequences can be
overlapping. The design is performed using a Mealy FSM.
The explanation of the FSM state diagram is given in video 2.
*/-----

module Sequence_101_Detector_Mealy (z_out, clk, reset, x_in);

output reg z_out;
input      clk, reset;
input      x_in;


reg [1:0] state, next_state;

parameter Snone = 2'b00; // None of the correct sequence bits received
parameter S1    = 2'b01; // A one was received
parameter S10   = 2'b10; // A 10 sequence was received


// sequential logic (flip flop) updating the state register
always @ (posedge clk)
    if (reset) state <= Snone;
    else      state <= next_state;

// combinational logic determining the next_state and the output
always @ *
    case (state)
        Snone : begin z_out = 1'b0;
                     if (x_in) next_state = S1;
                     else      next_state = Snone;
                   end
        S1     : begin z_out = 1'b0;
                     if (x_in) next_state = S1;
                     else      next_state = S10;
                   end
        S10    : begin
                     if (x_in) begin z_out = 1'b1; next_state = S1; end
                     else      begin z_out = 1'b0; next_state = Snone; end
                   end
        default : begin z_out = 1'b0; next_state = Snone; end
    endcase
endmodule


```

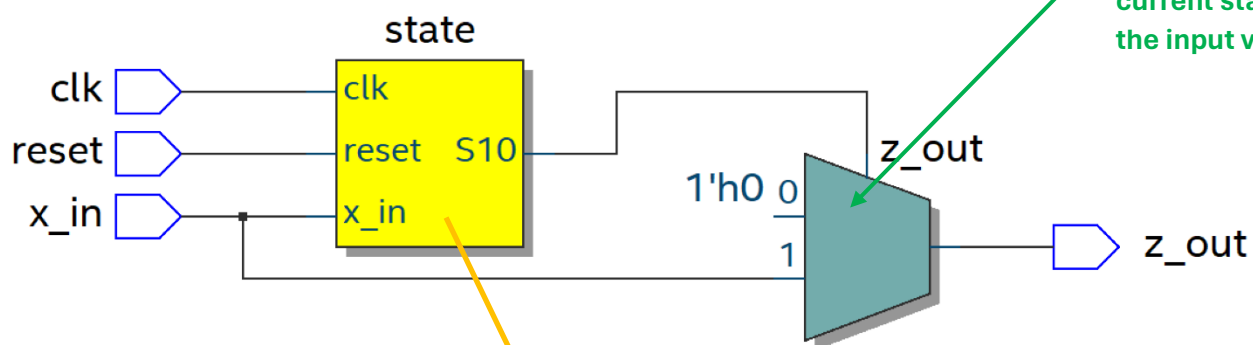

• Mealy FSM:

 

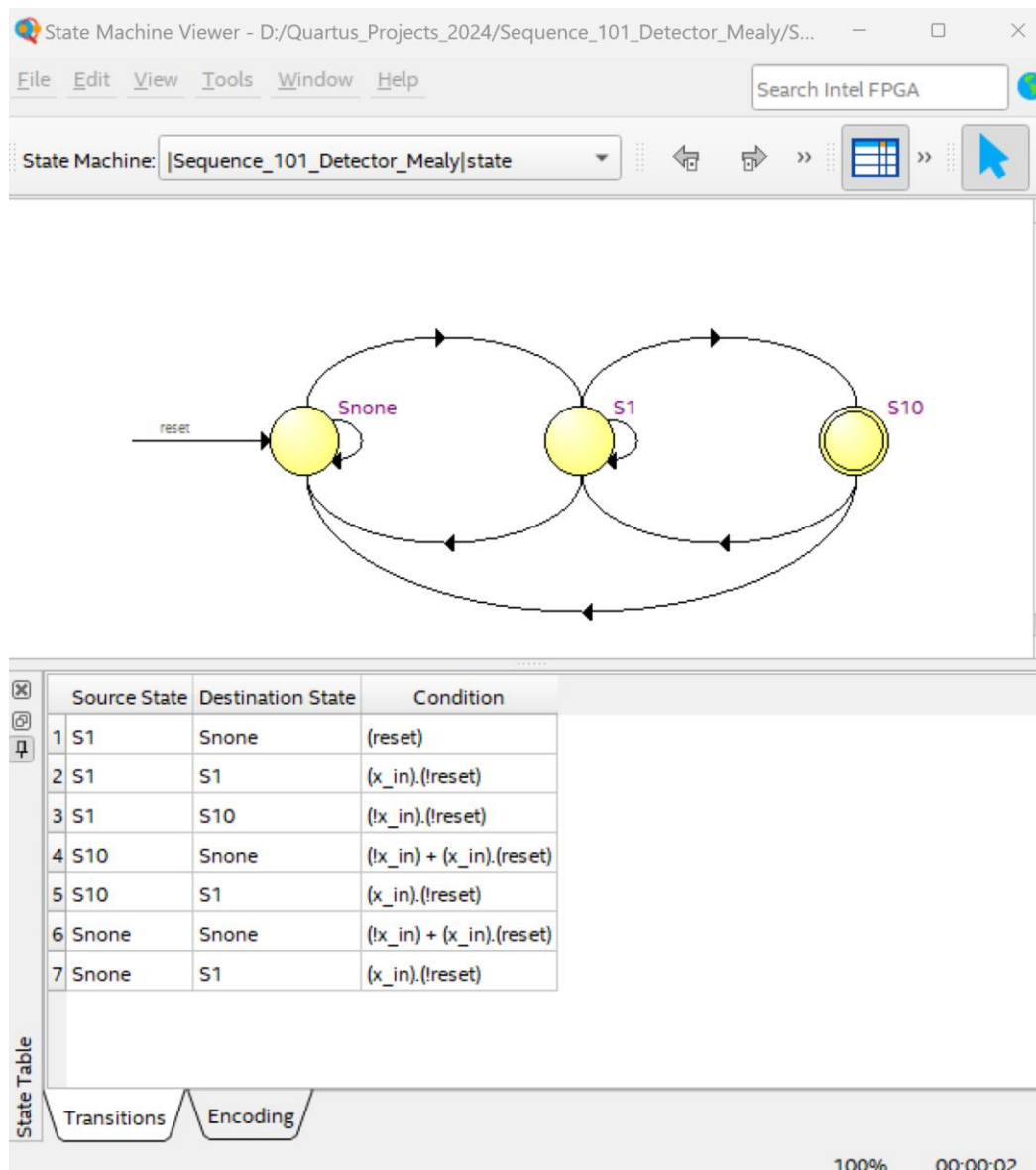To obtain and verify the FSM state graph, go to **Tools, Netlist Viewer, State Machine Viewer**, or double click on the flip flop register in the RTL viewer.



```

module Sequence_101_Detector_Mealy_TB ();

wire    z_out;
reg     clk, reset;
reg     x_in;

wire [1:0] state, next_state;    // internal probes

Sequence_101_Detector_Mealy UUT (z_out, clk, reset, x_in);

// internal probes to make it easy to track the logic and for troubleshooting
assign state = UUT.state;
assign next_state = UUT.next_state;

initial
begin
    clk = 1'b0;
    forever begin
        #5 clk = ~clk;    end
    end

initial
begin
    reset = 1'b1;
    # 30 reset = 1'b0;
    #200 reset = 1'b1;
    # 30 reset = 1'b0;
end

initial
begin
    x_in = 1'b0;        #15

    forever begin

        x_in = 1'b1; #10 x_in = 1'b0; #10 x_in = 1'b1; #10; // 101 sequence
        x_in = 1'b0; #10 x_in = 1'b1; #10 x_in = 1'b1; #10; // 011
        x_in = 1'b1; #10 x_in = 1'b0; #10 x_in = 1'b1; #10; // 101 sequence
        x_in = 1'b0; #10 x_in = 1'b1; #10 x_in = 1'b0; #10; // overlapping 101
        x_in = 1'b1; #10 x_in = 1'b0; #10 x_in = 1'b0; #10; // overlapping
        x_in = 1'b0; #10 x_in = 1'b0; #10 x_in = 1'b0; #10; // 000
        x_in = 1'b1; #10 x_in = 1'b1; #10 x_in = 1'b1; #10; // 111
        x_in = 1'b0; #10 x_in = 1'b1; #10 x_in = 1'b1; #10; // 1..011
    end
end
endmodule

```

