

```

1  /*-----*/
2  Name Lamin Jammeh
3  Class: EE417 Summer 2024
4  Lesson 06 HW Question 2
5  Group: Ron Kalin/ Lamin Jammeh
6  Project Description: This is the main module, it detects a comma symbol 4b'1101 once
7  the symbol is detect the index of the MSB of the symbol and send it as an output
8  -----*/
9  module comma_1101_search #(parameter word_size = 32,
10                          index_size = 4)
11      (output reg [index_size:0] index_out,      //4 bits index
12       [4:0]=16+8+4+2+1=31, possible index_out = 0:31
13       input  [word_size - 1:0] word_in,        //32 bits input [31:0]
14       input  trigger);                        //triggers the count
15  the comma code
16  always @ (posedge trigger)
17      begin: search_code
18          temp_reg = word_in;                  //copying the result into the
19  temporary register
20          for (index_out = 3; index_out < (word_size); index_out = (index_out + 1))
21              begin
22                  if (temp_reg[3:0] == 4'b1101) disable search_code; //always check the 3LSBs
23                  else begin
24                      temp_reg = temp_reg >> 1;                //shift the
25  temp_reg to the right
26                      if ((temp_reg == 0) | (index_out == (word_size - 1))) //the
27  temp_reg is all 0s
28                          begin
29                              index_out = 4'b0000;
30                              disable search_code;
31                              end
32                          end
33                  end
34          end
35  end
36  endmodule

```

```
1  /*-----*
2  Name Lamin Jammeh
3  Class: EE417 Summer 2024
4  Lesson 06 HW Question 2
5  Group: Ron Kalin/ Lamin Jammeh
6  Project Description: This is the test-bench for the comma symbol 4b'1101 detector
7  -----*/
8  module comma_1101_search_tb ();
9
10 //set the parameters wires and registers
11 parameter          word_size  = 32;
12 parameter          index_size = 4 ;
13 wire      [index_size:0] index_out;
14 reg       [word_size - 1:0] word_in;
15 reg                               trigger;
16
17 //define the unit under test UUT
18 comma_1101_search UUT (index_out, word_in, trigger);
19
20 //instantiate the trigger signal
21 initial begin
22     trigger      = 1'b0;
23     forever
24         #10      trigger = ~trigger;
25     end
26
27 //define the word input and observe the outputs
28 initial fork
29     word_in = 32'b_0000_0000_0000_0000_0000_0000_1101;
30     #40 word_in = 32'b_0000_1010_1010_0000_1101_0000_0000_0000;
31     #80 word_in = 32'b_1110_0000_0000_1101_1010_1010_0000_1001;
32     #120 word_in = 32'b_0000_0000_0000_0000_1111_1111_1101_0000;
33     #160 word_in = 32'b_1101_0101_0000_1111_0000_1010_1010_0000;
34     #200 word_in = 32'b_1111_1111_1111_1111_1111_1111_1101_0000;
35     #240 word_in = 32'b_0000_1010_1011_0111_1101_0101_0000_1111;
36     #280 word_in = 32'b_0000_1101_0000_1111_0000_1101_0000_1010;
37     join
38
39 ////monitor and display the output
40 initial
41     $monitor ($time,, "word_in = %b: index_out = %d", word_in, index_out);
42 endmodule
```

Wave - Default

Logic

trigger\_input  
/comma\_1101\_search\_0/trigger  
word\_in  
/comma\_1101\_search\_0/word\_in  
index\_out  
/comma\_1101\_search\_0/index\_out

170  
32h0d0f0d0a  
5d11

(trigger\_input)  
(word\_in)  
00000000 0a0d000 e00da09 0000f59 d50f0a0 fffffff0 0ab7d50f 0d0f0d0a  
(index\_out)  
0 15 16 17 18 19 20 21

Now 505588.12 ns  
Cursor 1 0.00 ns

0.05 ns 0.1 ns 0.15 ns 0.2 ns 0.25 ns 0.3 ns

[illegible]

- The design takes in a 32 bits input as word\_in
- Checks for a 4-bit set of 1101 and marks the index of the MSB of the set
- If the set is not found in the first 4 bits the index shifts one bit to the right and looks at the next 4 bits
- Once the set is found the index of the MSB is reported as index\_out
- If all 32 bits are checked OR a set of 1101 is not found index\_out becomes zero