 


Problem 2: (25 points)

Design a glitch-free Manchester-to-NRZ Mealy FSM data converter. Your submission should include:

- A state graph for your FSM. (5 points)
- A screen shot of your Verilog code for the data converter. (10 points)
- A screen shot of your testbench. Make sure that you do not align your data_in transitions with the clock to show how you were able to implement a glitch-free design. (4 points)
- A screenshot of your simulation results. (6 points)



```
/*-----
Manchester_2_NRZ Serial Data Line converter:
-----
This design will have two examples, one with registered output
to avoid glitches and one with an output directly connected
to combinational logic. The data_in is not aligned with the
positive clock edge. The registered output design is glitch free
while the simple Mealy FSM will have glitches.
The two designs will be combined in one top module and tested
using the same testbench to compare the simulation output.
The modules included:
- Manchester_NRZ_glitchy
- Manchester_NRZ_nonglitchy
- Manchester_2_NRZ (top module)
- Manchester_2_NRZ_tb (testbench)
-----*/

module Manchester_2_NRZ (input reset_in,
                        input clk_in,
                        input Manchester_in,
                        output NRZ_glitchy,
                        output NRZ_nonglitchy);

Manchester_NRZ_glitchy M1 (.reset (reset_in),
                           .clk (clk_in),
                           .Manchester (Manchester_in),
                           .NRZ_out (NRZ_glitchy) );

Manchester_NRZ_nonglitchy M2 (.reset (reset_in),
                              .clk (clk_in),
                              .Manchester (Manchester_in),
                              .NRZ_out (NRZ_nonglitchy) );

endmodule
```

```

module Manchester_NRZ_glitchy (reset, clk, Manchester, NRZ_out);

input      reset, clk, Manchester;
output reg  NRZ_out;                // to assign it values within the always block
reg [1:0]   state, next_state;

parameter RSt  = 2'b11;
parameter ONE  = 2'b01;
parameter ZERO = 2'b00;

// Sequential logic to update the state:
always @ (posedge clk)
    if (reset) state <= RSt;
    else      state <= next_state;

// Combinational logic to update the next_state and NRZ_out:
always @ *
    case (state)
        RSt      :    if (Manchester) begin
                        next_state = ONE;   NRZ_out = 1'b1;   end
                      else begin
                        next_state = ZERO;   NRZ_out = 1'b0;   end
        ONE       :    begin next_state = RSt;   NRZ_out = 1'b1;   end
        ZERO      :    begin next_state = RSt;   NRZ_out = 1'b0;   end
        default   :    begin next_state = RSt;   NRZ_out = 1'b0;   end
    endcase

endmodule

```

```

module Manchester_NRZ_nonglitchy (reset, clk, Manchester, NRZ_out);

input      reset, clk, Manchester;
output reg  NRZ_out;
reg        next_NRZ;
reg [1:0]   state, next_state;

parameter RSt  = 2'b11;
parameter ONE  = 2'b01;
parameter ZERO = 2'b00;

// Sequential logic to update the state and the NRZ output:
always @ (posedge clk)
    if (reset) begin state <= RSt;           NRZ_out <= 1'b0;   end
    else      begin state <= next_state;     NRZ_out <= next_NRZ; end

// Combinational logic to update the next_state and next_NRZ:
always @ *
    case (state)
        RSt      :    if (Manchester) begin
                        next_state = ONE;   next_NRZ = 1'b1;   end
                      else begin
                        next_state = ZERO;   next_NRZ = 1'b0;   end
        ONE       :    begin next_state = RSt;   next_NRZ = 1'b1;   end
        ZERO      :    begin next_state = RSt;   next_NRZ = 1'b0;   end
        default   :    begin next_state = RSt;   next_NRZ = 1'b0;   end
    endcase

endmodule

```

```

module Manchester_2_NRZ_tb ();

reg reset_in;
reg clk_in;
reg Manchester_in;
wire NRZ_glitchy;
wire NRZ_nonglitchy;

Manchester_2_NRZ uut (reset_in, clk_in, Manchester_in, NRZ_glitchy, NRZ_nonglitchy);

initial
begin
    clk_in = 1'b0;
    forever begin
        #10 clk_in = ~clk_in;    end    end

initial
begin
    reset_in = 1'b1;
    #95 reset_in = 1'b0;    end

initial
begin
    Manchester_in = 1'b0;
    #5 Manchester_in = 1'b1;    // 10 represents 1
    #20 Manchester_in = 1'b0;
    forever begin
        #20 Manchester_in = 1'b1;    // 10 represents 1
        #20 Manchester_in = 1'b0;

        #20 Manchester_in = 1'b0;    // 01 represents 0
        #20 Manchester_in = 1'b1;

        #20 Manchester_in = 1'b0;    // 01 represents 0
        #20 Manchester_in = 1'b1;

        #20 Manchester_in = 1'b1;    // 10 represents 1
        #20 Manchester_in = 1'b0;

        #20 Manchester_in = 1'b0;    // 01 represents 0
        #20 Manchester_in = 1'b1;    end
    end

endmodule

```

