 


```
1 // ee417 lesson 9 Assignment 1 L9A1
2 // Name: Ron Kalin, Date: 07-10-24 Group: Kalin/Jammeh
3 // Design: moving average FIR filter of overlapping windows of 4 input samples
4 // FIR order will be a power of 2, parameterized with word_size
5 // top level module
6 module moving_average_filter #(parameter word_size=8, order=4, n=2)(
7     output reg [2*word_size-1:0] filtered_sample,
8     input [word_size-1:0] sample_in,
9     input enable, clk, reset
10 );
11 // Coefficient values for a 4-tap moving average filter
12 //reg [word_size-1:0] coeff [0:order] = {16'h1000, 16'h1000, 16'h1000, 16'h1000};
13 reg [word_size-1:0] coeff0 = 4'd1; //coefficients of one were selected
14 reg [word_size-1:0] coeff1 = 4'd1; //because for moving average they aren't needed
15 reg [word_size-1:0] coeff2 = 4'd1;
16 reg [word_size-1:0] coeff3 = 4'd1;
17 reg [word_size-1:0] tap_outputs [0:3];
18
19 // Circular buffer to store input samples
20 reg [word_size-1:0] buffer0, buffer1, buffer2, buffer3;
21 reg [word_size-1:0] buffer [0:order-1];
22 always @(posedge clk) begin
23     if (reset || ~enable) begin
24         buffer0 = 0;
25         buffer1 = 0;
26         buffer2 = 0;
27         buffer3 = 0;
28     end else if (enable) begin
29         buffer3 = buffer2;
30         buffer2 = buffer1;
31         buffer1 = buffer0;
32         buffer0 = sample_in;
33     end
34     // Multipliers and accumulator
35     tap_outputs[0] = buffer0 * coeff0; //coeff[0];
36     tap_outputs[1] = buffer1 * coeff1; //coeff[1];
37     tap_outputs[2] = buffer2 * coeff2; //coeff[2];
38     tap_outputs[3] = buffer3 * coeff3; //coeff[3];
39
40     filtered_sample = (buffer0 + buffer1 + buffer2 + buffer3); // >> 2;
41     //filtered_sample = buffer[0] + buffer[1] + buffer[2] + buffer[3];
42     //filtered_sample <= (tap_outputs[0] + tap_outputs[1] + tap_outputs[2] + tap_outputs[3])
43     // Right shift by 2 bits to approximate division by 4
44     filtered_sample = (filtered_sample >> n); //shift n places to divide by 2^n
45     //shift n places requires 2^n samples (buffers and coefficients)
46 end
47 endmodule
48
49
```



```

1  /*-----*/
2  Name Ron Kalin
3  Class: EE417 Summer 2024
4  Lesson 09 HW Question 01
5  Group: Ron Kalin/ Lamin Jammeh
6  Project Description: test-bench for moving average FIR filter
7  -----*/
8  module moving_average_filter_tb();
9      // Parameters
10     parameter DATA_WIDTH = 8;
11     parameter FILT_LENGTH = 4;
12
13     // Signals
14     reg clk, reset, enable;
15     reg [DATA_WIDTH-1:0] sample_in;
16     wire [2*DATA_WIDTH-1:0] filtered_sample;
17
18     //wires monitor internal variables
19     wire [DATA_WIDTH-1:0] buffer0, buffer1, buffer2, buffer3;
20     wire [DATA_WIDTH-1:0] coeff0, coeff1,coeff2,coeff3;
21     wire [DATA_WIDTH-1:0] tap_outputs [0:3];
22
23     // Instantiate the moving_average_filter module
24     moving_average_filter UUT (
25         .filtered_sample(filtered_sample),
26         .sample_in(sample_in),
27         .enable(enable),
28         .clk(clk),
29         .reset(reset)
30     );
31     assign buffer0 =UUT.buffer0;
32     assign buffer1 =UUT.buffer1;
33     assign buffer2 =UUT.buffer2;
34     assign buffer3 =UUT.buffer3;
35     assign coeff0  =UUT.coeff0;
36     assign coeff1  =UUT.coeff1;
37     assign coeff2  =UUT.coeff2;
38     assign coeff3  =UUT.coeff3;
39     assign tap_outputs[0]=UUT.tap_outputs[0];
40     assign tap_outputs[1]=UUT.tap_outputs[1];
41     assign tap_outputs[2]=UUT.tap_outputs[2];
42     assign tap_outputs[3]=UUT.tap_outputs[3];
43
44     // Clock generation
45     always #5 clk = ~clk;
46
47     // Test stimulus
48     initial begin
49         clk = 0;
50         reset = 1;
51         #10 reset = 0; enable =1; // Release reset, enable
52         #20 sample_in = 8'b0000_0000; // input sample of 0
53         #20 sample_in = 8'b0000_0000; // input sample of 0
54         #20 sample_in = 8'b0000_0100; // input sample of 4
55         #20 sample_in = 8'b0000_0000; // input sample of 0
56         #20; // wait for some cycles
57
58         // Applying additional test vectors
59         #20 sample_in = 8'b0001_0001; // input sample of 17
60         #20 sample_in = 8'b0010_0001; // input sample of 33
61         #20 sample_in = 8'b0011_0001; // input sample of 49
62         #20 sample_in = 8'b0100_0001; // input sample of 65
63         #20 sample_in = 8'b0101_0001; // input sample of 81
64         #20 sample_in = 8'b0110_0001; // input sample of 97
65         #20 sample_in = 8'b0111_0001; // input sample of 113
66         #20 sample_in = 8'b1000_0001; // input sample of 129
67         #20 sample_in = 8'b1001_0001; // input sample of 145
68         #20 sample_in = 8'b1010_0001; // input sample of 161
69         #20 sample_in = 8'b1011_0001; // input sample of 177

```

```
70     #20 enable =0;
71     #40 enable =1;
72     #20 sample_in = 8'b1100_0001; // input sample of 193
73     #20 sample_in = 8'b1101_0001; // input sample of 209
74     #20 sample_in = 8'b1110_0001; // input sample of 225
75     #20 sample_in = 8'b1111_0001; // input sample of 241
76     #20 sample_in = 8'b1000_0001; // input sample of 129a
77     #20; // wait for some cycles
78
79     $display("Filtered Output: %h", filtered_sample);
80     //$finish;
81     $stop;
82 end
83
84 // Display the results
85 always @(posedge clk)
86 begin
87     $display("Filtered Output: %h", filtered_sample);
88 end
89
90 endmodule
```

```
1
2 # Filtered Output: xxxx
3 # Filtered Output: 0000
4 # Filtered Output: Xxxx
5 # Filtered Output: Xxxx
6 # Filtered Output: Xxxx
7 # Filtered Output: Xxxx
8 # Filtered Output: Xxxx
9 # Filtered Output: 0000
10 # Filtered Output: 0001
11 # Filtered Output: 0002
12 # Filtered Output: 0002
13 # Filtered Output: 0002
14 # Filtered Output: 0001
15 # Filtered Output: 0000
16 # Filtered Output: 0004
17 # Filtered Output: 0008
18 # Filtered Output: 0010
19 # Filtered Output: 0019
20 # Filtered Output: 0021
21 # Filtered Output: 0029
22 # Filtered Output: 0031
23 # Filtered Output: 0039
24 # Filtered Output: 0041
25 # Filtered Output: 0049
26 # Filtered Output: 0051
27 # Filtered Output: 0059
28 # Filtered Output: 0061
29 # Filtered Output: 0069
30 # Filtered Output: 0071
31 # Filtered Output: 0079
32 # Filtered Output: 0081
33 # Filtered Output: 0089
34 # Filtered Output: 0091
35 # Filtered Output: 0099
36 # Filtered Output: 00a1
37 # Filtered Output: 00a9
38 # Filtered Output: 0000
39 # Filtered Output: 0000
40 # Filtered Output: 0000
41 # Filtered Output: 0000
42 # Filtered Output: 002c
43 # Filtered Output: 0058
44 # Filtered Output: 0088
45 # Filtered Output: 00b9
46 # Filtered Output: 00c1
47 # Filtered Output: 00c9
48 # Filtered Output: 00d1
49 # Filtered Output: 00d9
50 # Filtered Output: 00e1
51 # Filtered Output: 00e9
52 # Filtered Output: 00d1
53 # Filtered Output: 00b9
54
```

Bitwave

