 


```

1 // ee417 lesson 11 Assignment 1 L11A1
2 // Name: Ron Kalin, Date: 07-25-24 Group: Kalin/Jammeh
3 // Design: FIFO using common clock for reading and writing, with reset.
4 // FIFO has input & output data ports, & flags denoting status of the stack (full or empty).
5 // FIFO module should not support simultaneous read & write, and gives preference to the
  read operation.
6 // parameters are used for the stack height and width. starting point: data width=5 & stack
  height=8
7 module FIFO ( Data_out,      // data path from FIFO
8               stack_empty,   // flag asserted high for empty stack
9               stack_almost_empty,
10              stack_full,     // flag asserted high for full stack
11              stack_almost_full,
12              Data_in,        // data path into FIFO
13              write_to_stack, // input controlling write to stack
14              read_from_stack, // input controlling read to stack
15              clk,            // clock
16              rst );          // reset
17 parameter stack_width = 5;    // width of stack and data points (bit length of word)
18 parameter stack_height = 8;   // height of stack (# of words)
19 parameter stack_ptr_width = $clog2(stack_height); //3; // pointer width stack addresses,
  log2 fcn = no. bits to represent addr for all values in stack
20
21 output [stack_width - 1 : 0] Data_out;
22 output stack_empty, stack_full;
23 output stack_almost_empty, stack_almost_full;
24 input [stack_width - 1 : 0] Data_in;
25 input write_to_stack, read_from_stack;
26 input clk, rst;
27
28 // Pointers for reading and writing
29 reg [stack_ptr_width - 1 : 0] read_ptr, write_ptr;
30 reg [stack_ptr_width : 0] ptr_diff; //pointer difference
31 reg [stack_width - 1 : 0] Data_out; //declaring as output register
32 reg [stack_width - 1 : 0] stack [stack_height - 1 : 0]; // memory array
33
34 /*assign stack_empty = (ptr_diff == 0) ? 1 : 0; //1'b1 : 1'b0; //single bit setup
35 assign stack_full = (ptr_diff == stack_height) ? 1 : 0; //1'b1 : 1'b0;*/
36
37 assign stack_empty = (ptr_diff == 0) ? 1 : 0; //stack fullness indicators
38 assign stack_full = (ptr_diff == stack_height) ? 1 : 0;
39 assign stack_almost_empty = (ptr_diff == 1) ? 1 : 0;
40 assign stack_almost_full = (ptr_diff == stack_height - 1) ? 1 : 0;
41
42 always @ (posedge clk or posedge rst)
43 begin
44   if (rst) begin
45     Data_out <= 0; // reset output and pointers to zero
46     read_ptr <= 0;
47     write_ptr <= 0;
48     ptr_diff <= 0;
49   end
50
51   else begin
52     if ( (read_from_stack) && (!stack_empty) ) //prioritize reading over writing
53       begin
54         Data_out <= stack [read_ptr]; //send stack to data_out
55         read_ptr <= read_ptr + 1; // incr read pointer
56         ptr_diff <= ptr_diff - 1; // decr pointer diff
57       end
58     else if ( (write_to_stack) && (!stack_full) )
59       begin
60         stack [write_ptr] <= Data_in; //send stack to data_in
61         write_ptr <= write_ptr + 1; // incr write pointer
62         ptr_diff <= ptr_diff + 1; // incr pointer diff
63       end
64   end
65 end
66 endmodule

```



```

1  //Name: Ron Kalin EE417 Summer 2024, Date: 07/25/24
2  //Group: Ron Kalin/ Lamin Jammeh
3  //Lesson 11 HW Question 01. Project: test-bench for FIFO
4  module FIFO_tb ();
5  parameter stack_width = 5; // width of stack and data paths (word length)
6  parameter stack_height = 8; // height of stack (# of words)
7  parameter stack_ptr_width = $clog2(stack_height); //3;// width of pointer to address stack
8  //declare outputs and inputs
9  wire [stack_width-1 : 0] Data_out;
10 wire stack_empty, stack_full;
11 wire stack_almost_empty, stack_almost_full;
12 reg [stack_width-1 : 0] Data_in;
13 reg [stack_width-1 : 0] Data_in_array [stack_height-1 : 0]; //internal register array
14 of data
15 reg clk, rst;
16 reg write_to_stack, read_from_stack;
17 wire [stack_width-1: 0] stack0, stack1, stack2, stack3,
18 stack4, stack5, stack6, stack7;
19 wire [stack_ptr_width-1: 0] read_ptr, write_ptr;
20 wire [stack_ptr_width : 0] ptr_diff; //pointer difference
21 integer
22 j;
23 //initialize the unit under testM1
24 FIFO M1 ( Data_out, stack_empty, stack_almost_empty, stack_almost_full, stack_full,
25 Data_in, write_to_stack, read_from_stack, clk, rst );
26 // assign probe wires for troubleshooting and visibility
27 assign stack0 = M1.stack [0];
28 assign stack1 = M1.stack [1];
29 assign stack2 = M1.stack [2];
30 assign stack3 = M1.stack [3];
31 assign stack4 = M1.stack [4];
32 assign stack5 = M1.stack [5];
33 assign stack6 = M1.stack [6];
34 assign stack7 = M1.stack [7];
35 assign read_ptr = M1.read_ptr;
36 assign write_ptr = M1.write_ptr;
37 assign ptr_diff = M1.ptr_diff;
38
39 always begin clk = 0; forever #5 clk = ~clk; end // create clock
40 initial #1500 $stop;
41
42 initial begin
43 #10 rst = 1; #40 rst = 0; #420 rst = 1; # 460 rst = 0; end // cycle reset
44
45 initial begin
46 $readmemb ("FIFO_Input_Data.txt", Data_in_array); // read data to Data_in_array from
47 text file saved in simulation path
48 end
49
50 initial begin
51 // #80 Data_in = 1; forever #10 Data_in = Data_in + 1; //manual method for creating Data_in
52 #80 Data_in = 1;
53 for (j=0; j<stack_height; j=j+1)
54 begin
55 Data_in = Data_in_array[j]; // data in coming from text file
56 $display("Data_out: %u, Data_in: %u", Data_out, Data_in );
57 end //for
58 end
59
60 initial fork // cycling read/write inputs
61 # 80 write_to_stack = 1;
62 #180 write_to_stack = 0;
63 #250 read_from_stack = 1;
64 #350 read_from_stack = 0;
65 #420 write_to_stack = 1;
66 #480 write_to_stack = 0;
67 join

```

```
67
68 //display results
69 always @(posedge clk)
70 begin
71     $display("Data_out: %u, Data_in: %u, Data_in_array: %u, write_to_stack: %b,
72     read_from_stack: %b, stack_empty: %b, stack_full: %b",
73     Data_out, Data_in, Data_in_array, write_to_stack, read_from_stack, stack_empty,
74     stack_full );
75 end
76
77 endmodule
```

