



Objective: Behavioral Models in Verilog - Designing combinational circuits that can perform binary-to-decimal number conversion.

Part (1): Seven Segment Display (Book example page 170 & 171)

We wish to display on 7-segment display the values set by 4 input switches. Your circuit should be able to display the digits from 0 to 9 and should treat the values 1010 to 1111 as BLANK display (all OFF). The LEDs for the 7-segment display are all active low (common anode), which means that the LED would turn ON when its assigned bit value is a logic '0'.

Create a design that assigns the correct output bits to the 7-segments based on the 4-bit input value. Use parameters for the 10 different decimal digits (0 to 9) and the BLANK case.

```
parameter BLANK = 7'b_1111_1111;  
parameter ZERO  = 7'b_0000_0001;
```

Part (2): Binary-Coded Decimal

You are to design a circuit that converts a four-bit binary number $V = v_3 v_2 v_1 v_0$ into its two-digit decimal equivalent $D = d_1 d_0$. Table 1 shows the required output values.

$v_3 v_2 v_1 v_0$	d_1	d_0
0000	0	0
0001	0	1
0010	0	2
...
1001	0	9
1010	1	0
1011	1	1
1100	1	2
1101	1	3
1110	1	4
1111	1	5

Table 1: Binary-to-decimal conversion values.

Structural Design:

It includes a comparator that checks when the value of V is greater than 9 and uses the output of this comparator in the control of the 7-segment displays. You can use the conditional and comparison operators.

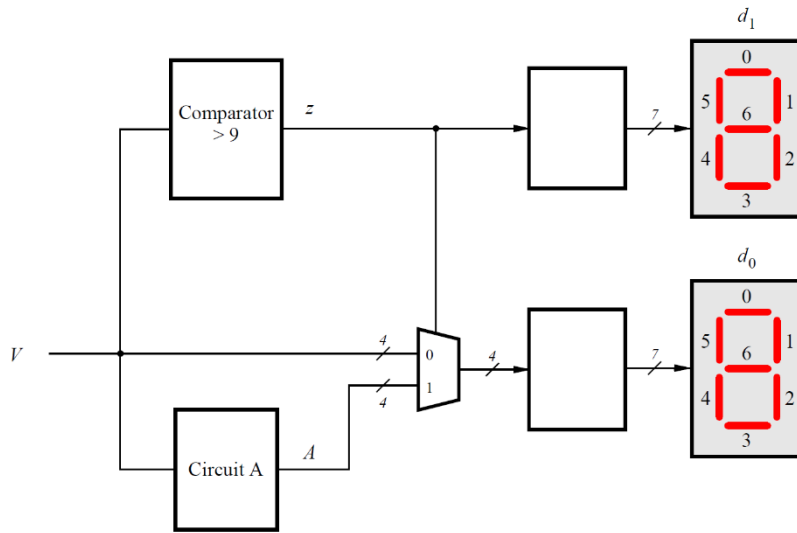


Figure 1: Partial design of the binary-to-decimal conversion circuit.

Notice that the circuit in Figure 1 includes a 4-bit wide 2-to-1 multiplexer. The purpose of this multiplexer is to drive digit d_0 with the value of V when $z = 0$, and the value of A when $z = 1$. To design circuit A consider the following. For the input values $V < 9$, the circuit A does not matter, because the multiplexer in Figure 1 just selects V in these cases. But for the input values $V > 9$, the multiplexer will select A . Thus, A has to provide output values that properly implement Table 1 when $V > 9$.

You need to design circuit A so that the input $V = 1010$ gives an output $A = 0000$, the input $V = 1011$ gives the output $A = 0001$, and the input $V = 1111$ gives the output $A = 0101$. Design circuit A using a case structure.

The top code module should instantiate the needed submodules with correct interconnections.

EE 417 - Assignment 3 – Problem 3 – BCD – Seven Segment Display

```

module BCD_SevenSegment (v, do_7segment, d1_7segment);

input    [3:0]  v;
output   [6:0]  do_7segment, d1_7segment;
wire     [3:0]  digit0, do, d1;
wire     v_grtr9;

parameter BLANK = 7'b111_1111; // 127
parameter ONE  = 7'b111_1001; // 121

assign v_grtr9    = (v > 4'b1001);
assign d1_7segment = v_grtr9 ? ONE    : BLANK;
assign d1         = v_grtr9 ? 4'b0001 : 4'b0000;
assign do         = v_grtr9 ? digit0 : v;

circuitA      M1 (v, digit0) ;
Binary_7segment D0 (do, do_7segment);

endmodule

```

```

module circuitA (v, do) ;
input    [3:0]  v;
output reg [3:0]  do;

always @ *
    case (v)
        4'b1010 : do = 4'b0000;
        4'b1011 : do = 4'b0001;
        4'b1100 : do = 4'b0010;
        4'b1101 : do = 4'b0011;
        4'b1110 : do = 4'b0100;
        4'b1111 : do = 4'b0101;
        default  : do = 4'bxxxx;
    endcase
endmodule

```

```

module Binary_7segment (BCD, SevenSegment);
input    [3:0]  BCD;
output reg [6:0]  SevenSegment;

parameter BLANK = 7'b111_1111; // 127
parameter ZERO  = 7'b100_0000; // 64
parameter ONE   = 7'b111_1001; // 121
parameter TWO   = 7'b010_0100; // 36
parameter THREE = 7'b011_0000; // 48
parameter FOUR  = 7'b001_1001; // 25
parameter FIVE  = 7'b001_0010; // 18
parameter SIX   = 7'b000_0001; // 1
parameter SEVEN = 7'b111_1000; // 120
parameter EIGHT = 7'b000_0000; // 0
parameter NINE  = 7'b001_1000; // 24

always @ *
    case (BCD)
        4'b0000 : SevenSegment = ZERO;
        4'b0001 : SevenSegment = ONE;
        4'b0010 : SevenSegment = TWO;
        4'b0011 : SevenSegment = THREE;
        4'b0100 : SevenSegment = FOUR;
        4'b0101 : SevenSegment = FIVE;
        4'b0110 : SevenSegment = SIX;
        4'b0111 : SevenSegment = SEVEN;
        4'b1000 : SevenSegment = EIGHT;
        4'b1001 : SevenSegment = NINE;
        default  : SevenSegment = BLANK;
    endcase

endmodule

```

```

module BCD_SevenSegment_tb ();

reg [3:0] BCD;
wire [6:0] do_7segment, d1_7segment;
wire [3:0] do, d1;
wire V_grtr9;
wire [3:0] digit0;


BCD_SevenSegment UUT (BCD, do_7segment, d1_7segment);

assign V_grtr9 = UUT.V_grtr9;
assign do      = UUT.do;
assign d1      = UUT.d1;
assign digit0  = UUT.digit0;

initial
begin
BCD = 4'b0000;
forever
begin
#10 BCD = BCD + 1;
end
end

endmodule

```

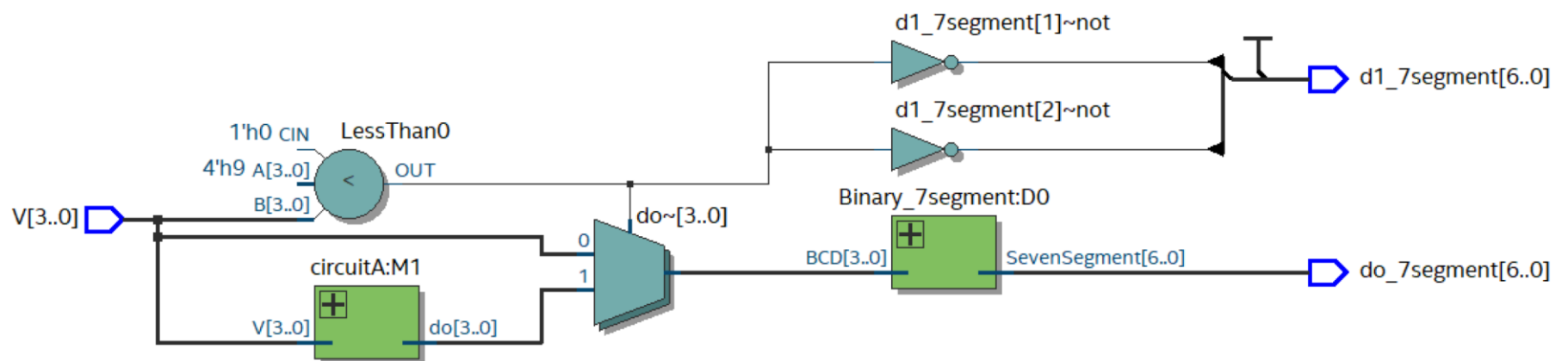


(inputBCD)																
0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	0
(output d1)																
0										1						0
(output do)																
0	1	2	3	4	5	6	7	8	9	0	1	2	3	4	5	0
(d1_7Segment)																
127										121						127
(do_7Segment)																
64	121	36	48	25	18	1	120	0	24	64	121	36	48	25	18	64
(input greater than 9)																
(internal do)																
										0	1	2	3	4	5	

```

BLANK = 7'b111_1111; // 127
ZERO  = 7'b100_0000; // 64
ONE    = 7'b111_1001; // 121
TWO    = 7'b010_0100; // 36
THREE  = 7'b011_0000; // 48
FOUR   = 7'b001_1001; // 25
FIVE   = 7'b001_0010; // 18
SIX    = 7'b000_0001; // 1
SEVEN  = 7'b111_1000; // 120
EIGHT  = 7'b000_0000; // 0
NINE   = 7'b001_1000; // 24

```



7-segment display

 


pin connected to FPGA output pin

LED 0 has its anode connected to high voltage (3V for example)

 
 
The cathode is connected to an FPGA pin assigned to the bit `display[0]`.



 If the 7-segment display is blank and all LEDs will be off, then
`display[6:0] = 7'b111_1111`




display word

  

If the 7-segment display should show a digit zero, then all LEDs should be ON except LED 6.
`display[6,0] = 7'b100_0000`

BCD_greater_9

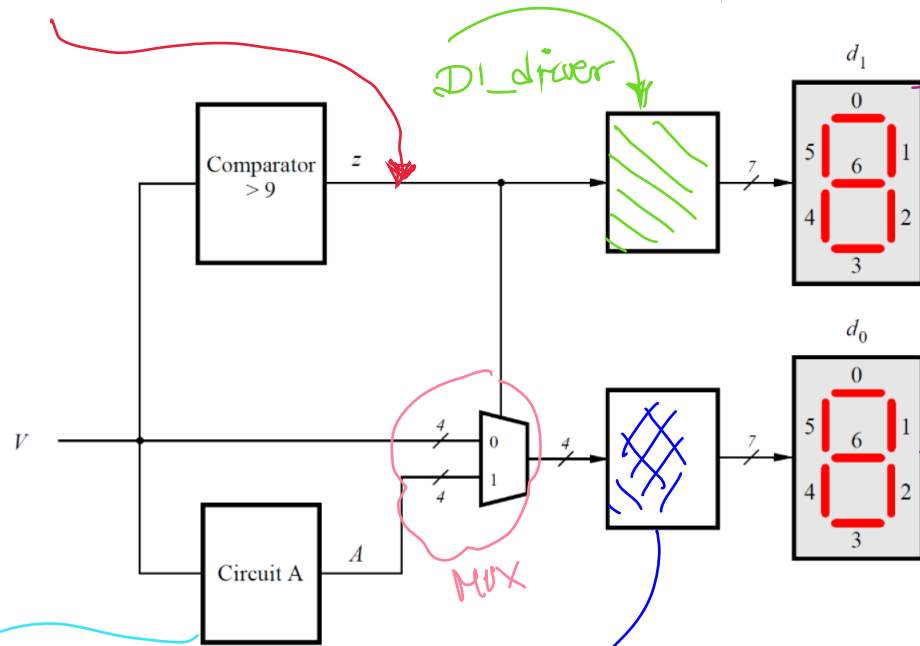If $V \geq 9$ display \Rightarrow ONE
 $V < 9$ display \Rightarrow Blank



Displaying the ten's digit
 For 4 bit inputs the values range goes from 0 \rightarrow 15, hence d_1 will be either blank or 1.

Displaying the one's digit

In case $V > 9$
 module A should find the correct value for d_0 equivalent binary value

V in decimal	d_1
10	0
11	1
12	2
13	3
14	4
15	5

BCD_to_Seven

module that takes 4 bit word representing values from 0 \rightarrow 9 and finds the corresponding 7 bit display word that will be driving the 7-segment display.

Binary_in	Decimal	display
0000	0	100_0000
0001	1	111_1001
0010	2	010_0100
0011	3	011_0000
...
1001	9	001_1000

```
module DI_driver (V_greater_than_9_in, display_d1_out);
```

```
input V_greater_than_9_in;
```

```
output [6:0] display_d1_out;
```

```
parameter Blank = 7'b111_1111; // Giving special numbers a name to
```

```
parameter ONE = 7'b111_1001; // make the code more readable.
```

```
// Conditional operator
```

```
assign display_d1_out = (V_greater_than_9_in ?) ONE : Blank;
```

```
endmodule
```

// Another way to design DI_driver is by using a case structure

```
module DI_driver (V_greater_than_9_in, display_d1_out);
```

```
input V_greater_than_9_in;
```

```
output reg [6:0] display_d1_out; // If assigned a value within case structure then  
// it has to be defined as register.
```

```
always @ (V_greater_than_9_in)
```

```
case (V_greater_than_9_in)
```

```
1'b0 : display_d1_out = 7'b111_1111;
```

```
1'b1 : display_d1_out = 7'b111_1001;
```

```
default : display_d1_out = 7'b111_1111;
```

// or use parameters as we did before ↑

endcase

endmodule

Circuit A will have an effect if the input word V is greater than 9.

```
module circuitA (V, A);  
    input [3:0] V;  
    output reg [3:0] A; // Had to define A as a reg to assign it values  
                        // within the always block.  
    always @ (V)  
    case (V)  
        4'b1010 : A = 4'b0000; // 10  
        4'b1011 : A = 4'b0001; // 11  
        4'b1100 : A = 4'b0010; // 12  
        4'b1101 : A = 4'b0011; // 13  
        4'b1110 : A = 4'b0100; // 14  
        4'b1111 : A = 4'b0101; // 15  
        default : A = 4'bxxxx;  
    endcase  
endmodule
```

We could have also designed the module circuit using combinational logic with K-map for every binary output bit

For A_2 :

$V_3 V_2 V_1 V_0$	$A_3 A_2 A_1 A_0$
1 0 1 0	0 0 0 0
1 0 1 1	0 0 0 1
1 1 0 0	0 0 1 0
1 1 0 1	0 0 1 1
1 1 1 0	0 1 0 0
1 1 1 1	0 1 0 1

$V_3 V_2 \backslash V_1 V_0$	00	01	11	10
00	X 0	X 4	0 12	X 8
01	X 1	X 5	0 13	X 9
11	X 3	X 7	1 15	0 10
10	X 2	X 6	1 14	0 11

all the values less than or equal to 9 are don't cares.

$$A_2 = V_2 V_1$$

$$\text{assign } A[3] = 1'b0;$$

$$\text{assign } A[2] = V[2] \& V[1];$$

$$\text{assign } A[1] = V[2] \& (\sim V[1]);$$

$$\text{assign } A[0] = V[0];$$

Obtained using K-map for A_1 and another Kmap for A_0 .

```
module circuitA_combinational (V, A);
```

```
input [3:0] V;
```

```
output [3:0] A; // by default outputs are wires
```

```
assign A[3] = 1'b0;
```

```
assign A[2] = V[2] & V[1];
```

```
assign A[1] = V[2] & (~V[1]);
```

```
assign A[0] = V[0];
```

```
endmodule
```