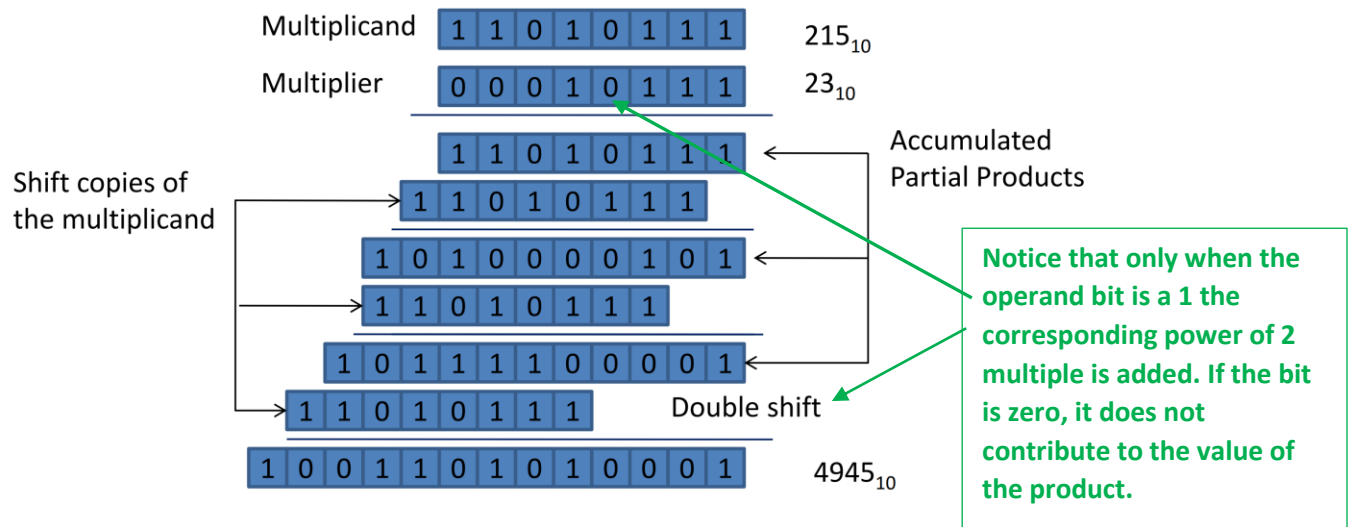



### Problem 3: (25 points)

Consider the following technique used for combinational binary multiplying. If you want to multiply 215 by 23, you can add ( $215 \cdot 2^0 + 215 \cdot 2^1 + 215 \cdot 2^2 + 215 \cdot 2^4 = 215 \cdot 1 + 215 \cdot 2 + 215 \cdot 4 + 215 \cdot 16 = 215(1+2+4+16) = 215(23)$  )

To get the power 2 multiples of the multiplicand, all what we need to do is to shift it to the left as many positions as the exponent or power value. This is an optimized method compared to adding the multiplicand 23 times!



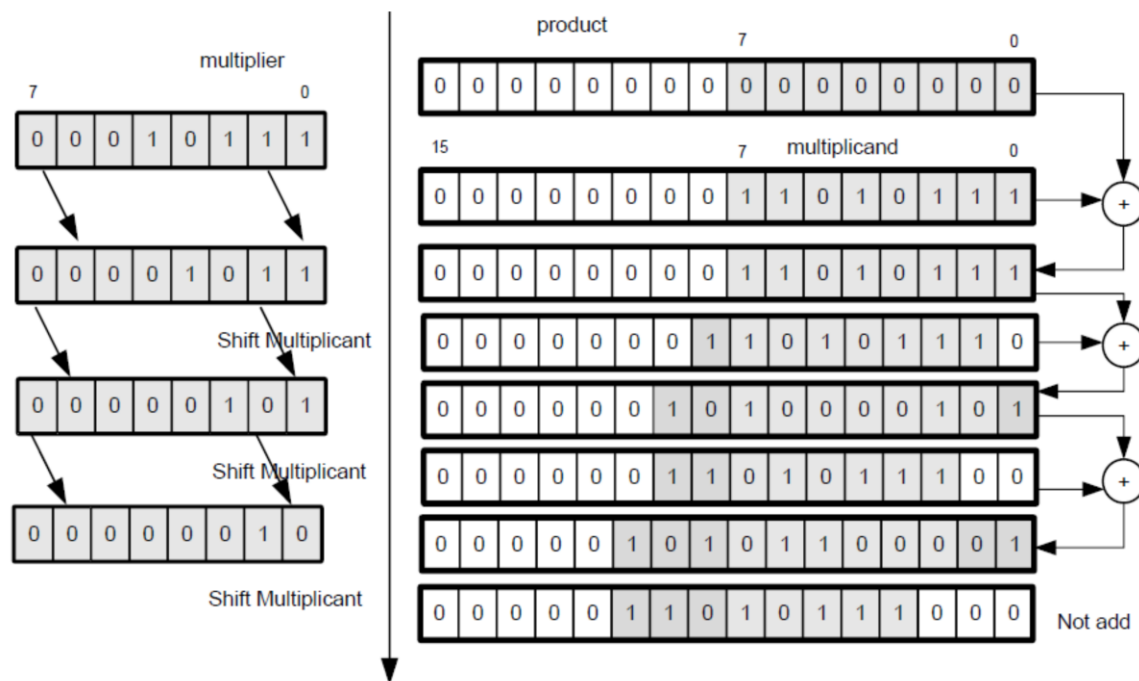The following is the datapath idea of operation:



```

module Datapath (product, final_product,
                multiplier_LSB, zero_flag,
                word1, word2,
                Load_words, Shift, Add, latch,
                clk, rst);

    parameter L_WORD= 4;

    output reg    [2*L_WORD-1: 0]    product, final_product;
    output        [ L_WORD-1: 0]     multiplier_LSB;
    input         [ L_WORD-1: 0]     word1, word2;
    input         Load_words, Shift, Add, latch;
    input         clk, rst;

    reg          [2*L_WORD-1: 0]     multiplicand;
    reg          [ L_WORD-1: 0]     multiplier;

    assign multiplier_LSB = multiplier[0];
    assign zero_flag     = (multiplier == 0);

    always @ (posedge clk)
        begin
            if (rst)                begin multiplier    <= 0;
                                     multiplicand    <= 0;
                                     product         <= 0;
                                     final_product    <= 0; end
            else if (Load_words) begin multiplicand    <= word1;
                                     multiplier       <= word2; |
                                     product         <= 0;
                                     final_product    <= 0; end
            else if (Shift)         begin multiplier    <= multiplier >> 1;
                                     multiplicand    <= multiplicand << 1; end
            else if (Add)           begin product      <= product+ multiplicand; end
            else if (latch)         begin final_product <= product; end
            end
endmodule

```

```

module Sequential_Multiplier (product, final_product,
                             Ready, start,
                             word1, word2,
                             clk, rst);

    parameter L_WORD= 4; // Datapathsize
    output    [2*L_WORD-1: 0] product, final_product;
    output    Ready;
    input     [L_WORD -1: 0] word1, word2;
    input     start, clk, rst;

    wire multiplier_LSB, Load_words, shift, Add, latch, zero_flag;

    Datapath M1 (product, final_product,
                multiplier_LSB, zero_flag,
                word1, word2,
                Load_words, shift, Add, latch,
                clk, rst);

    Controller M2 (Load_words, shift, Add, latch,
                  Ready, multiplier_LSB, start, zero_flag,
                  clk, rst);

endmodule

```

The module should raise a ready flag when it is ready to load new input words. The user should activate a start input to indicate that a new multiplication operation needs to be started. These are the initial statements for the controller code. Complete the code and include the FSM state graph and include a testbench to test the top module.

```

module Controller (Load_words, shift, Add, latch,
                  Ready, multiplier_LSB, start, zero_flag,
                  clk, rst);

output          reg    Load_words, shift, Add, latch;
input           multiplier_LSB, zero_flag;
input           start, clk, rst;
output          Ready;    // The multiplier is ready and the reset is not active

reg             ready;    // The multiplier is in the idle state

assign Ready = ready & (~rst);

parameter       S_idle      = 3'b000;
parameter       S_load     = 3'b001;
parameter       S_add      = 3'b010;
parameter       S_shift    = 3'b011;
parameter       S_latch    = 3'b100;
parameter       S_zeroCheck = 3'b101;

reg [2:0]       state, next_state;

always @ (posedge clk)
    if (rst) state <= S_idle;
    else    state <= next_state;


always @ *
begin
    Load_words = 1'b0;
    shift      = 1'b0;
    Add        = 1'b0;
    ready      = 1'b0;
    latch      = 1'b0;

    case (state)
        S_idle:      begin
                        ready = 1'b1;
                        if(start) next_state = S_load;
                        else      next_state = S_idle;    end
        S_load:      begin
                        Load_words = 1'b1; next_state = S_zeroCheck; end
        S_zeroCheck: begin
                        if (zero_flag)      next_state = S_latch;
                        else if (multiplier_LSB) next_state = S_add;
                        else                  next_state = S_shift;    end
        S_shift:     begin
                        shift = 1'b1;
                        next_state = S_zeroCheck;    end
        S_add:       begin
                        Add = 1'b1;
                        next_state = S_shift;        end
        S_latch:     begin
                        latch = 1'b1;
                        next_state = S_idle;          end
        default:     begin
                        next_state = S_idle;          end
    endcase
end

endmodule

```


(10 points)

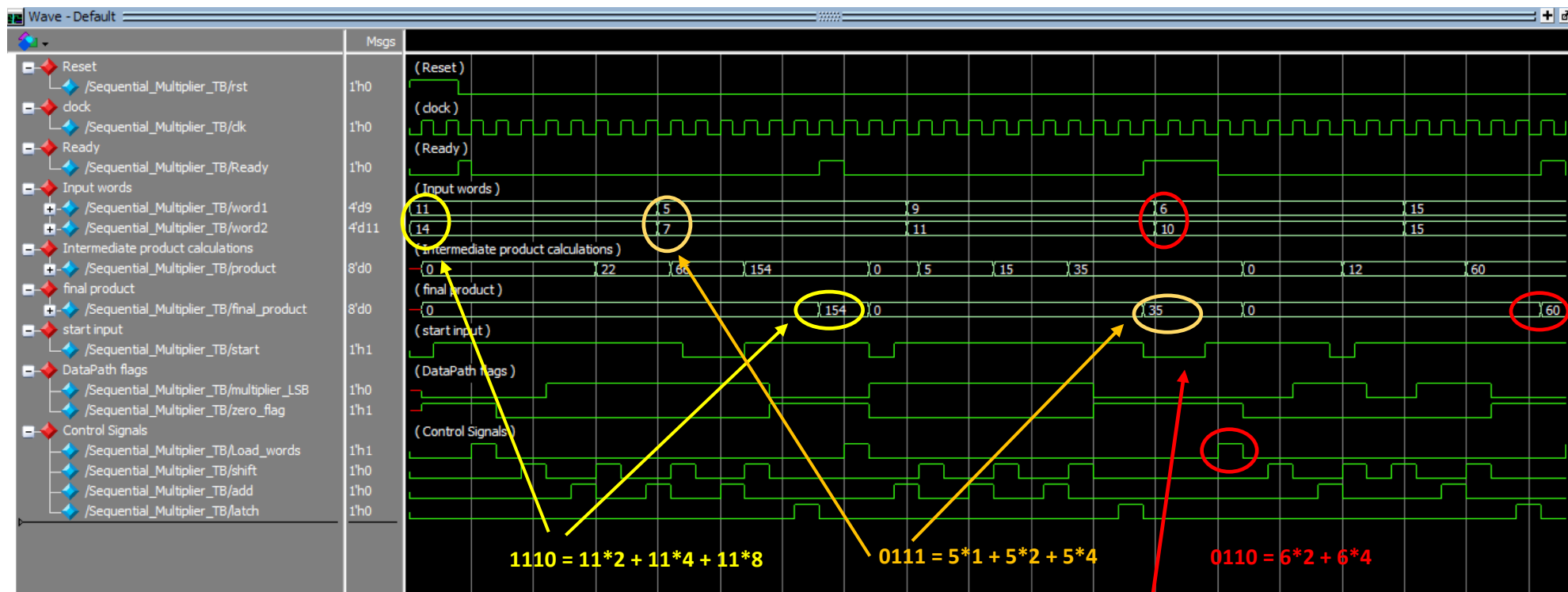

The latency for calculating the product is data dependent. Numbers with a smaller number of ones finish faster, and smaller numbers with higher bits equal to zero latch faster as well.

When the start is inactive the multiplier stays in the idle state. When the multiplier is ready and the start is activated, the word loading starts.

(5 points)

 

```

module Sequential_Multiplier_TB ();

parameter      L_WORD= 4;           // Datapathsize

wire           [2*L_WORD-1: 0]      product, final_product;
wire           Ready;
wire           multiplier_LSB, zero_flag;
wire           Load_words, shift, add, latch;
reg            [ L_WORD-1: 0]       word1, word2;
reg            start, clk, rst;

// instantiation of the unit under test:
Sequential_Multiplier UUT ( product, final_product,
                             Ready, start,
                             word1, word2, clk, rst);

assign multiplier_LSB = UUT.M1.multiplier_LSB;
assign zero_flag      = UUT.M1.zero_flag;
assign Load_words     = UUT.M2.Load_words;
assign shift          = UUT.M2.shift;
assign add             = UUT.M2.Add;
assign latch          = UUT.M2.latch;

initial
begin
  clk = 0;
  forever begin
    #10  clk = ~clk; end
end

initial
begin
  rst = 1;
  forever begin
    #40  rst = 0;
    #1200 rst = 1; end
end

initial
begin
  start = 0;
  forever begin
    #20  start = 1;
    #200 start = 0;
    #50  start = 1;
    #100 start = 0; end
end

initial
begin
  word1 = 11;  word2 = 14;
  forever begin
    #200 word1 = 5;   word2 = 7;
    #200 word1 = 9;   word2 = 11;
    #200 word1 = 6;   word2 = 10;
    #200 word1 = 15;  word2 = 15;
    #200 word1 = 14;  word2 = 15;
    #200 word1 = 12;  word2 = 13; end
end


endmodule

```


Probes to observe the internal control signals and verify the FSM operation.

(5 points)

Netlist Viewer

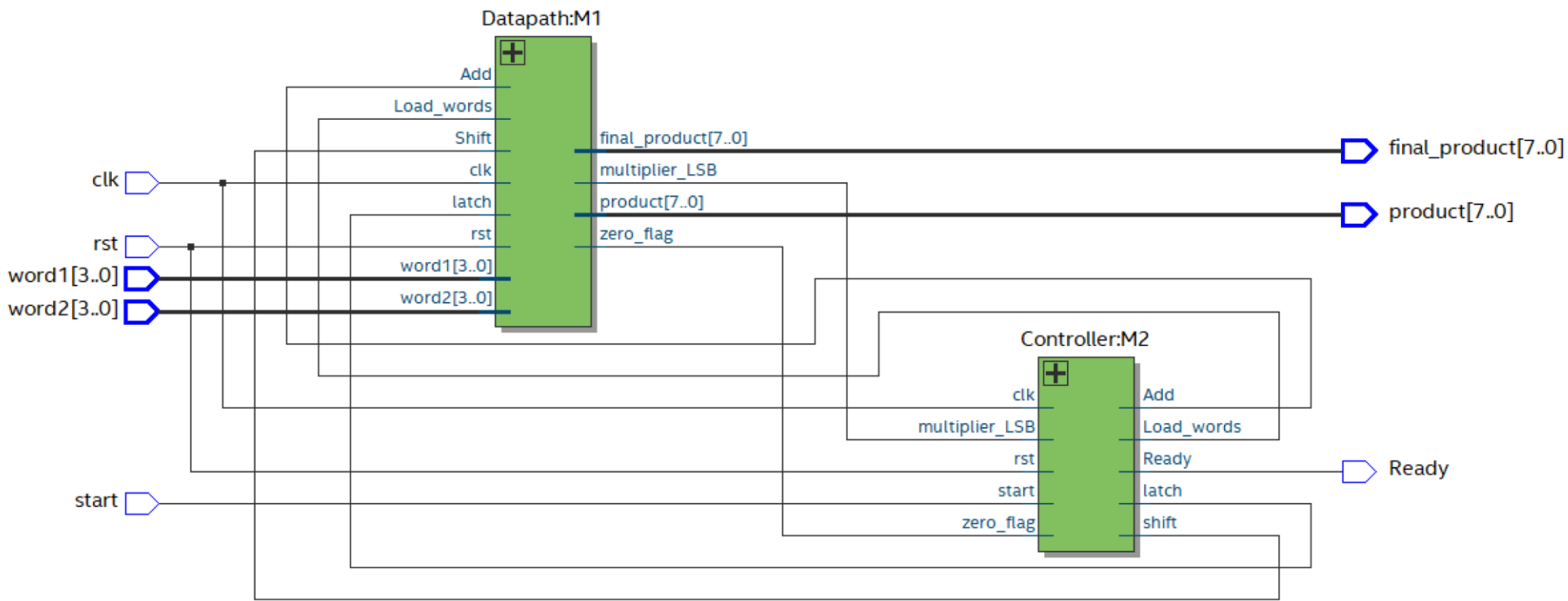

Finite State Machine State Graph

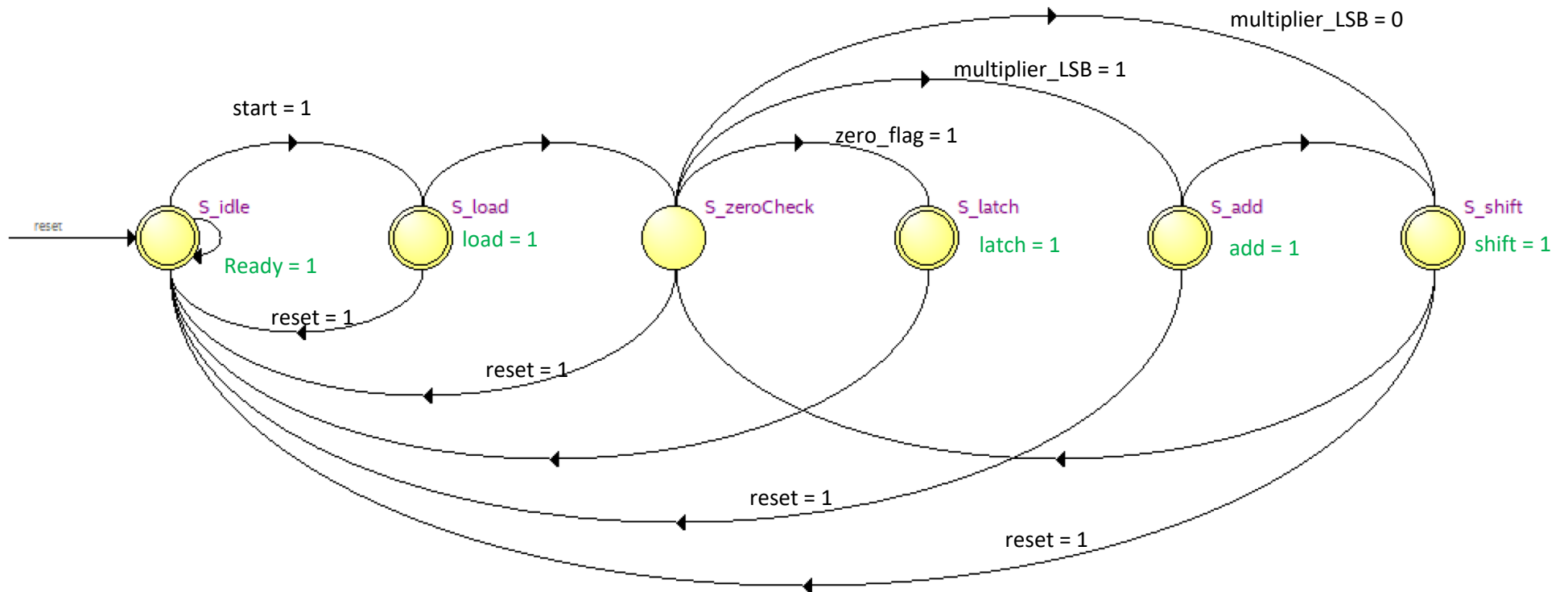

(5 points)