

```

1 //ee417 lesson 4 Assignment 3 Part 2, L4A3P2
2 // Name: Lamin Jammeh, Date: 06-09-24 Group: Kalin/Jammeh
3 //top module BCD_or_2421_up_down_counter
4 module BCD_or_2421_up_down_counter(output [3:0] count_out,
5                                     input clk,
6                                     input reset,
7                                     input enable,
8                                     input select_up_down,
9                                     input select_code2421_BCD );
10 //define internal wires
11 wire [3:0] downCount2421;
12 wire [3:0] upCount2421;
13 wire [3:0] count2421code;
14 wire [3:0] countBCD;
15 //instantiate submodules
16 code2421_downCounter DNCNT (downCount2421,clk,reset,enable);
17 code2421_upCounter UPCNT (upCount2421, downCount2421);
18 mux2to1_4bit MUX1 (downCount2421, upCount2421, select_up_down, count2421code);
19 weighted2421ToBCDConverter CONV (count2421code, countBCD);
20 mux2to1_4bit MUX2 (count2421code, countBCD, select_code2421_BCD, count_out);
21
22 endmodule
23 //-----BLOCK
24 A-----
25 //code2421_down_counter using Moore FSM with case structure
26 module code2421_downCounter (output reg [3:0] count,
27                               input clk,
28                               input reset,
29                               input enable);
30 //define the states
31 reg [3:0] state, next_state;
32
33 //define parameters
34
35 //sequential logic
36 always @(posedge clk or posedge reset)
37     if (reset)
38         state <= 4'b1111;
39     else if (enable) state<= next_state; //if reset high, reset, else..countdown
40
41     always @ * //any variable changes, combinational logic from given state table
42     case (state)
43         0: begin //state 0
44             next_state =1;
45             count=4'b1111;
46         end
47         1: begin //state 1
48             next_state =2;
49             count=4'b1110;
50         end
51         2: begin //state 2
52             next_state =3;
53             count=4'b1101;
54         end
55         3: begin //state 3
56             next_state =4;
57             count=4'b1100;
58         end
59         4: begin //state 4
60             next_state =5;
61             count=4'b1011;
62         end
63         5: begin //state 5
64             next_state =6;
65             count=4'b0100;
66         end
67         6: begin //state 6
68             next_state =7;


```

```

69         count=4'b0011;
70     end
71     7: begin //state 7
72         next_state =8;
73         count=4'b0010;
74     end
75     8: begin //state 8
76         next_state =9;
77         count=4'b0001;
78     end
79     9: begin //state 9
80         next_state =0;
81         count=4'b0000;
82     end
83     default: next_state <=0;
84             //count=4'b1111;
85 endcase
86 endmodule
87
88 /*-----
89 Project Description: This portion takes use the output of the code2421_downCounter
90 and inverts it to form an up counter. this is possible because of the complementary
91 characteristics of 2421 code
92 -----*/
93 //define the input as the output of the downCounter and the assign and output
94 // note the system is already initialize from the code2421_downCounter block
95 //define the output as wire since the upcount block is intermediate to enable assignment
96 //operation
97 module code2421_upCounter (output [3:0] upcount, input [3:0] count);
98 //wire [3:0] count;
99
100 //call the file for the code2421_downCounter
101 //code2421_downCounter UDM_downCount (.count(count),
102 //                                // .clk(clk),
103 //                                // .reset(reset),
104 //                                // .enable(enable));
105 //assign a function to the output of the upcounter
106 assign upcount = ~count;
107
108 endmodule
109
110 //4-bit wide 2 to 1 multiplexer
111 module mux2to1_4bit(
112     input [3:0] data0, // 4-bit input data 0
113     input [3:0] data1, // 4-bit input data 1
114     input select,      // select signal (0 or 1), z
115     output reg [3:0] muxout); //4-bit output
116     always @ (data0, data1) //put input only in sensitivity list
117         if (select) //select = 1
118             muxout = data1; //data1
119         else
120             muxout = data0; //data0
121 endmodule
122
123 // weighted 2421 to BCD Converter
124 module weighted2421ToBCDConverter (
125     input [3:0] weighted2421, // Input in weighted 2421 format
126     output reg [3:0] bcd ); // output in BCD format
127
128     always @ (weighted2421) //put input only in sensitivity list
129         case (weighted2421)
130             4'b0000: bcd = 4'b0000; // 0
131             4'b0001: bcd = 4'b0001; // 1
132             4'b0010: bcd = 4'b0010; // 2
133             4'b0011: bcd = 4'b0011; // 3
134             4'b0100: bcd = 4'b0100; // 4
135             4'b1011: bcd = 4'b0101; // 5
136             4'b1100: bcd = 4'b0110; // 6


```
 
```
137         4'b1101: bcd = 4'b0111; // 7
138         4'b1110: bcd = 4'b1000; // 8
139         4'b1111: bcd = 4'b1001; // 9
140         default: bcd = 4'b1111; // Default to unique value so invalid input code can be
        recognized
141     endcase
142 // Alternative description is given below
143 //assign bcd = (weighted2421 < 5) ? weighted2421 : weighted2421 - 6;
144 endmodule
145
```



```
1 //ee417 Lesson 4 Assignment 3 Part 2, L4A3P2
2 //Name: Lamin Jammeh, Date: 06-09-24, Group: Kalin/Jammeh
3 //Testbench for BCD_or_2421_up_down_counter using Moore FSM with case structure
4 //can select down or up counting for 2421code & also select (2421code or BCD) counting
5 //Step1 define test bench name
6 module BCD_or_2421_up_down_counter_tb();
7 /* original module declaration
8 module BCD_or_2421_up_down_counter(output [3:0] count_out,
9                                     input clk,
10                                    input reset,
11                                    input enable,
12                                    input select_up_down,
13                                    input select_code2421_BCD );*/
14 //Step2 define inputs as registers, outputs as wires
15 reg clk, rst,enable, select_up_down, select_code2421_BCD;
16 wire [3:0] count_out;
17 //internal probe wires: observe change in state..this gives Questa error if not enough
  digits
18 wire [3:0] downCount2421;
19 wire [3:0] upCount2421;
20 wire [3:0] count2421code;
21 wire [3:0] countBCD;
22 //wire [2:0] state, next_state;
23
24 //Step3 define unit under test
25 BCD_or_2421_up_down_counter UUT (count_out,clk,rst,enable,select_up_down,
26                                   select_code2421_BCD);
27
28 //internal probes to track logic and troubleshoot
29 assign downCount2421= UUT.downCount2421;
30 assign upCount2421= UUT.upCount2421;
31 assign count2421code= UUT.count2421code;
32 assign countBCD= UUT.countBCD;
33 //assign next_state= UUT.next_state;
34
35 //Step4 open initial block, define all possible input combinations
36 // Clock generation (adjust the period as needed)
37 initial begin
38     clk=0;
39     forever
40         #5 clk = ~clk;
41 end
42
43 initial //reset is active high, longer time to count when reset is inactive (low)
44 begin //4 cases with two selects
45     rst = 1'b1; //reset on
46     # 10 rst = 1'b0; enable=1'b1; select_up_down=1'b0; select_code2421_BCD=1'b0;
47     //reset off, enable on, select down, select 2421
48     #120 rst = 1'b1; //reset on
49     # 20 rst = 1'b0; enable=1'b1; //reset off, enable on
50     # 60 enable=1'b0; //enable off: freeze count
51
52     # 10 rst = 1'b0; enable=1'b1; select_up_down=1'b0; select_code2421_BCD=1'b1;
53     //reset off, enable on, select down, select BCD
54     #120 rst = 1'b1; //reset on
55     # 20 rst = 1'b0; enable=1'b1; //reset off, enable on
56     # 60 enable=1'b0; //enable off: freeze count
57
58     # 10 rst = 1'b0; enable=1'b1; select_up_down=1'b1; select_code2421_BCD=1'b0;
59     //reset off, enable on, select up, select 2421
60     #120 rst = 1'b1; //reset on
61     # 20 rst = 1'b0; enable=1'b1; //reset off, enable on
62     # 60 enable=1'b0; //enable off: freeze count
63
64     # 10 rst = 1'b0; enable=1'b1; select_up_down=1'b1; select_code2421_BCD=1'b1;
65     //reset off, enable on, select up, select BCD
66     #120 rst = 1'b1; //reset on
67     # 20 rst = 1'b0; enable=1'b1; //reset off, enable on
68     # 60 enable=1'b0; //enable off: freeze count
```

```
69
70     #100 $stop; //close debug window to view waveform viewer
71 end
72
73 //Step5 Display the results
74 initial begin //monitor counter value
75     $display("_____output_count_out = -count-");
76     $monitor("clk_in = %b: rst_in = %b: enable_in=%b: select_up_down=%b:
select_code2421_BCD=%b: output_count_out = %d ";
77     clk, rst, enable, select_up_down, select_code2421_BCD, count_out);
78 end
79 endmodule
80
```

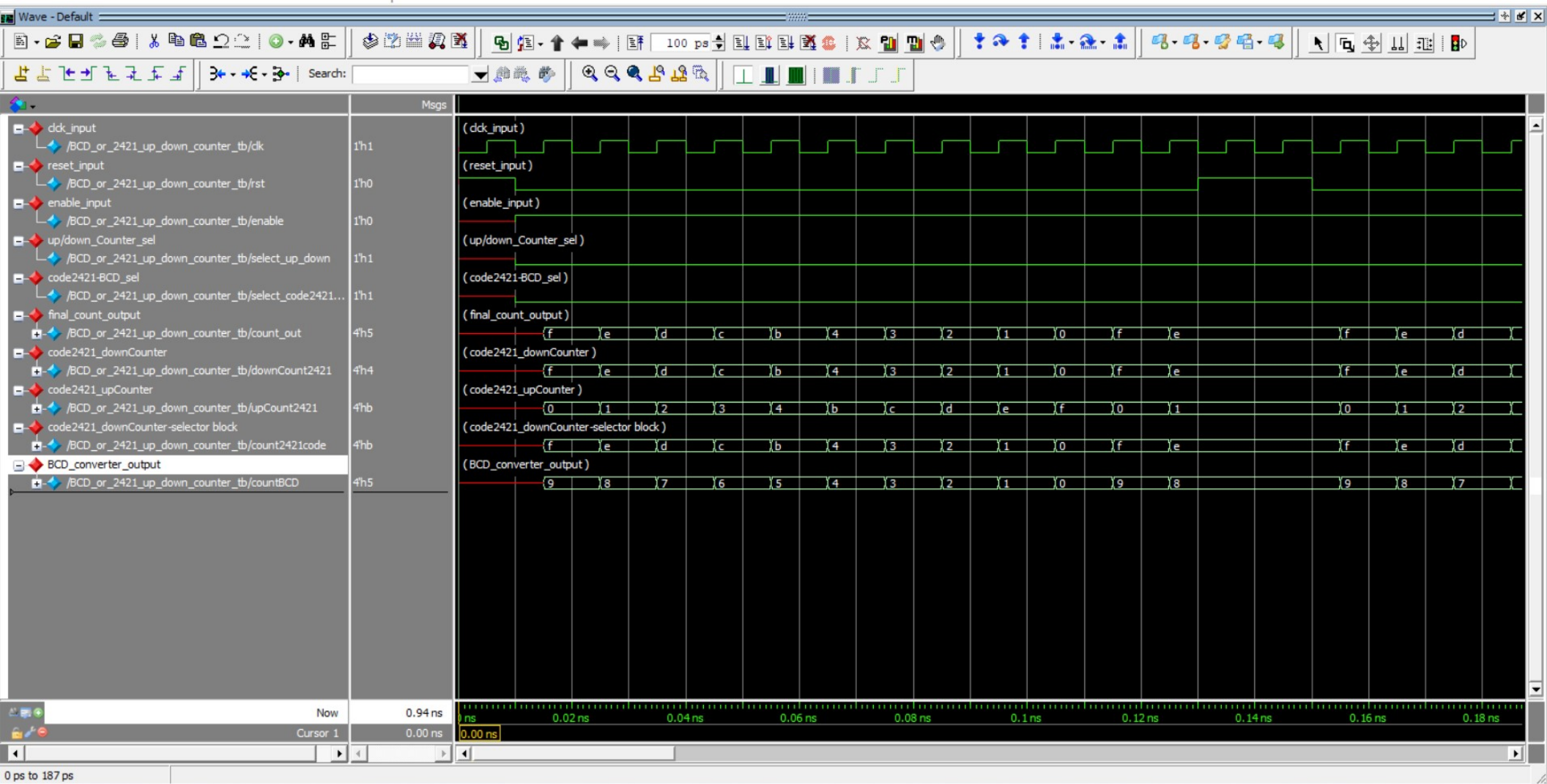

Part of the Simulation transcript

```
#                                     output_count_out = -count-
# clk_in = 0: rst_in = 1: enable_in=x: select_up_down=x: select_code2421_BCD=x: output_count_out = x
# clk_in = 1: rst_in = 1: enable_in=x: select_up_down=x: select_code2421_BCD=x: output_count_out = x
# clk_in = 0: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = x
# clk_in = 1: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 15
# clk_in = 0: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 15
# clk_in = 1: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 14
# clk_in = 0: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 14
# clk_in = 1: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 13
# clk_in = 0: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 13
# clk_in = 1: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 12
# clk_in = 0: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 12
# clk_in = 1: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 11
# clk_in = 0: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 11
# clk_in = 1: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 4
# clk_in = 0: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 4
# clk_in = 1: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 3
# clk_in = 0: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 3
# clk_in = 1: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 2
# clk_in = 0: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 2
# clk_in = 1: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 1
# clk_in = 0: rst_in = 0: enable_in=1: select_up_down=0: select_code2421_BCD=0: output_count_out = 1
# ** Note: $stop      : C:/Users/lmnjm/OneDrive/Documents/Summer 2024/EE417 Programmable Logic Devices/Lecture 04/Quartu
# Time: 940 ps Iteration: 0 Instance: /BCD_or_2421_up_down_counter_tb
# Break in Module BCD_or_2421_up_down_counter_tb at C:/Users/lmnjm/OneDrive/Documents/Summer 2024/EE417 Programmable L
```

The simulation summary shows the following

- The system takes in a code2421 and counts it down in the first block
- In the second block the output sends to code2421 upCounter and a selector block
- Block three is the selector block 1 it takes input from the downCounter and the upCounter
 - It uses a select bit to determine which input to output
- The third block is a code2421 to BCD converter
 - Takes input from the selector or third block and outputs BCD
- The final block is another selector block
 - Takes input from the first selector block and code2421 to BCD converter block
 - Outputs either a BCD code or code2421 depending on a select bit