

# FIR Filter Design

PROJECT 1 CE6325 VLSI DESIGN: VERILOG HDL

LAMIN JAMMEH      NET-ID: DAL852207

## Project Description:

A Finite Impulse Response (FIR) filter was designed with pre-determined specifications. The filter order, and the Data\_in size were parameterized to allow the design to be scalable. The filter takes in a sample input, processes the sample input and passes it to an output register

## Design Specifications

Filter order: 5

Filter coefficients: [7, 8, 9, 12, 4]

Data\_in size: 4

Data\_out size: 16

## Data flow of the design

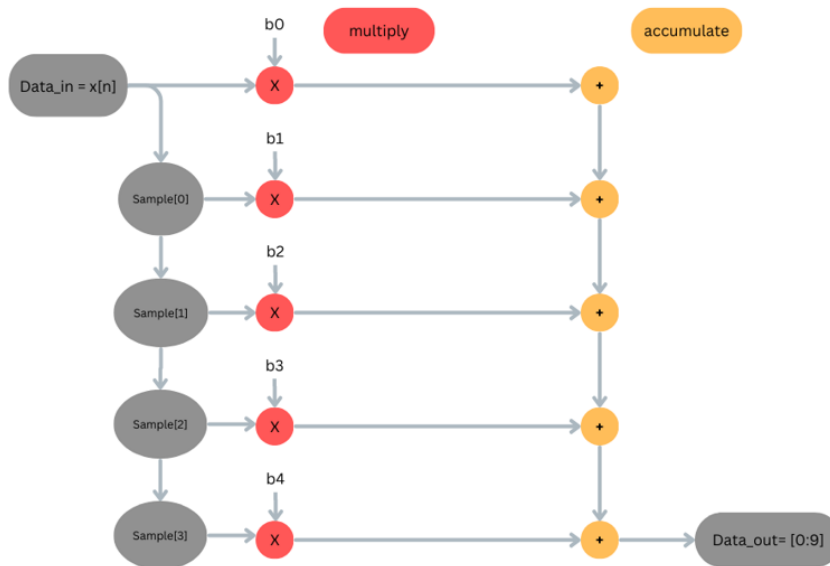


Figure1: Finite Impulse Response (FIR) Filter using Multiply and Accumulate

Design Netlist

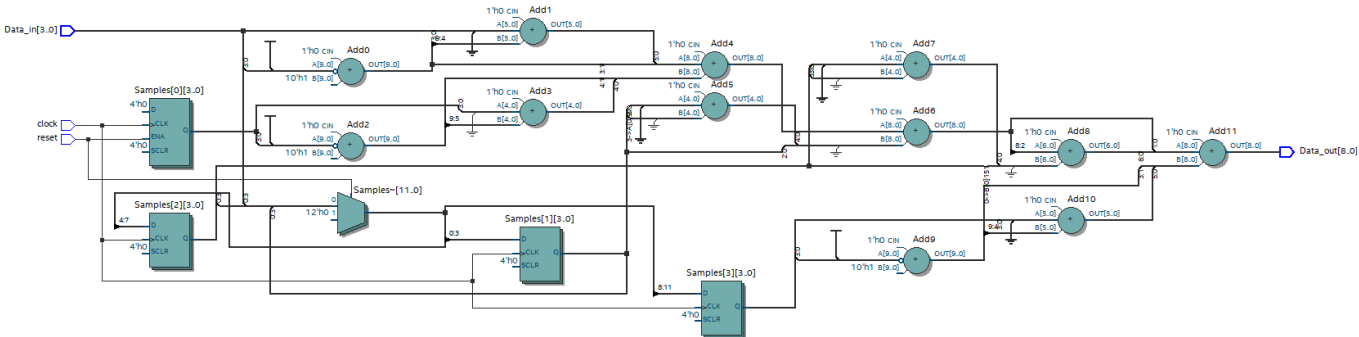


Figure 2: Netlist for the FIR filter

Testbench Process Flow

 


Figure 3: Shows the Testbench Process flow

Table 1 showing Filter out with when Data\_in = decimal (6)

Data_in		Sample[k]	Filter Coefficient (bn)		bn * Sample[k]		Acc @ filter stage
6	Data_in →	6	7	bn * Sample[k] →	42	acc0	42
		6	8		48	acc1	90
		6	9		54	acc2	144
		6	12		72	acc3	216
		6	4		24	Data_out/acc4	240

Table 1 shows that Data\_in will go shift through all of Sample[k] when enough time is allowed before changing the value at the input. The value in each register of Sample[k] is multiplied by the filter

coefficient ( $b_n$ ). The values of the multiply is accumulated or summed to form the output of the filter.

$$Mux = b_n * Sample[k]$$

$$acc = \sum_n^0 Mux_n$$

## Register Transistor Logic (RTL) Simulation Result


Table3 shows the observed values from the simulation results

```
# run -all
# Time: 0 | Data_in: 0 | Data_out: x | reset: 1
# Time: 5 | Data_in: 0 | Data_out: 0 | reset: 1
# Time: 10 | Data_in: 0 | Data_out: 0 | reset: 0
# Time: 110 | Data_in: 6 | Data_out: 0 | reset: 0
# Time: 115 | Data_in: 6 | Data_out: 42 | reset: 0
# Time: 125 | Data_in: 6 | Data_out: 90 | reset: 0
# Time: 135 | Data_in: 6 | Data_out: 144 | reset: 0
# Time: 145 | Data_in: 6 | Data_out: 216 | reset: 0
# Time: 155 | Data_in: 6 | Data_out: 240 | reset: 0
# Time: 210 | Data_in: 3 | Data_out: 240 | reset: 0
# Time: 215 | Data_in: 3 | Data_out: 219 | reset: 0
# Time: 225 | Data_in: 3 | Data_out: 195 | reset: 0
# Time: 235 | Data_in: 3 | Data_out: 168 | reset: 0
# Time: 245 | Data_in: 3 | Data_out: 132 | reset: 0
# Time: 255 | Data_in: 3 | Data_out: 120 | reset: 0
# Time: 310 | Data_in: 2 | Data_out: 120 | reset: 0
# Time: 315 | Data_in: 2 | Data_out: 113 | reset: 0
# Time: 325 | Data_in: 2 | Data_out: 105 | reset: 0
# Time: 335 | Data_in: 2 | Data_out: 96 | reset: 0
# Time: 345 | Data_in: 2 | Data_out: 84 | reset: 0
# Time: 355 | Data_in: 2 | Data_out: 80 | reset: 0
# Time: 410 | Data_in: 5 | Data_out: 80 | reset: 0
# Time: 415 | Data_in: 5 | Data_out: 101 | reset: 0
# Time: 420 | Data_in: 5 | Data_out: 101 | reset: 1
# Time: 425 | Data_in: 5 | Data_out: 0 | reset: 1
# Time: 430 | Data_in: 5 | Data_out: 0 | reset: 0
# Time: 435 | Data_in: 5 | Data_out: 35 | reset: 0
# Time: 445 | Data_in: 5 | Data_out: 75 | reset: 0
# Time: 455 | Data_in: 5 | Data_out: 120 | reset: 0
# Time: 465 | Data_in: 5 | Data_out: 180 | reset: 0
# Time: 475 | Data_in: 5 | Data_out: 200 | reset: 0
# Time: 530 | Data_in: 2 | Data_out: 200 | reset: 0
# Time: 535 | Data_in: 2 | Data_out: 179 | reset: 0
# Time: 545 | Data_in: 2 | Data_out: 155 | reset: 0
# Time: 555 | Data_in: 2 | Data_out: 128 | reset: 0
# Time: 565 | Data_in: 2 | Data_out: 92 | reset: 0
# Time: 575 | Data_in: 2 | Data_out: 80 | reset: 0
# Time: 630 | Data_in: 0 | Data_out: 80 | reset: 0
# Time: 635 | Data_in: 0 | Data_out: 66 | reset: 0
# Time: 645 | Data_in: 0 | Data_out: 50 | reset: 0
# Time: 655 | Data_in: 0 | Data_out: 32 | reset: 0
# Time: 665 | Data_in: 0 | Data_out: 8 | reset: 0
# Time: 675 | Data_in: 0 | Data_out: 0 | reset: 0
# Time: 730 | Data_in: 2 | Data_out: 0 | reset: 0
# Time: 735 | Data_in: 2 | Data_out: 14 | reset: 0
# Time: 745 | Data_in: 2 | Data_out: 30 | reset: 0
# Time: 755 | Data_in: 2 | Data_out: 48 | reset: 0
# Time: 765 | Data_in: 2 | Data_out: 72 | reset: 0
# Time: 775 | Data_in: 2 | Data_out: 80 | reset: 0
# Time: 830 | Data_in: 4 | Data_out: 80 | reset: 0
# Time: 835 | Data_in: 4 | Data_out: 94 | reset: 0
# Time: 845 | Data_in: 4 | Data_out: 110 | reset: 0
# Time: 855 | Data_in: 4 | Data_out: 128 | reset: 0
# Time: 865 | Data_in: 4 | Data_out: 152 | reset: 0
# Time: 875 | Data_in: 4 | Data_out: 160 | reset: 0
# ** Note: $stop : C:/Users/lmnm/OneDrive/Documents/Grad School/UTD/Fall 2024/EEDG 6325/Projects/Project 1/FIR_Filter_Project1_tb.v(66)
# Time: 930 ps Iteration: 0 Instance: /FIR_Filter_Project1_tb
```

When Data\_in =6 Data\_out=240 @ next rising clock after Data\_in goes through all the filter taps or stages

@ reset = 1 Data\_out = 0 since the Sample register is cleared @reset high. This happens @ next rising clock

Simulation Wave form

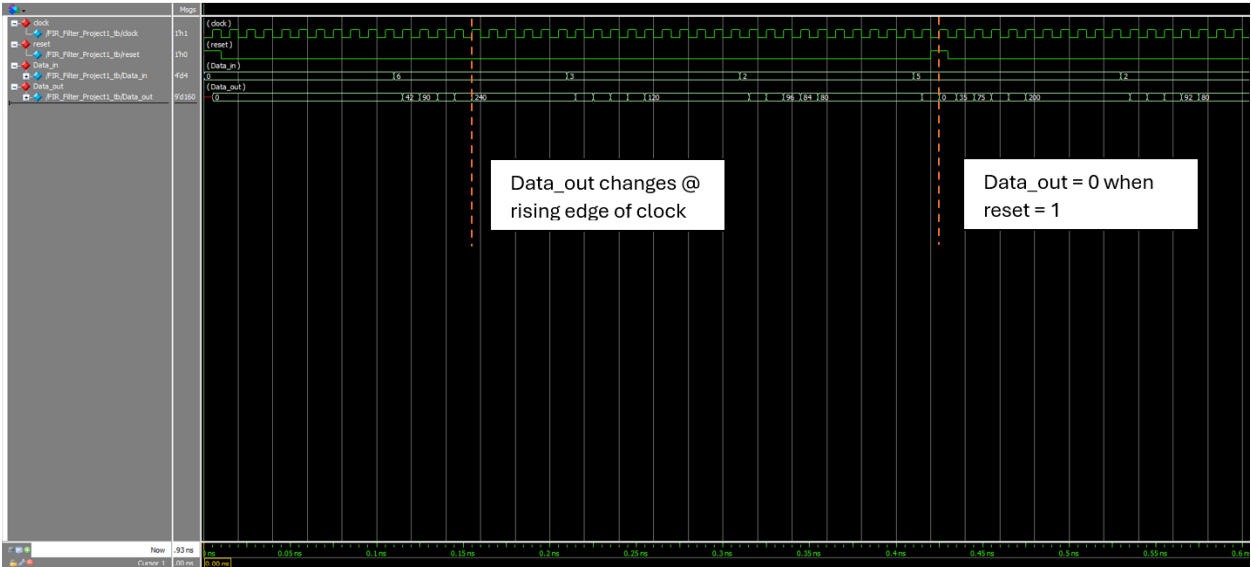

```

1  /*-----
2  Name:    Lamin Jammeh
3  Class:   CE6325 Fall_2024
4  Project: 1
5  Project Description: this is a Finite Impulse Response (FIR) filter design using Verilog HDL
6  The design follows the concepts below
7  **The filter order is selected and parameterized so the design can be scaled in the future
8  **The filter coefficients are pre-determined
9  **Data_in samples will be provided in the testbench to determine the filter behavior
10 **The Data_in sample is Multiplied and accumulated through the different filter stages/taps
11 **The Data_out word_size = word_in + coeff_size + [log2[N]] where N= # of taps in the filter
12
13 -----*/
14 module FIR_Filter_Project1 #(parameter order = 5,                      //filter
15 order [pre-determined]
16                               parameter word_size_in = 4,              //size of
17 data_in [pre-determined]
18                               parameter word_size_out = 16) //word_size = word_in +
19                               coeff_size + [log2[N]] N=4, & coeff=word_in
20
21 //declare inputs and outputs
22 (
23   output [word_size_out - 1:0] Data_out,
24   input  [word_size_in - 1:0]  Data_in,
25   input  clock, reset
26 );
27
28 reg [word_size_in - 1:0] Samples[order-1:0]; //temp storage for input samples
29 (x(n))
30 reg [word_size_out - 1:0] acc; //temp storage for output data
31 integer k;
32
33 //Filter Coefficients
34 parameter b0 = 4'd7;
35 parameter b1 = 4'd8;
36 parameter b2 = 4'd9;
37 parameter b3 = 4'd12;
38 parameter b4 = 4'd4;
39
40 //define the formula for the output
41 assign Data_out = acc;
42
43 always @(posedge clock)
44 begin
45   if (reset == 1)
46     //when reset is high and clock is rising samples[k] = 0 regardless of k value
47     begin
48       for (k = 0; k < order; k = k+1)
49         begin
50           Samples[k] <= 0;
51           acc <= 0;
52         end
53     end
54   else
55     //when reset is low and clock is rising compute Samples with data_in to get Data_out
56     begin
57       Samples[0] <= Data_in; //@ k=0 Samples[0] <= Data_in
58       for (k = 1; k < order; k = k + 1) // from k=1 to k=order Samples[k]
59         <=Samples[k-1]
60         begin
61           Samples[k] <= Samples[k - 1]; //Data_in will go through all the
62           filter coefficients
63           acc <= b0*Data_in
64             + b1*Samples[0]
65             + b2*Samples[1]
66             + b3*Samples[2]
67             + b4*Samples[3];
68         end
69     end
70 end

```

```
64     end
65 endmodule
```

```

1  /*-----
2  Name:    Lamin Jammeh
3  Class:   CE6325 Fall_2024
4  Project: 1
5  Project Description: Teestbench for Project1
6  **create a clock signal
7  **Initialize all the input signals
8  **apply some Sample Data_in as [6325] in 10 time unit intervals
9  **apply reset to test the reset signal
10 **apply anothe set of sample Data_in as [2024] in 10 time unit intervals
11 **monitor the signals and end the test
12
13 -----*/
14
15 module FIR_Filter_Project1_tb;
16
17 parameter order = 4;
18 parameter word_size_in = 4;
19 parameter word_size_out = 2 * word_size_in + 1;
20
21 //declare ports for the design
22 wire [word_size_out-1:0] Data_out;
23 reg [word_size_in-1:0] Data_in;
24 reg clock, reset;
25
26 //declare the unit under test UUT
27 FIR_Filter_Project1 #(order, word_size_in, word_size_out) UUT(.Data_out(Data_out),
28                                                                .Data_in(Data_in),
29                                                                .clock(clock),
30                                                                .reset(reset)
31                                                                );
32
33 // Instantiate the clock signal
34 initial
35 begin
36     clock = 0;
37     forever #5 clock = ~clock;
38 end
39
40 //Instantiate the diiferent test scenarios to validate the design
41 //*****Scenario 1 initialize all input signals
42 initial
43 begin
44     reset = 1;
45     Data_in = 0;
46
47     #10 reset = 0; //wait for 10 timing units for the inital signals to go through
48
49 //Scenario 2 apply some Data_in samples and observe the outputs use [6 3 2 5] @ 100 time
unit intervals
50     #100 Data_in = 4'd6; //make sure time is long enough for Data_in to mkae it
to the last filter Coefficient
51     #100 Data_in = 4'd3;
52     #100 Data_in = 4'd2;
53     #100 Data_in = 4'd5;
54
55 //Scenario 3 test the reset signal to validate the behavior
56     #10 reset = 1; //Sample registers should be cleared
57     #10 reset = 0; //Sample register will accept Data_in
58
59 //Scenario 4 apple more samples to make sure the design works after reset
60     #100 Data_in = 4'd2;
61     #100 Data_in = 4'd0;
62     #100 Data_in = 4'd2;
63     #100 Data_in = 4'd4;
64
65 //stop the test
66     #100 $stop;
67 end

```



```
68
69 // Monitor output
70 initial
71     begin
72         $monitor("Time: %4t\t | Data_in: %0d\t | Data_out: %3d\t | reset: %b," $time,
73             Data_in, Data_out, reset); //use %10 as padding for time and data_out
74     end
75 endmodule
76
77
78
```