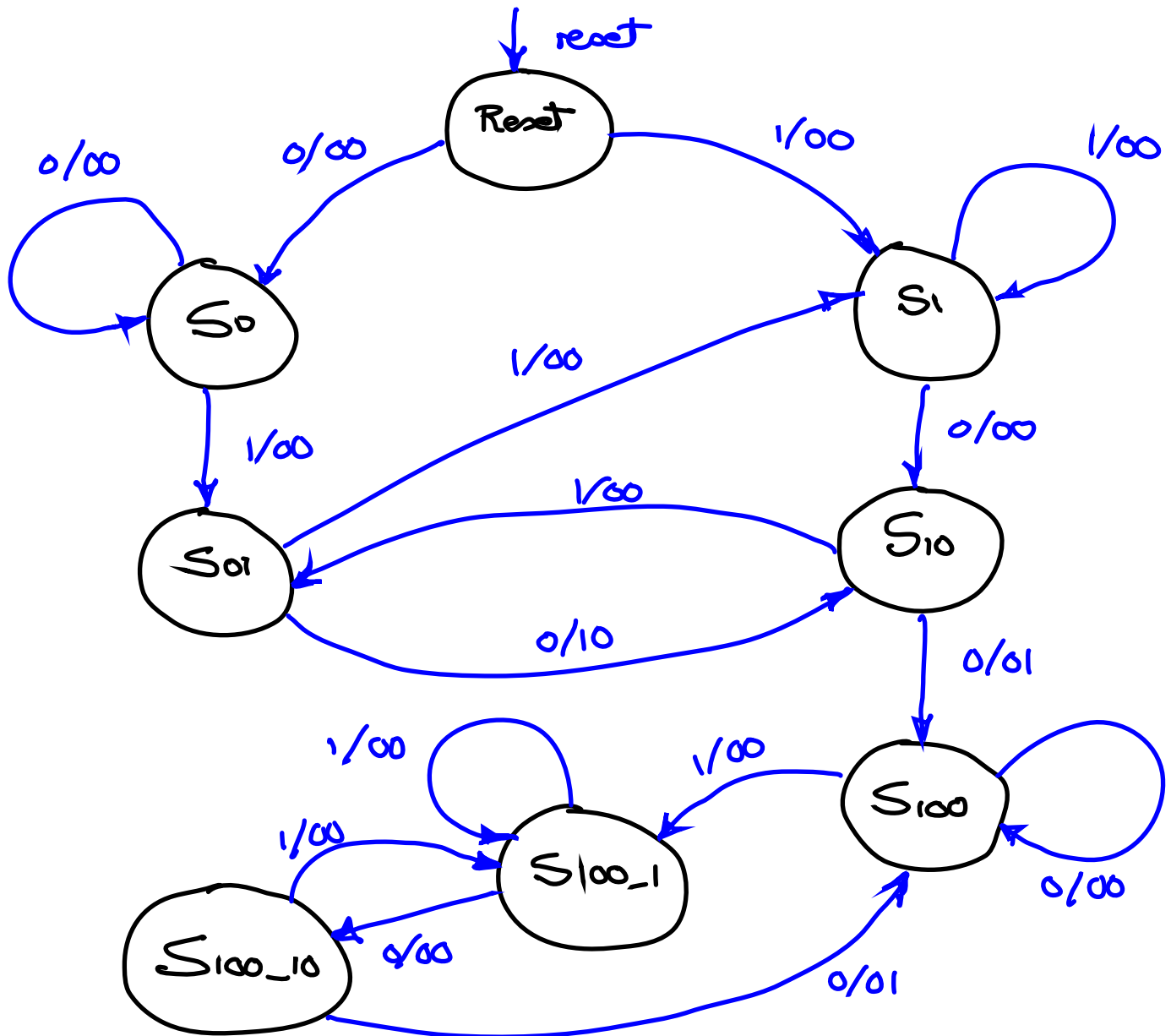


EE 417 – Assignment 3 – Problem 1 – Sequence detector with two outputs

A sequential circuit has one input (X) and two outputs (z1 and z2). An output $z1 = 1$ occurs every time the input sequence 010 is completed, provided that the sequence 100 has never occurred.

An output $z2 = 1$ occurs every time the input 100 is completed. Note that once a $z2 = 1$ output has occurred, $z1 = 1$ can never occur but not vice versa. Find a Mealy state graph and state table (minimum number of states is eight).

Sketch the state graph, and then create the Verilog code and verify the functionality of the FSM. Use a reset input to initialize the FSM state at the reset state.



```

/* -----
A sequential circuit has one input (x) and two outputs (z1 and z2).
An output Z1 = 1 occurs every time the input sequence 010 is completed,
provided that the sequence 100 has never occurred.
An output Z2 = 1 occurs every time the input 100 is completed.
Note that once a Z2 = 1 output has occurred, Z1 = 1 can never occur
but not vice versa.
Find a Mealy state graph and state table (minimum number of states is eight).

Sketch the state graph, and then create the Verilog code and verify the functionality
of the FSM. Use a reset input to initialize the FSM state at the reset state.
-----*/

```

```

module SequenceDetector (clk, reset, x, z1_o, z2_o);

input      clk, reset, x;
output reg z1_o, z2_o;

reg [2:0] state, next_state;
reg       z1, z2;

parameter SRst    = 3'b111; // Rst state - no inputs received // 7

//----- 100 was never detected
parameter S0      = 3'b000; // A 0 was received // 0
parameter S1      = 3'b001; // A 1 was received // 1
parameter S01     = 3'b011; // Sequence 01 was received // 3
parameter S10     = 3'b010; // Sequence 10 was received // 2

//----- 100 was received
parameter S100    = 3'b100; // sequence 100 received // 4
parameter S100_1  = 3'b101; // Received 1 after z2 was 1 // 5
parameter S100_10 = 3'b110; // sequence 10 after z2 was 1 // 6

// assign z1_o = z1;
// assign z2_o = z2;

always @ (posedge clk)
if (reset) begin
    state <= SRst;
    z1_o <= 1'b0;
    z2_o <= 1'b0; end
else begin
    state <= next_state;
    z1_o <= z1;
    z2_o <= z2; end

always @ *
case (state)
    SRst : begin z1 = 1'b0; z2 = 1'b0;
              if (x) next_state = S1;
              else next_state = S0; end
    S0   : begin z1 = 1'b0; z2 = 1'b0;
              if (x) next_state = S01;
              else next_state = S0; end
    S1   : begin z1 = 1'b0; z2 = 1'b0;
              if (x) next_state = S1;
              else next_state = S10; end
    S01  : if (x) begin next_state = S1;
                  z1 = 1'b0; z2 = 1'b0; end
              else begin next_state = S10;
                  z1 = 1'b1; z2 = 1'b0; end
    S10  : if (x) begin next_state = S01;
                  z1 = 1'b0; z2 = 1'b0; end
              else begin next_state = S100;
                  z1 = 1'b0; z2 = 1'b1; end
    S100 : begin z1 = 1'b0; z2 = 1'b0;
              if (x) next_state = S100_1;
              else next_state = S100; end
    S100_1 : begin z1 = 1'b0; z2 = 1'b0;
              if (x) next_state = S100_1;
              else next_state = S100_10; end
    S100_10 : if (x) begin next_state = S100_1;
                  z1 = 1'b0; z2 = 1'b0; end
              else begin next_state = S100;
                  z1 = 1'b0; z2 = 1'b1; end
    default: begin z1 = 1'b0; z2 = 1'b0;
                  next_state = SRst; end
endcase
endmodule

```

```

module SequenceDetector_tb ();

wire  z1_o, z2_o;
reg    clk, reset, x;

wire  z1, z2;
wire  [2:0] state, next_state;

SequenceDetector UUT (.clk    (clk),
                      .reset  (reset),
                      .x      (x),
                      .z1_o   (z1_o),
                      .z2_o   (z2_o) );

assign state      = UUT.state;
assign next_state = UUT.next_state;
assign z1         = UUT.z1;
assign z2         = UUT.z2;


initial
begin
  clk = 1'b0;
  forever
  #5   clk = ~clk;
end

initial
begin
  reset = 1'b1;
  #20   reset = 1'b0;
  #200  reset = 1'b1;
  #20   reset = 1'b0;
end

initial
begin
  x = 1'b0;
  repeat (4) // repeats the code how many times it is assigned
  begin
    #10 x = 1'b1;
    #10 x = 1'b0; end
    #10
    x = 1'b0;    #50 // testing a long string of 0s
    x = 1'b1;    #50 // testing a long string of 1s
    x = 1'b0;    #20 // two 0s following a 1 - 100 sequence
  repeat (4) // repeats the sequence 010 but after 100 was received    z2 = 1
  begin // z1 is not expected to rise to 1 again
    #10 x = 1'b1;
    #10 x = 1'b0; end
  repeat (4) // repeated sequence 100
  begin
    #10 x = 1'b1;
    #10 x = 1'b0;
    #10 x = 1'b0; end
  end
end
endmodule

```

 
Correct value of z1 following a 010 sequence at the input, but z1 will not remain high for a full clock cycle, as x changed within the clock cycle. The registered output was able to hold the correct z1 value for the full clock cycle.




The next_state combinational logic updates with every change in state and x. The state is only updated at the positive clock edge.

Next_state is glitchy because of misalignment of x transitions with the clock positive edge. The registered state follows the state graph based on the sampled x at the posedge clk.

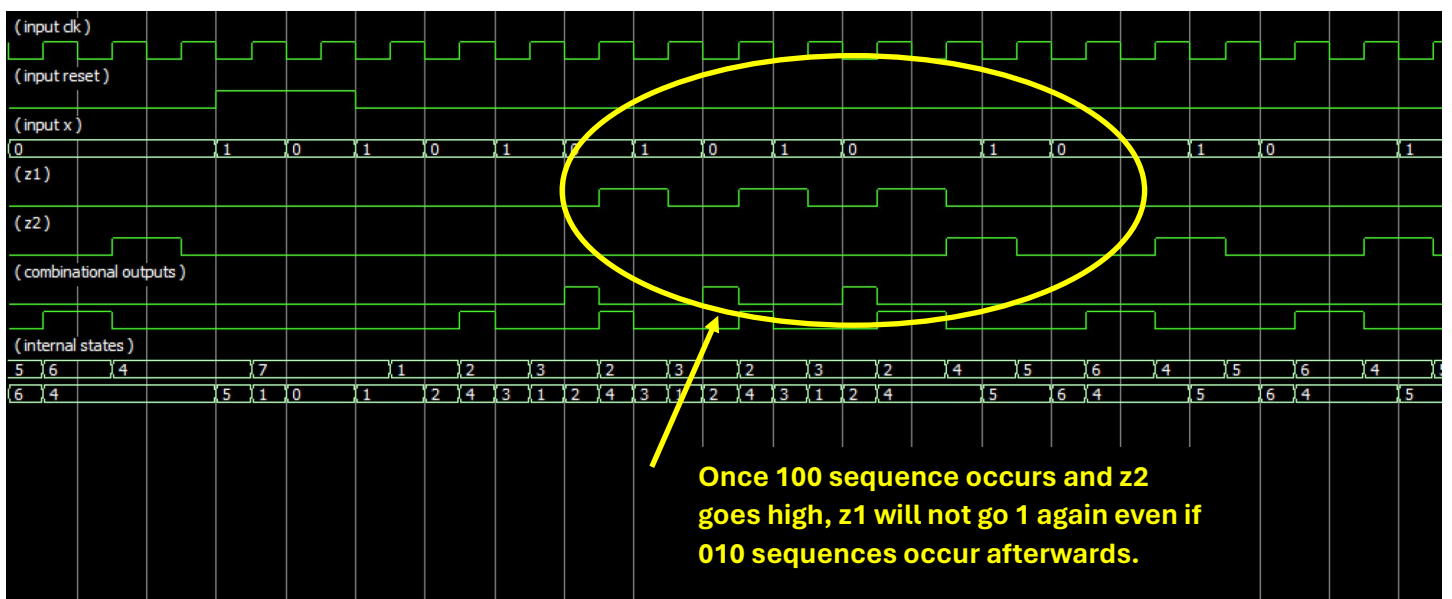A glitch showing wrong value for z1 mistakenly assuming 100 was received because of the misalignment of x with the change of the state at the positive clock edge. Z2 should remain 0, and this is what we get with the registered output z2_o.




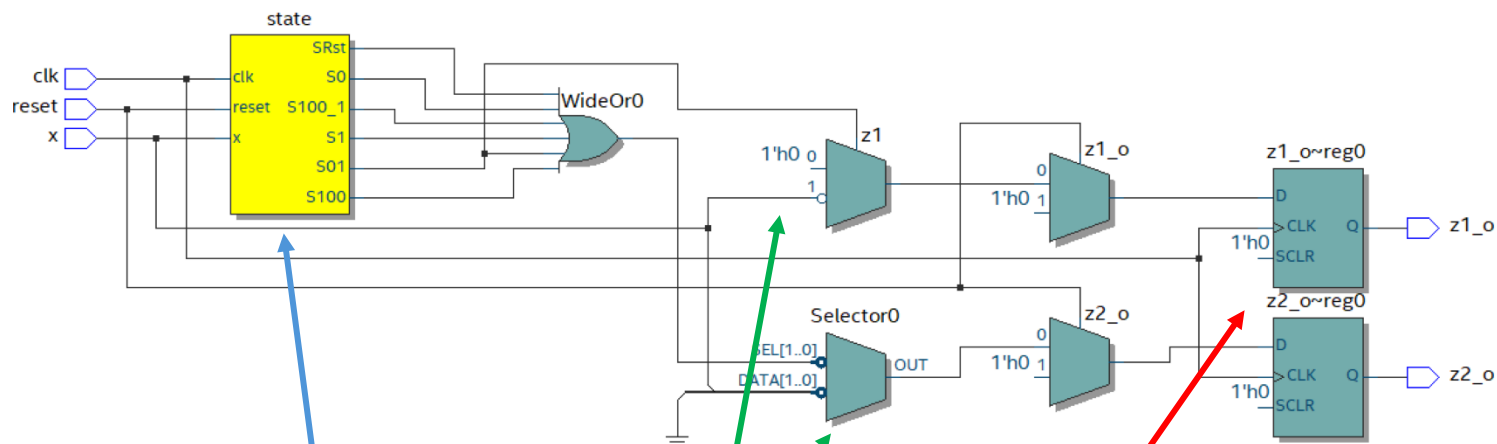

The FF for the state update

Combinational logic (MUX) finding the z1 and z2 internal values

The FF for the outputs z1 and z2

 

	Source State	Destination State	Condition
1	S0	SRst	(reset)
2	S0	S01	(x).(!reset)
3	S0	S0	(!x).(!reset)
4	S1	SRst	(reset)
5	S1	S10	(!x).(!reset)
6	S1	S1	(x).(!reset)
7	S01	SRst	(reset)
8	S01	S10	(!x).(!reset)
9	S01	S1	(x).(!reset)
10	S10	SRst	(reset)
11	S10	S01	(x).(!reset)
12	S10	S100	(!x).(!reset)
13	S100	SRst	(reset)
14	S100	S100_1	(x).(!reset)
15	S100	S100	(!x).(!reset)
16	S100_1	S100_10	(!x).(!reset)
17	S100_1	SRst	(reset)
18	S100_1	S100_1	(x).(!reset)
19	S100_10	SRst	(reset)
20	S100_10	S100_1	(x).(!reset)
21	S100_10	S100	(!x).(!reset)
22	SRst	SRst	(reset)
23	SRst	S1	(x).(!reset)
24	SRst	S0	(!x).(!reset)