
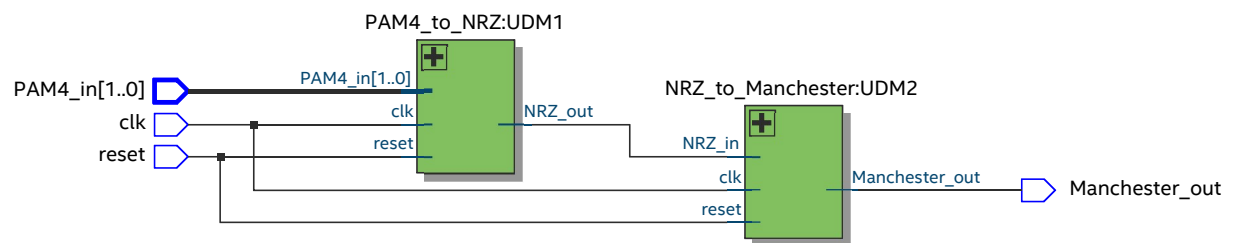


```
1  module PAM4_to_Manchester (
2      Manchester_out,
3      PAM4_in,
4      clk,
5      reset
6  );
7
8  //assign the inputs and outputs as registers and wires
9  input wire    clk, reset;           //clk and reset signal
10 input wire [1:0] PAM4_in;          //2 bits PAM4_in input signal
11 output wire    Manchester_out;      //declare as wire since it will be connected to module
12
13 //internal probe
14 wire NRZ_data;                     //output signal from the PAM4_to NRZ module
15
16 //instantiate the PAM4-NRZ and NRZ-Manchester modules as user define modules (UDM1 and UDM2)
17 PAM4_to_NRZ UDM1 (
18     .NRZ_out(NRZ_data),             //note NRZ_out becomes
19     NRZ_data
20     .PAM4_in(PAM4_in),
21     .clk(clk),
22     .reset(reset)
23 );
24 NRZ_to_Manchester UDM2 (
25     .Manchester_out(Manchester_out),
26     .NRZ_in(NRZ_data),              //note NRZ_in becomes NRZ_data
27     .clk(clk),
28     .reset(reset)
29 );
30
31 endmodule
```

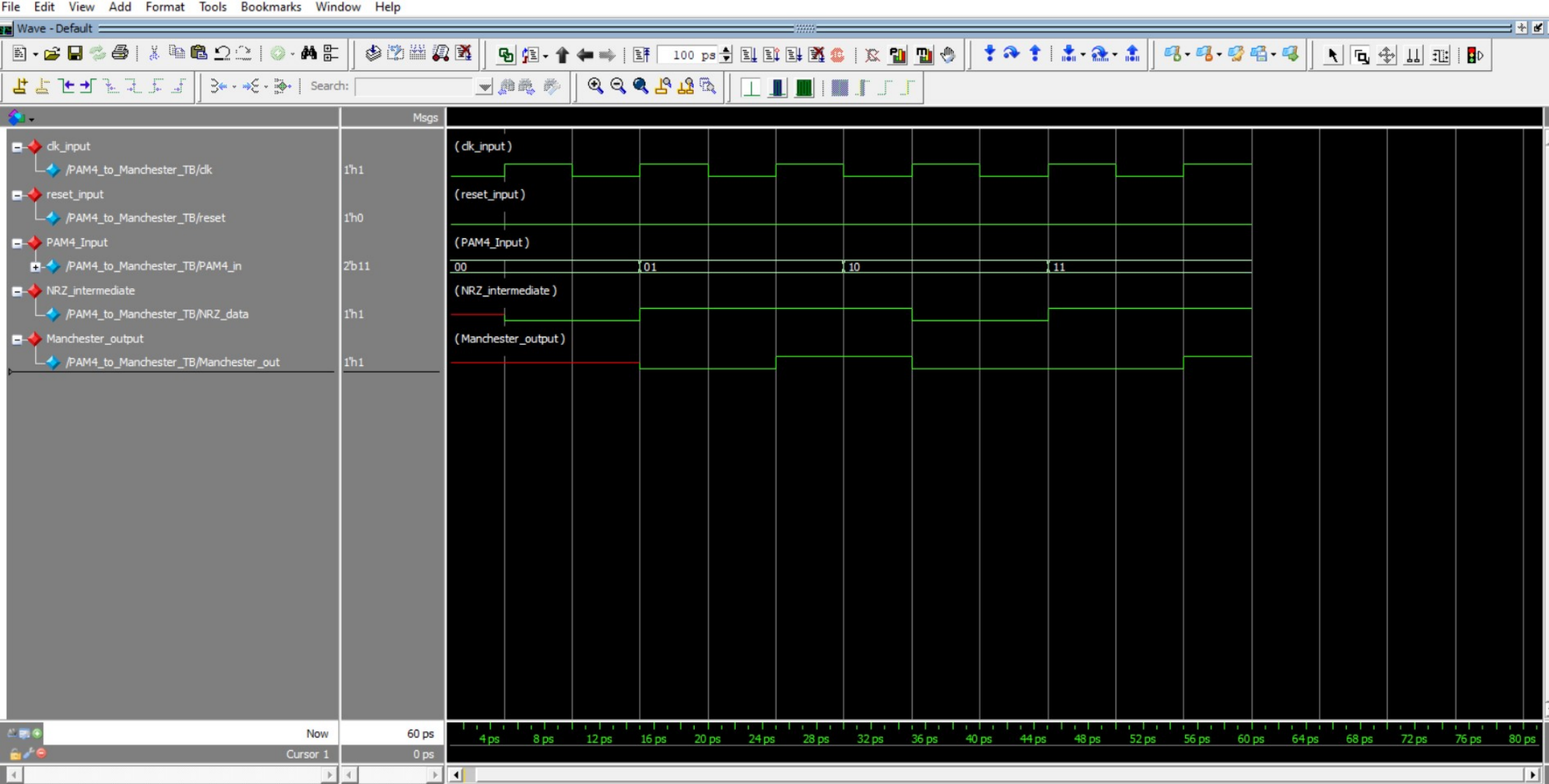

```
1  module PAM4_to_Manchester_TB ();
2
3  //define the registers=wire and wires=registers from desing-to-testbench
4  reg      clk, reset;          //clk and reset signal
5  reg [1:0] PAM4_in;           //2 bits PAM4_in input signal
6  wire      Manchester_out;
7
8  //define the unit under test UUT
9  PAM4_to_Manchester UUT (
10      .Manchester_out(Manchester_out),
11      .PAM4_in(PAM4_in),
12      .clk(clk),
13      .reset(reset)
14  );
15
16  //monitor internal probe
17  assign NRZ_data = UUT.UDM1.NRZ_out;
18
19  //instantiate the clk signal
20  initial
21  begin
22      clk = 1'b0;
23      forever #5 clk = ~clk;    //10ns clk period
24  end
25
26  //instantiate the reset signal
27  initial
28  begin
29      reset = 1'b0;             //togel the reset signal on
30      PAM4_in = 2'b00;
31      #100 reset = 1'b1;        //toggle the reset signal off
32  end
33
34  //instantiate all the posibble states for PAM4_in with time intervals
35  initial
36  begin
37      PAM4_in = 2'b00; #15;
38      PAM4_in = 2'b01; #15;
39      PAM4_in = 2'b10; #15;
40      PAM4_in = 2'b11; #15;
41
42      $stop;
43  end
44
45  //display the results
46  initial begin
47      $display("PAM4_in-----Binary/NRZ_out-----Manchester_out");
48      $monitor("%b          %b          %b ", PAM4_in, NRZ_data,
49      Manchester_out);
50  end
51 endmodule
```



## Output table

#	PAM4_in-----	Binary/NRZ_out-----	Manchester_out
# 00		x	x
# 00		0	x
# 01		1	0
# 01		1	1
# 10		1	1
# 10		0	0
# 11		1	0
# 11		1	1

## PAM4 to Manchester out

- This module instantiates 2 different modules
- The final modules take PAM4 data converts the data to NRZ
- The NRZ data is converter to Manchester code as final output