 


Assignment 4: Problem 2: 4Bit Jerky counter

Using a FSM, design a 4-bit jerky counter that follows the same pattern as the counter given in the book page 226. Test your counter and include the code and simulation results.



For the following solution, the (a) counter was followed. The only difference in the design for (b) will be the output assigned to the different states as shown in the comments within the code.

```

/* -----
Name:      Nashwa Elaraby
file:      Jerky_4Bit_counter
testbench: Jerky_4Bit_counter_tb
Description: Using a FSM, design a 4-bit jerky counter that follows the same
            pattern as the counter given in the book page 226. Test your counter
            and include the code and simulation results.
            Moore FSM
-----
            (a)      0001      (b)      1000
                     0010      0100
            •         0001      1000
                     0100      0010
                     0001      1000
                     1000      0001
----- */

```

```

module Jerky_4Bit_counter (clk, reset, count);

input      clk;
input      reset;
output reg [3:0] count;

reg [2:0] state, next_state;

parameter S0 = 3'b000;
parameter S1 = 3'b001;
parameter S2 = 3'b010;
parameter S3 = 3'b011;
parameter S4 = 3'b100;
parameter S5 = 3'b101;
parameter S6 = 3'b110;


always @ (posedge clk)
if (reset) state <= S0;
else state <= next_state;

always @ *
case (state)
S0 : begin count      = 4'b0001; // count = 1000;
           next_state = S1;      end
S1 : begin count      = 4'b0010; // count = 0100;
           next_state = S2;      end
S2 : begin count      = 4'b0001; // count = 1000;
           next_state = S3;      end
S3 : begin count      = 4'b0100; // count = 0010;
           next_state = S4;      end
S4 : begin count      = 4'b0001; // count = 1000;
           next_state = S5;      end
S5 : begin count      = 4'b1000; // count = 0001;
           next_state = S0;      end
default: begin count      = 4'b0001; // count = 1000;
           next_state = S0;      end
endcase

endmodule

```

 Internal probes to observe the state and the net state registers.



When the reset is active, the FSM counter stays at S0 state.