 


```

1  /*-----
2  Name Lamin Jammeh
3  Class: EE417 Summer 2024
4  Lesson 09 HW Question 3
5  Group: Ron Kalin/ Lamin Jammeh
6  Project Description: Interpolator Filter, the filter takes Data_in and sending through
7  bufffer1 and buffer2 to double the rate at the output
8  -----*/
9
10 module Linear_Interpolator #(parameter word_size = 8)
11     (
12         output reg [word_size-1:0] Data_out,
13         input  [word_size-1:0] Data_in,
14         input  clock, reset
15     );
16
17 // internal registers and wires
18 reg [word_size-1:0] buffer1; // internal register for storing Data_in
19 reg [word_size-1:0] buffer2; // internal register for storing average
20 reg filter;
21
22 always @ (posedge clock)
23     begin
24         if (reset)
25             /*-----
26             @ reset everything goes to zero exception Data_in
27             since Data_in is coming from an external source
28             -----*/
29             begin
30                 buffer1 <= 0;
31                 buffer2 <= 0;
32                 filter <= 0;
33                 Data_out <= 0;
34             end
35         else
36             begin
37                 /*-----
38                 @ reset low the internal filter truns on and the
39                 filtering logic is carry out below
40                 -----*/
41                 filter <= ~filter;
42                 if (filter)
43                     /*-----
44                     when the filter is high perform the following
45                     ** set buffer1 to store the Data_in values
46                     ** set buffer2 to interpolate (average) current Data_in with buffer1
47                     ** set Data_out to be combination of buffer1 and buffer2
48                     -----*/
49                     begin
50                         buffer1 <= Data_in;
51                         buffer2 <= (Data_in + buffer1) >> 1;
52                         Data_out <= buffer1 + buffer2;
53                     end
54                 else
55                     /*-----
56                     when the filter is low or not active
57                     ** set Data_out to be the current value of buffer1
58                     -----*/
59                     begin
60                         Data_out <= buffer1;
61                     end
62                 /*-----
63                 the above logic shows that Data_in is always filter before
64                 getting to Data_out
65                 Data_out only reads from buffer1 and buffer2
66                 -----*/
67             end
68         end
69

```

```
70  endmodule  
71
```



```

1  /*-----*/
2  Name Lamin Jammeh
3  Class: EE417 Summer 2024
4  Lesson 09 HW Question 3
5  Group: Ron Kalin/ Lamin Jammeh
6  Project Description: TestBench for Interpolator Filter
7  -----*/
8  module Linear_Interpolator_tb ();
9
10 //define the registers and wire for the signals to monitor
11 reg      clock, reset;
12 reg [7:0] Data_in;
13 wire [7:0] Data_out;
14
15 //define the internal probes in the testbench for buffer1 and buffer2
16 wire      filter; // New wire for observing filter
17 wire [7:0] buffer1; // New wire for observing buffer1
18 wire [7:0] buffer2; // New wire for observing buffer2
19
20 //Instantiate the unit under test UUT
21 Linear_Interpolator #(8)  UUT (
22     .Data_out(Data_out),
23     .Data_in(Data_in),
24     .clock(clock),
25     .reset(reset)
26 );
27
28 // Assign buffer1 and buffer2 in the testbench to buffer1 and buffer2 in the Unit under test
29 assign filter = UUT.filter;
30 assign buffer1 = UUT.buffer1;
31 assign buffer2 = UUT.buffer2;
32
33 //instantiate the clock cycle
34 initial
35     begin
36         clock = 0;
37         forever #5 clock = ~clock;
38     end
39
40 initial
41     begin
42         //Initialize all the inputs
43         reset = 1;
44         Data_in = 8'b0;
45         #20 reset = 0;
46
47         //multiple Data_in samples and observe the buffer and Data_out
48         Data_in = 8'b10101010;
49         #20 Data_in = 8'b01101001;
50         #20 Data_in = 8'b00110011;
51         #20 Data_in = 8'b11101001;
52
53         //take everything back Data_out back to zero by setting reset to high
54         #20 reset = 1;
55         #20 reset = 0;
56
57         // Final test case to ensure the interpolator works correctly after reset
58         Data_in = 8'b00001001;
59         #20 Data_in = 8'b01101011;
60         #20 Data_in = 8'b11101011;
61         #20 Data_in = 8'b11101111;
62
63         // stop the simulation
64         #20;
65         $stop;
66     end
67
68 // Display the results
69 always @(posedge clock)


```

```
70     begin
71         $display("@ Time = %t  Data_in = %d  Filter = %d  Buffer1 = %d  Buffer2 = %d
72         Data_out = %d", $time, Data_in, filter, buffer1, buffer2, Data_out);
73     end
74 endmodule
```

Output table

```
# @ Time =          5 Data_in =  0 Filter = x Buffer1 =  x Buffer2 =  x Data_out =  x
# @ Time =         15 Data_in =  0 Filter = 0 Buffer1 =  0 Buffer2 =  0 Data_out =  0
# @ Time =         25 Data_in = 170 Filter = 0 Buffer1 =  0 Buffer2 =  0 Data_out =  0
# @ Time =         35 Data_in = 170 Filter = 1 Buffer1 =  0 Buffer2 =  0 Data_out =  0
# @ Time =         45 Data_in = 105 Filter = 0 Buffer1 = 170 Buffer2 =  85 Data_out =  0
# @ Time =         55 Data_in = 105 Filter = 1 Buffer1 = 170 Buffer2 =  85 Data_out = 170
# @ Time =         65 Data_in =  51 Filter = 0 Buffer1 = 105 Buffer2 =  9  Data_out = 255
# @ Time =         75 Data_in =  51 Filter = 1 Buffer1 = 105 Buffer2 =  9  Data_out = 105
# @ Time =         85 Data_in = 233 Filter = 0 Buffer1 =  51 Buffer2 =  78 Data_out = 114
# @ Time =         95 Data_in = 233 Filter = 1 Buffer1 =  51 Buffer2 =  78 Data_out =  51
# @ Time =        105 Data_in = 233 Filter = 0 Buffer1 = 233 Buffer2 = 14  Data_out = 129
# @ Time =        115 Data_in = 233 Filter = 0 Buffer1 =  0 Buffer2 =  0 Data_out =  0
# @ Time =        125 Data_in =  9 Filter = 0 Buffer1 =  0 Buffer2 =  0 Data_out =  0
# @ Time =        135 Data_in =  9 Filter = 1 Buffer1 =  0 Buffer2 =  0 Data_out =  0
# @ Time =        145 Data_in = 107 Filter = 0 Buffer1 =  9 Buffer2 =  4  Data_out =  0
# @ Time =        155 Data_in = 107 Filter = 1 Buffer1 =  9 Buffer2 =  4  Data_out =  9
# @ Time =        165 Data_in = 235 Filter = 0 Buffer1 = 107 Buffer2 =  58 Data_out = 13
# @ Time =        175 Data_in = 235 Filter = 1 Buffer1 = 107 Buffer2 =  58 Data_out = 107
# @ Time =        185 Data_in = 239 Filter = 0 Buffer1 = 235 Buffer2 =  43 Data_out = 165
# @ Time =        195 Data_in = 239 Filter = 1 Buffer1 = 235 Buffer2 =  43 Data_out = 235
```

Bitwave

 

Summary:

- @ reset everything goes to zero except Data_in, since Data_in is coming from an external source
- when the filter is high perform the following
 - set buffer1 to store the Data_in values
 - set buffer2 to interpolate (average) current Data_in with buffer1
 - set Data_out to be combination of buffer1 and buffer2
- when the filter is low or not active
 - set Data_out to be the current value of buffer1

- The above logic shows that Data_in is always filtered before getting to Data_out. Data_out only reads from buffer1 and buffer2