



---

**Objective:** Structural Design using Verilog modules and using the RTL viewer to verify the nested structure of the design.

**Design:**

- (a) Write a gate-level model describing the operation of a TwoBit comparator. The module will have 2 Two-bit inputs: **a**, and **b**. Three outputs indicate whether a equals b, a is less than b, or a is greater than b. Create the Karnaugh map and find the expression for the switching function for **the three outputs**.
- (b) Use the TwoBit comparator to design a FourBit comparator. Add any additional logic needed.
- (c) Verify the connection using the RTL Viewer, and verify the interconnections of the instantiated module.
- (d) The Verilog Code should be well documented.