

```
1  /*-----*
2  Name Lamin Jammeh
3  Class: EE417 Summer 2024
4  Lesson 04 HW Question 4 Part 3
5  Group: Ron Kalin/ Lamin Jammeh
6  Project Description: This portion takes uses a 2-to-1 MUX to select between up and down
7  counter. when the sel bit is high the upcounter output is transfered to the next stage
8  else the downcounter output is transfered to the next state
9  -----*/
10 //Step1: define the module and (port list)
11 module selectorBlock_A (output wire y,
12                         input sel,
13                         input clk,
14                         input reset,
15                         input enable);
16
17 wire [3:0] count;
18 wire [3:0] upcount;
19
20 //step 2 call the file for the code2421_downCounter
21 code2421_downCounter UDM_downCount(
22     .count(count),
23     .clk(clk),
24     .reset(reset),
25     .enable(enable)
26 );
27
28 //call the file for the code2421_upCounter
29 code2421_upCounter UDM_upCount(
30     .upcount(upcount),
31     .clk(clk),
32     .reset(reset),
33     .enable(enable)
34 );
35 //Instantiate the wire and logic gates
36 //note when sel is high we count up and when low we count down
37 //equation for output of mux  $Y = (In\_1 \& sel) \mid (In\_2 \& \sim sel)$ 
38 assign y = (upcount & sel) | (count & ~sel);
39
40 endmodule
```