




Objective:

- Designing Verilog modules using the instantiation of primitive modules and using structural design to build larger modules with more inputs and outputs.
- Creating testbenches that verify the functionality of the modules designed

Assignment I:

Design a **Two-8bit-input** adder using primitive full adders and structural hierarchical design.

 - Design a primitive **Adder_sum** with 3 inputs for a, b, and c_in that finds the LSB of the sum of the three inputs.
- Design a primitive **Adder_carry** with 3 inputs for a, b, and c_in that finds the MSB or carry_out of the sum of the three inputs.
- Design a **full_adder** top module that instantiates the two primitives created in parts (a) and (b) as shown in the given netlist viewer.



- Create a higher level two-4bit_input adder by instantiating the single-bit full adder 4 times as follows as indicated in the book and the PowerPoint document.
- Design your top module **Two-8bit-input (sum_out, a_in, b_in)** that add two 8-bit inputs. Make sure that the size of the output sum can accommodate the maximum numbers that can be reached by the inputs a_in and b_in without any overflow.
- Create a testbench that tests the functionality of the single building blocks of the design as well as the interconnections.

Assignment II:

Design a module using the structural design of simple logic gates that takes as an input a 4bit word and has two single-bit outputs divBy3 and divBy5:

divBy3 is raised to a logic high if the 4-bit input is divisible by 3 including 0.

divBy5 is raised to a logic high if the 4-bit input is divisible by 5 including 0.

- Use Karnaugh map to derive the switching function for the two output bits.
- Use simple logic gates and internal wires to build the structural design for the module.
- Create a testbench to verify the functionality of your design.