

```

1  /*-----FIR Pipeline
   MAC-----*/
2  /*-----
   -----
3  Name Lamin Jammeh
4  Class: EE417 Summer 2024
5  Lesson 10 HW Question 3
6  Group: Ron Kalin/ Lamin Jammeh
7  Project Description: In this module the Pipeline registers are placed at the output of the
   adders
8  note that Current_adder = Prev_adder + b(n) * Sample_Array[n]
9  -----*/
10
11 module FIR_Pipeline_MAC (FIR_out_pipeline, Sample_in, clock, reset);
12
13 //define the parameter sets for the design
14 parameter FIR_order      = 6;
15 parameter Sample_size    = 6;           //maximum sample value is 63
16 parameter weight_size    = 4;           //maximum value may be 31
17 parameter word_size_out  = 2 * Sample_size + 3; //log2(2^2 * 2^5 * (order+1))
18 parameter product_size   = Sample_size + weight_size + 3;
19
20 //define output
21 output reg [word_size_out-1:0] FIR_out_pipeline;
22
23 //define inputs
24 input  [Sample_size-1:0] Sample_in;
25 input  clock, reset;
26
27 //define the filter coefficients
28 parameter b0 = 4'd2;
29 parameter b1 = 4'd5;
30 parameter b2 = 4'd9;
31 parameter b3 = 4'd14;
32 parameter b4 = 4'd9;
33 parameter b5 = 4'd5;
34 parameter b6 = 4'd2;
35
36
37 reg [Sample_size-1:0] Sample_Array[1:FIR_order]; //5th coefficient
   multiplied by Data_in
38 integer k;
39
40 //define PR0 to PR3 as registers
41 reg [word_size_out-1:0] PR0 [0:FIR_order];
42 reg [word_size_out-1:0] PR1 [1:FIR_order];
43 reg [word_size_out-1:0] PR2 [2:FIR_order];
44
45 //define the transition logic
46 always @ (posedge clock)
47     if (reset == 1)
48     /*-----
49     if reset is high do the following
50     *****set all Pipeline registers to zero
51     *****IR = 0      Input register or Sample_Array
52     *****PR = 0      Pipeline register or PR
53     *****OR = 0      Output register or FIR_out_pipeline
54     -----*/
55     begin
56         //The input shift register
57         for (k=1; k <= FIR_order; k = k + 1)
58             Sample_Array[k] <= 0;
59
60         //The pipeline register
61         for (k = 0; k <= FIR_order; k = k + 1)
62             PR0[k] <= 0;
63         //The pipeline register
64         for (k = 1; k <= FIR_order; k = k + 1)

```

```

65         PR1[k] <= 0;
66
67     //The pipeline register
68     for (k = 2; k <= FIR_order; k = k + 1)
69         PR2[k] <= 0;
70
71     //The output register
72     FIR_out_pipeline <= 0;
73 end
74
75 else
76     /*-----
77     if reset is low do the following
78     *****1 => move the Sample in into a cutset (Input register) to reduce idle time
of the input
79     *****2 => PR = Prev_PR + b(n) * x[n] since the first PR is the at the output of
the first adder
80     *****3 => add all the products to generate the output
81     -----*/
82     begin
83         //The input shift register
84         Sample_Array[1] <= Sample_in;
85         for (k = 2; k <= FIR_order; k = k + 1)
86             Sample_Array[k] <= Sample_Array[k-1];
87
88         //@ input of add_0 there is no Pipeline Register
89         //PR0[0] <= b0 * Sample_in; //ignore the other input (c_in = 0) to
the summation (add_0)
90
91         //@ input of add_1 or output of add_0 there is PR0 and b1*Sample_in[1]
92         //make sure the countour line with pipeline registers is extended to rest of the
coefficients from b2...bn for data coherency
93         PR0[1] <= b1 * Sample_Array[1] + (b0 * Sample_in);
94         PR0[2] <= b2 * Sample_Array[2];
95         PR0[3] <= b3 * Sample_Array[3];
96         PR0[4] <= b4 * Sample_Array[4];
97         PR0[5] <= b5 * Sample_Array[5];
98         PR0[6] <= b6 * Sample_Array[6];
99
100        //@ input of add_2 or output of add_1 there is PR1 and b2*Sample_in[2]
101        //PR2[2] <= PR0[1] + PR0[2];
102
103        //@ input of add_3 or output of add_2 there is PR2 and b3*Sample_in[3]
104        //make sure the countour line with pipeline registers is extended to rest of the
coefficients from b4...bn for data coherency
105        PR1[3] <= PR0[3] + (PR0[1] + PR0[2]);
106        PR1[4] <= PR0[4];
107        PR1[5] <= PR0[5];
108        PR1[6] <= PR0[6];
109
110        //@ input of add_4 or output of add_3 there is PR3 and b4*Sample_in[4]
111        //PR4[4] <= PR0[4] + PR1[3];
112
113        //@ input of add_5 or output of add_4 there is PR4 and b5*Sample_in[5]
114        //make sure the countour line with pipeline registers is extended to rest of the
coefficients from b6...bn for data coherency
115        PR2[5] <= PR1[5] + (PR1[4] + PR1[3]);
116        PR2[6] <= PR1[6];
117
118        //The output register
119        FIR_out_pipeline <= PR2[6] + PR2[5];
120    end
121 endmodule

```