

```

1  /*-----
2  Name Lamin Jammeh
3  Class: EE417 Summer 2024
4  Lesson 09 HW Question 3
5  Group: Ron Kalin/ Lamin Jammeh
6  Project Description: Interpolator Filter, the filter takes Data_in and sending through
7  bufffer1 and buffer2 to double the rate at the output
8  -----*/
9
10 module Linear_Interpolator #(parameter word_size = 8)
11     (
12         output reg [word_size-1:0] Data_out,
13         input  [word_size-1:0] Data_in,
14         input  clock, reset
15     );
16
17 // internal registers and wires
18 reg [word_size-1:0] buffer1; // internal register for storing Data_in
19 reg [word_size-1:0] buffer2; // internal register for storing average
20 reg filter;
21
22 always @ (posedge clock)
23     begin
24         if (reset)
25             /*-----
26             @ reset everything goes to zero exception Data_in
27             since Data_in is coming from an external source
28             -----*/
29             begin
30                 buffer1 <= 0;
31                 buffer2 <= 0;
32                 filter <= 0;
33                 Data_out <= 0;
34             end
35         else
36             begin
37                 /*-----
38                 @ reset low the internal filter truns on and the
39                 filtering logic is carry out below
40                 -----*/
41                 filter <= ~filter;
42                 if (filter)
43                     /*-----
44                     when the filter is high perform the following
45                     ** set buffer1 to store the Data_in values
46                     ** set buffer2 to interpolate (average) current Data_in with buffer1
47                     ** set Data_out to be combination of buffer1 and buffer2
48                     -----*/
49                     begin
50                         buffer1 <= Data_in;
51                         buffer2 <= (Data_in + buffer1) >> 1;
52                         Data_out <= buffer1 + buffer2;
53                     end
54                 else
55                     /*-----
56                     when the filter is low or not active
57                     ** set Data_out to be the current value of buffer1
58                     -----*/
59                     begin
60                         Data_out <= buffer1;
61                     end
62                 /*-----
63                 the above logic shows that Data_in is always filter before
64                 getting to Data_out
65                 Data_out only reads from buffer1 and buffer2
66                 -----*/
67             end
68         end
69

```

70 `endmodule`
71