

```

1  // ee417 lesson 7 Assignment 1 L7A1
2  // Name: Ron Kalin, Date: 06-25-24 Group: Kalin/Jammeh
3  // Design: Sequential_multiplier
4  // top level module raises a ready flag when ready to load new input words
5  // user should activate a start input to indicate a new multiplication operation starts
6  module Sequential_multiplier (product, final_product,
7                               Ready, start,
8                               word1, word2,
9                               clk, rst);
10 parameter L_WORD = 4; //Datapathsize
11 output [2*L_WORD-1: 0] product, final_product;
12 output Ready;
13 input [L_WORD -1: 0] word1, word2;
14 input start, clk, rst;
15
16 reg [L_WORD-1:0] mcand, mult;
17
18 wire multiplier_LSB, Load_words, shift, Add, latch, zero_flag;
19 wire [L_WORD-2:0] state;
20
21 Datapath M1 (product, final_product,
22             Ready, multiplier_LSB, zero_flag,
23             word1, word2,
24             Load_words, shift, Add, latch,
25             clk, rst);
26
27 controller M2 (Load_words, shift, Add, latch, state,
28               Ready, multiplier_LSB, start, zero_flag,
29               clk, rst);
30
31 endmodule
32
33 //Datapath
34 module Datapath (product, final_product,
35                 Ready, multiplier_LSB, zero_flag,
36                 word1, word2,
37                 Load_words, shift, Add, latch,
38                 clk, rst);
39
40 parameter L_WORD= 4; //declare parameter values
41
42 //declare outputs and input
43 output reg [2*L_WORD-1:0] product, final_product;
44 output reg Ready;
45 output multiplier_LSB, zero_flag;
46 input [ L_WORD-1:0] word1, word2;
47 input Load_words, shift, Add, latch;
48 input clk, rst;
49 //declare internal wires
50 reg [2*L_WORD-1: 0] multiplicand;
51 reg [ L_WORD-1: 0] multiplier;
52 //assign values
53 assign multiplier_LSB = multiplier[0]; //least significant bit of multiplier
54 assign zero_flag = (multiplier == 0); //if multiplier=all zeros, zero_flag=1
55
56 //create always block
57 always @ (posedge clk)
58 begin
59     if (rst) begin multiplier <= 0; //if reset =1 then zero
60                 multiplicand <= 0;
61                 product <= 0;
62                 final_product <= 0;
63                 Ready <= 1; end //ready high= accept input words
64     else if (Load_words) begin multiplicand <= word1; //Load_words=1
65                               multiplier <= word2; //then m..cand gets value of word1
66                               product <= 0; //mult gets value word2
67                               final_product <= 0; //prod and final_prod=0
68                               Ready <= 0; end //ready low means calculate
69     else if (shift) begin multiplier <= multiplier >> 1; //shift right 1


```

```

70         multiplicand <= multiplicand << 1; //shift left 1
71         Ready <= 0; end
72     else if (Add)      begin product <= product + multiplicand;
73                         Ready <= 0; end
74     else if (latch)    begin final_product <= product; //adding done
75                         Ready <= 1; end //ready for new input
76     else               begin end
77 end
78
79 endmodule
80
81 //controller
82 module controller (Load_words, shift, Add, latch, state,
83                 Ready, multiplier_LSB, start, zero_flag,
84                 clk, rst);
85     //parameter L_WORD= 4; //declare parameter values
86
87     //declare outputs/inputs, control unit only handles single bit inputs and outputs
88     output reg Load_words, shift, Add, latch;
89     output reg [2:0] state;
90     input      Ready, multiplier_LSB, start, zero_flag;
91     input      clk, rst;
92
93     reg [2:0] next_state; //3 bits for up to 8 states
94     //build code from FSM diagram
95
96     //declare states from FSM
97     parameter idle    = 3'b000;
98     parameter loading = 3'b001;
99     parameter loaded  = 3'b010;
100    parameter add      = 3'b011;
101    parameter shift    = 3'b100;
102    parameter buff     = 3'b101;
103    parameter ltch     = 3'b110;
104
105    always @ (posedge clk)
106    if (rst) state <= idle;
107    else state <= next_state;
108
109    always @ *
110    //assign probe <= state;
111    case (state)
112    idle: begin
113        Load_words = 1'b0;
114        latch      = 1'b0;
115        Add        = 1'b0;
116        shift      = 1'b0;
117        if (Ready && start) next_state = loading;
118        else next_state = idle;    end
119    loading: begin
120        Load_words = 1'b1;
121        latch      = 1'b0;
122        Add        = 1'b0;
123        shift      = 1'b0;
124        next_state = loaded;    end
125    loaded: begin //2nd load stage is needed because input data changes
126        Load_words = 1'b0; //1 cycle is needed to look at the change
127        latch      = 1'b0;
128        Add        = 1'b0;
129        shift      = 1'b0;
130        if (multiplier_LSB) next_state = add;
131        else next_state = shift;    end
132    add: begin
133        Load_words = 1'b0;
134        latch      = 1'b0;
135        Add        = 1'b1; //output changes
136        shift      = 1'b0;
137        next_state = shift;    end //shift always follows after an add
138    shift: begin


```


```
139         Load_words = 1'b0;
140         latch       = 1'b0;
141         Add         = 1'b0;
142         shift       = 1'b1;
143         next_state = buff;           end
144     buff: begin //buffer state needed after shift because input data changes
145         Load_words = 1'b0; //1 cycle is needed to take a look at the change
146         latch       = 1'b0;
147         Add         = 1'b0;
148         shift       = 1'b0;
149         if (multiplier_LSB) next_state = add;
150         else if (zero_flag) next_state = ltch;
151         else next_state = shft;
152     end
153     ltch: begin
154         Load_words = 1'b0;
155         Add         = 1'b0;
156         shift       = 1'b0;
157         latch       = 1'b1;
158         next_state = loading;     end //cycle back to loading stage
159     //below is initial pseudocode
160     //if rst=1 then load_words=0, shift=add=latch=0
161     //if rst=0 and start=1 and ready=1 then load_words=1, shift=0, add=0, latch=0
162     //if rst=0 and start=1 and ready=0 then
163     //if multiplier_LSB=0 then load_words=0, shift=1, add=0, latch=0
164     //
165     //else if multiplier_LSB=1 then load_words=0, shift=0, add=1, latch=0
166     //
167     //else if zero_flag=1      then load_words=0, shift=0, Add=0, latch=1, ready=1 ...done
168     endcase
169 endmodule
170
171
```

 

Date: June 30, 2024

Project: Sequential_multiplier

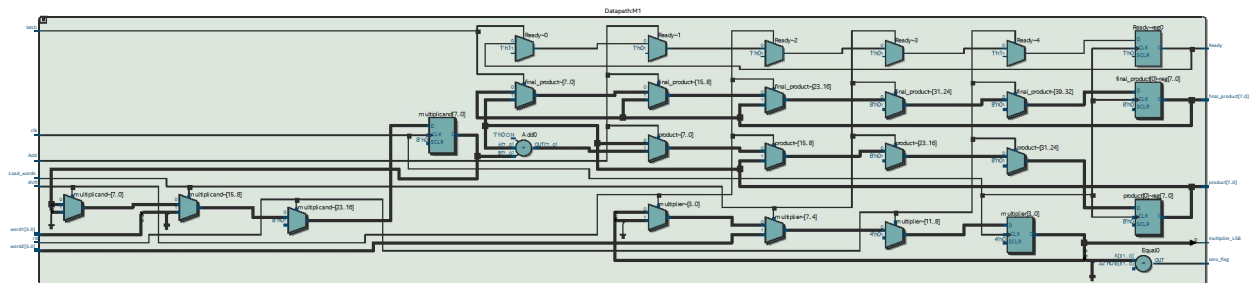

 


```

1  /*-----
2  Name Ron Kalin
3  Class: EE417 Summer 2024
4  Lesson 07 HW Question 01
5  Group: Ron Kalin/ Lamin Jammeh
6  Project Description: test-bench for sequential multiplier
7  -----*/
8  module Sequential_multiplier_tb ();
9
10 //set the parameters wires and registers
11 parameter word_size = 4; //bit length of word inputs
12 parameter half_cycle = 5; //half cycle time of clock
13 parameter full_cycle = 10; //full cycle time of clock
14 parameter cycle_time = 160; //number of cycles before next cycle
15 /*top level module under test original declaration
16 module Sequential_multiplier (product, final_product,
17                               Ready, start,
18                               word1, word2,
19                               clk, rst);*/
20 //define outputs as wires, inputs as registers
21 wire [2*word_size-1: 0] product, final_product;
22 wire Ready;
23 wire [word_size-2:0] stateProbe2; //internal probe wire for troubleshooting
24 wire [word_size-1:0] multiplierProbe;
25 wire [2*word_size-1: 0] multiplicandProbe;
26 reg [word_size-1: 0] multiplier2;
27 reg [2*word_size-1: 0] multiplicand1;
28 reg start, clk, rst;
29 integer cycles;
30 //define the unit under test UUT
31 Sequential_multiplier UUT (product, final_product,
32                            Ready, start,
33                            multiplicand1, multiplier2,
34                            clk, rst);
35 //internal probes to track logic and troubleshoot
36 //assign stateProbe = UUT.state;
37 assign stateProbe2 = UUT.M2.state; //UUT=top module, M2 =submodule instance name, state is
    register
38 assign multiplierProbe = UUT.M1.multiplier;
39 assign multiplicandProbe = UUT.M1.multiplicand;
40
41 //instantiate clock
42 initial
43     begin: clock_loop
44         clk = 1'b1;
45         cycles = 0;
46         forever begin
47             #half_cycle clk = ~clk;
48             cycles = cycles + 1;
49         end
50         if (cycles == cycle_time) disable clock_loop;
51     end
52
53 //define input words and observe the outputs
54 initial begin
55     start = 1; //start to high means start process
56     rst = 1; //reset high will set everything to zero and ready to high
57     multiplicand1 = 8'b0000_0101; //initialize both words random test values
58     multiplier2 = 4'b0101;
59     #10 rst = 0; //reset low
60     #cycle_time
61     rst = 1;
62     multiplicand1 = 8'b0000_1111; //initialize both words random test values
63     multiplier2 = 4'b1101;
64     #10 rst = 0;
65     #cycle_time //disable clock_loop;
66 //end
67 multiplier2 = 4'b0000;
68 multiplicand1 = 8'b0000_0000;

```

```
69  forever begin: input_loop
70      multiplier2 = multiplier2 + 1'b1; //increment multiplier
71      if (multiplier2 == 4'b1111) begin //if multiplier reaches max value
72          multiplier2 = 4'b0001; //reset multiplier to one
73          multiplicand1 = multiplicand1 + 1'b1; //incr multiplicand
74      end
75      if (multiplicand1 == 8'b1111_1111 && multiplier2 == 4'b1111) begin //both reach max value
76          disable input_loop; disable clock_loop; end
77      #cycle_time;
78  end
79  end
80  ////monitor and display the output
81  initial begin
82      $monitor("multiplicand1 = %b: multiplier2 = %b: stateProbe2=%d: product=%d:
83      final_product=%d:",multiplicand1, multiplier2,
84          stateProbe2,product, final_product);
85  end
86  endmodule
```

 [illegible]