

```

1  /*-----
2  Name:    Lamin Jammeh
3  Class:   CE6325 Fall_2024
4  Project: 1
5  Project Description: Teestbench for Project1
6  **create a clock signal
7  **Initialize all the input signals
8  **apply some Sample Data_in as [6325] in 10 time unit intervals
9  **apply reset to test the reset signal
10 **apply anothe set of sample Data_in as [2024] in 10 time unit intervals
11 **monitor the signals and end the test
12
13 -----*/
14
15 module FIR_Filter_Project1_tb;
16
17 parameter order = 4;
18 parameter word_size_in = 4;
19 parameter word_size_out = 2 * word_size_in + 1;
20
21 //declare ports for the design
22 wire [word_size_out-1:0] Data_out;
23 reg [word_size_in-1:0] Data_in;
24 reg clock, reset;
25
26 //declare the unit under test UUT
27 FIR_Filter_Project1 #(order, word_size_in, word_size_out) UUT(.Data_out(Data_out),
28                                                                .Data_in(Data_in),
29                                                                .clock(clock),
30                                                                .reset(reset)
31                                                                );
32
33 // Instantiate the clock signal
34 initial
35 begin
36     clock = 0;
37     forever #5 clock = ~clock;
38 end
39
40 //Instantiate the diiferent test scenarios to validate the design
41 //*****Scenario 1 initialize all input signals
42 initial
43 begin
44     reset = 1;
45     Data_in = 0;
46
47     #10 reset = 0; //wait for 10 timing units for the inital signals to go through
48
49 //Scenario 2 apply some Data_in samples and observe the outputs use [6 3 2 5] @ 100 time
unit intervals
50     #100 Data_in = 4'd6; //make sure time is long enough for Data_in to mkae it
to the last filter Coefficient
51     #100 Data_in = 4'd3;
52     #100 Data_in = 4'd2;
53     #100 Data_in = 4'd5;
54
55 //Scenario 3 test the reset signal to validate the behavior
56     #10 reset = 1; //Sample registers should be cleared
57     #10 reset = 0; //Sample register will accept Data_in
58
59 //Scenario 4 apple more samples to make sure the design works after reset
60     #100 Data_in = 4'd2;
61     #100 Data_in = 4'd0;
62     #100 Data_in = 4'd2;
63     #100 Data_in = 4'd4;
64
65 //stop the test
66     #100 $stop;
67 end

```

```
68
69 // Monitor output
70 initial
71     begin
72         $monitor("Time: %4t\t | Data_in: %0d\t | Data_out: %3d\t | reset: %b," $time,
73             Data_in, Data_out, reset); //use %10 as padding for time and data_out
74     end
75 endmodule
76
77
78
```