
 


General Types of Memories in Hardware Design

ROM Read Only Memory

 


Asynchronous ROM design – no clock




Synchronous ROM design – clocked

Any ROM design has an input address to determine the location of the memory register to be accessed. ROMs do not have data to be written into the memory, as they are **Read ONLY**. All ROMs have an output data port.

RAM Read And Write Memory

 


Asynchronous RAM design

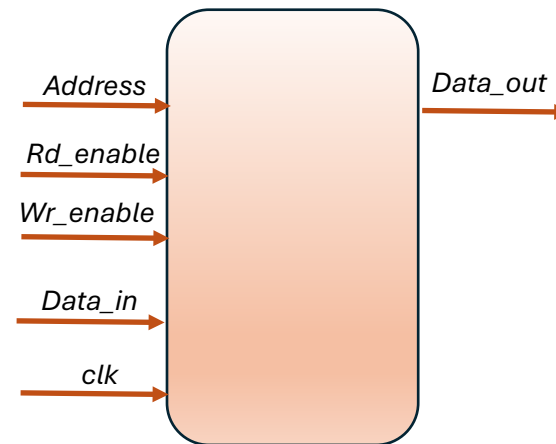

Synchronous RAM design

The RAM may have one clock for the read and one clock for the write, or just a single clock for both. Some RAMs can read and write at the same time, and will have different read and write address lines.

FIFO First In First Out

 

Synchronous FIFO design

Notice that the FIFO **does not have address input ports**. The FIFO internal pointers decide where to write the incoming data, and what data to read based on a First_in First_out sequence. If the stack of FIFO memory is full, and a wr_enable request is placed at the input, the incoming data will be ignored because the stack is full. Only after some data are read and the full flag is low, more data can be written in the stack of memory. Also, if all the data has been read, the empty flag will be raised. The full and empty flags are internally managed based on the read and write pointers and the difference between them.

ROM Design Examples:

1. Look-up table for data conversion: Compare the conversion code using the case structure versus the ROM

```
module Binary_7segment (BCD, SevenSegment);
input   [3:0] BCD;
output reg [6:0] SevenSegment;

parameter BLANK = 7'b111_1111; // 127
parameter ZERO  = 7'b100_0000; // 64
parameter ONE   = 7'b111_1001; // 121
parameter TWO   = 7'b010_0100; // 36
parameter THREE = 7'b011_0000; // 48
parameter FOUR  = 7'b001_1001; // 25
parameter FIVE  = 7'b001_0010; // 18
parameter SIX   = 7'b000_0001; // 1
parameter SEVEN = 7'b111_1000; // 120
parameter EIGHT = 7'b000_0000; // 0
parameter NINE  = 7'b001_1000; // 24

always @ *
case (BCD)
4'b0000 : SevenSegment = ZERO;
4'b0001 : SevenSegment = ONE;
4'b0010 : SevenSegment = TWO;
4'b0011 : SevenSegment = THREE;
4'b0100 : SevenSegment = FOUR;
4'b0101 : SevenSegment = FIVE;
4'b0110 : SevenSegment = SIX;
4'b0111 : SevenSegment = SEVEN;
4'b1000 : SevenSegment = EIGHT;
4'b1001 : SevenSegment = NINE;
default : SevenSegment = BLANK;
endcase
endmodule
```

```
module Binary_7segment_converter (BCD, SevenSegment);
input   [3:0] BCD;
output   [6:0] SevenSegment;

// Instantiation of the ROM look-up-table
Binary_7segment_ROM lookUpTable (.ROM_address (BCD),
                                  .ROM_data    (SevenSegment) );

endmodule

module Binary_7segment_ROM (ROM_address, ROM_data);

input   [3:0] ROM_address;
output   [6:0] ROM_data;

reg [6:0] ROM [15:0]; // width is 7 bits and depth is 16 words


parameter BLANK = 7'b111_1111; // 127
parameter ZERO  = 7'b100_0000; // 64
parameter ONE   = 7'b111_1001; // 121
parameter TWO   = 7'b010_0100; // 36
parameter THREE = 7'b011_0000; // 48
parameter FOUR  = 7'b001_1001; // 25
parameter FIVE  = 7'b001_0010; // 18
parameter SIX   = 7'b000_0001; // 1
parameter SEVEN = 7'b111_1000; // 120
parameter EIGHT = 7'b000_0000; // 0
parameter NINE  = 7'b001_1000; // 24

initial
begin
ROM [0] = ZERO;
ROM [1] = ONE;
ROM [2] = TWO;
ROM [3] = THREE;
ROM [4] = FOUR;
ROM [5] = FIVE;
ROM [6] = SIX;
ROM [7] = SEVEN;
ROM [8] = EIGHT;
ROM [9] = NINE;
ROM [10] = BLANK;
ROM [11] = BLANK;
ROM [12] = BLANK;
ROM [13] = BLANK;
ROM [14] = BLANK;
ROM [15] = BLANK;
end

endmodule
```

2. Look-up table to find the next_state and output value for a FSM:

Mealy FSM to detect a 1000 sequence

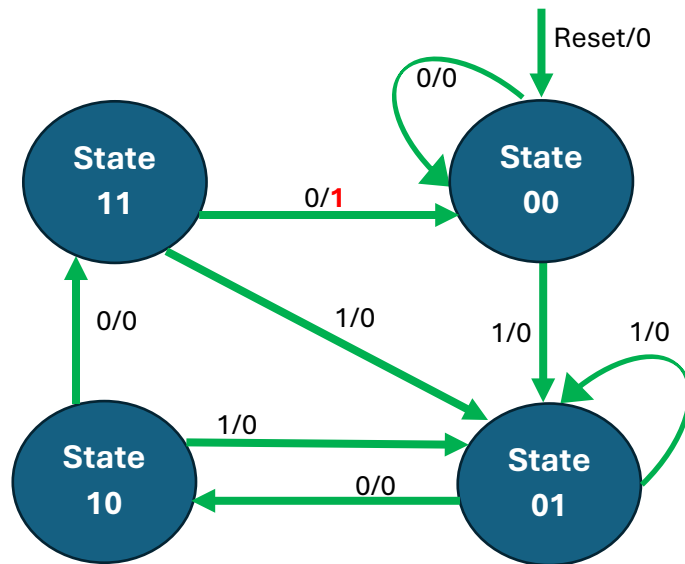

state	x_in	next_state	z_out
00	0	00	0
00	1	01	0
01	0	10	0
01	1	01	0
10	0	11	0
10	1	01	0
11	0	00	1
11	1	01	0

```

module ROM_FSM (clk, reset, z_out, x_in);
input      clk, reset, x_in;
output reg z_out;

reg [1:0] state;
wire [1:0] next_state;
wire [2:0] address, data_out;

always @ (posedge clk)
  if (reset) begin
    state <= 2'b00;
    z_out <= 1'b0;
  end
  else begin
    state <= next_state;
    z_out <= z;
  end

// combinational logic to find next_state and z

assign address = {state, x_in};
assign next_state = data_out [2:1];
assign z = data_out [0];

ROM lookupTable (address, data_out);

endmodule

module ROM (address, data_out);
input [2:0] address;
output reg [2:0] data_out;

reg [2:0] ROM_reg [7:0] ;

initial
begin
  ROM_reg [0] = 3'b000;
  ROM_reg [1] = 3'b010;
  ROM_reg [2] = 3'b100;
  ROM_reg [3] = 3'b010;
  ROM_reg [4] = 3'b110;
  ROM_reg [5] = 3'b010;
  ROM_reg [6] = 3'b001;
  ROM_reg [7] = 3'b010;
end

endmodule
  
```

Example designs for two RAM modules:

```
module RAM_ONE_clk (
    input      clk,           // one clk for read and write
    input  [ 5:0] address,     // one address for read and write    (log2(memory depth) log2(64) = 6)
    input      mem_read,      // read enable
    input      mem_write,     // write enable
    input  [15:0] data_in,
    output [15:0] data_out
);

reg [15:0] memory [63:0];      // The memory has a depth of 64 words (addresses from 0 to 63)

always @(posedge clk)
    if(mem_write) memory[address] <= data_in;    // synchronized write

assign data_out = (mem_read == 1'b1) ? memory[address] : 16'd0; // combinational logic for data_out
endmodule
```




```
module RAM_clear (
    input      clk,           // one clk for read and write
    input  [ 5:0] address,     // (log2(memory depth) log2(64) = 6)
    input      read_or_write,  // read = 0, write = 1
    input      clear,          // clear memory option
    input  [15:0] data_in,
    output reg [15:0] data_out // registered output
);

reg [15:0] memory [63:0];      // The memory has a depth of 64 words (addresses from 0 to 63)
integer k;

always @(posedge clk)
    if (clear)
        for (k = 0 ; k < 64 ; k = k+1)
            memory[k] <= 16'd0;
    else if (read_or_write)
        memory[address] <= data_in;    // priority to write
    else if (~read_or_write)
        data_out <= memory[address];

endmodule
```

FIFO Explanation:

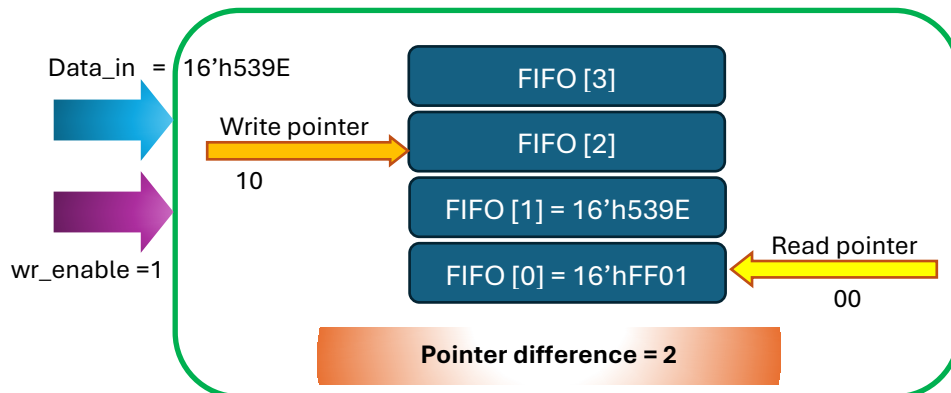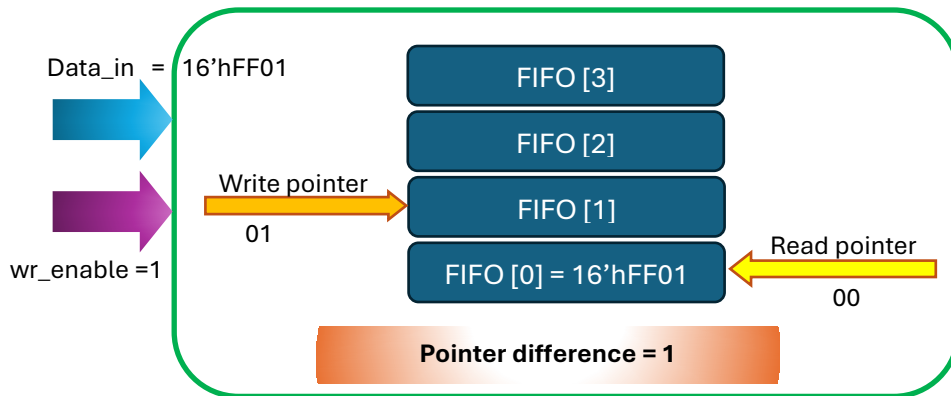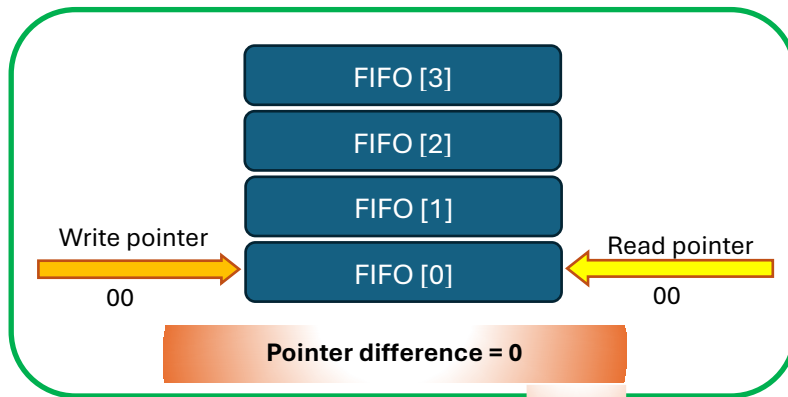

A FIFO with a memory stack of just 4 memory locations (words). The width of each word is 16 bits [15:0]. As we have 4 memory locations (FIFO depth is 4), we need 2 bits to address the memory locations, each by a unique address.

Before writing anything to the FIFO, both the read and write pointers will be pointing at address 00.


The pointer difference will be 0 indicating that the FIFO is empty. No reading will be allowed as there is no saved data.

When a `wr_enable` is activated, the value on the `Data_in` will be passed to the FIFO and written in the memory location pointed at by the write pointer. Then, the write pointer will be incremented by 1 (00+1=01 in binary), and the pointer difference will be incremented by 1 (000+1 = 001 in binary). The empty flag will be now 0. The FIFO is not empty anymore. It stores a value that was not read yet.


The pointers and memory locations will be updated by the assigned values at the positive clock edge.

If the `wr_enable` is active again, the value on the `Data_in` will be passed to the FIFO and written in the memory location pointed at by the write pointer. Then, the write pointer will be incremented by 1 (01+1=10 in binary), and the pointer difference will be incremented by 1 (001+1 = 010 in binary). The FIFO is not empty and it stores two values that were not read yet.

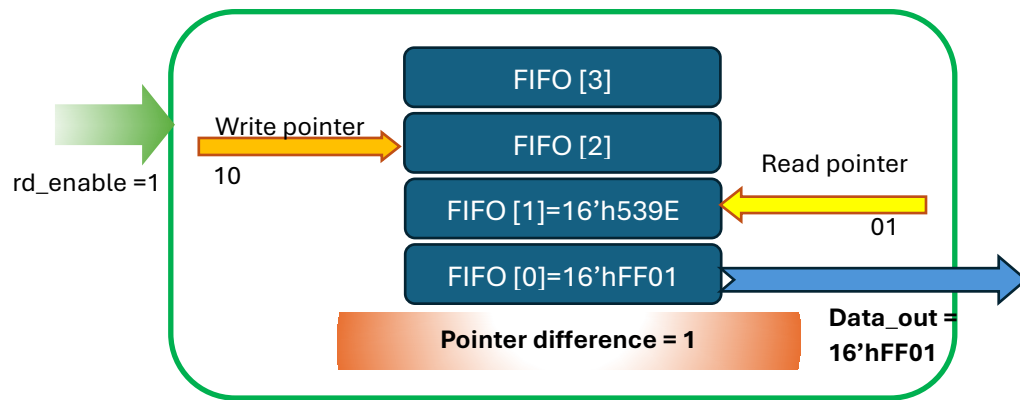The pointers and memory locations are updated by the assigned values at the positive clock edge.




If the read enable is activated, then the data content saved in the memory location pointed at by the read pointer will be sent to the output data port. Then Read pointer will be incremented by 1 ($00+1=01$ in binary). The pointer difference will be decremented by 1 ($10 - 1=01$ in binary) This indicates that there is exactly one data saved in the FIFO that was written and not read yet. (That is the 16'h539E saved in the memory location 01). Now what about the 16'hFF01 value saved in memory location 00? This value has been already read by now, it is OK to overwrite it! We will not delete it, but we can overwrite it when the memory space is needed for new incoming values.

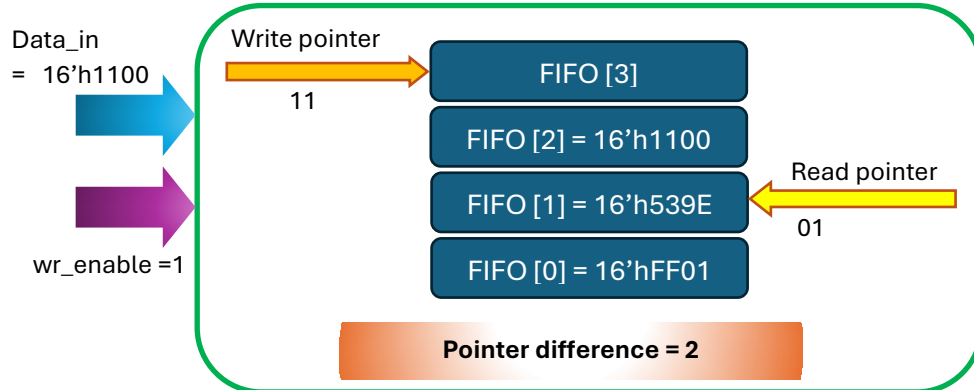


When a **wr_enable** is activated, the value on the **Data_in** will be passed to the FIFO and written in the memory location pointed at by the write pointer. Then, the write pointer will be incremented by 1 ($10+1=11$ in binary), and the pointer difference will be incremented by 1 ($001+1 = 010$ in binary). The FIFO is not empty, it stores 2 values that were not read yet.

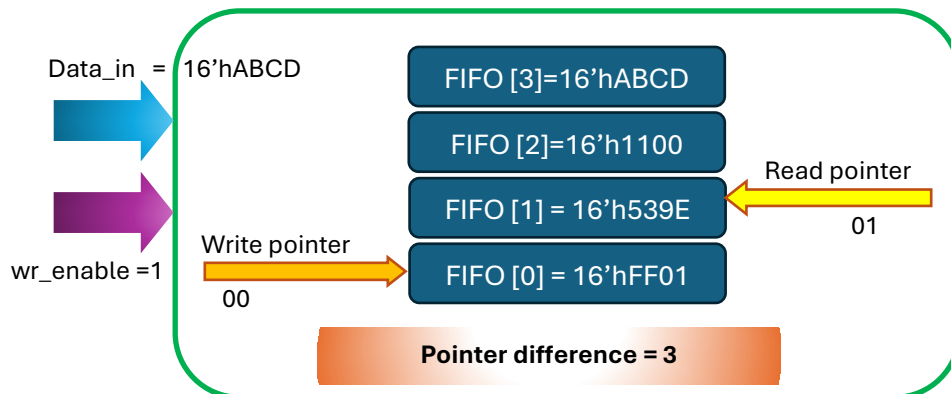The pointers and memory locations will be updated by the assigned values at the positive clock edge.




If the **wr_enable** is active again, the value on the **Data_in** will be passed to the FIFO and written in the memory location pointed at by the write pointer. Then, the write pointer will be incremented by 1 ($11+1=00$ in binary, as the overflow bit does not exist 100 with the size of the address not large enough), and the pointer difference will be incremented by 1 ($010+1 = 011$ in binary). The FIFO is not empty and it stores 3 values that were not read yet. This number is saved by the pointer difference.

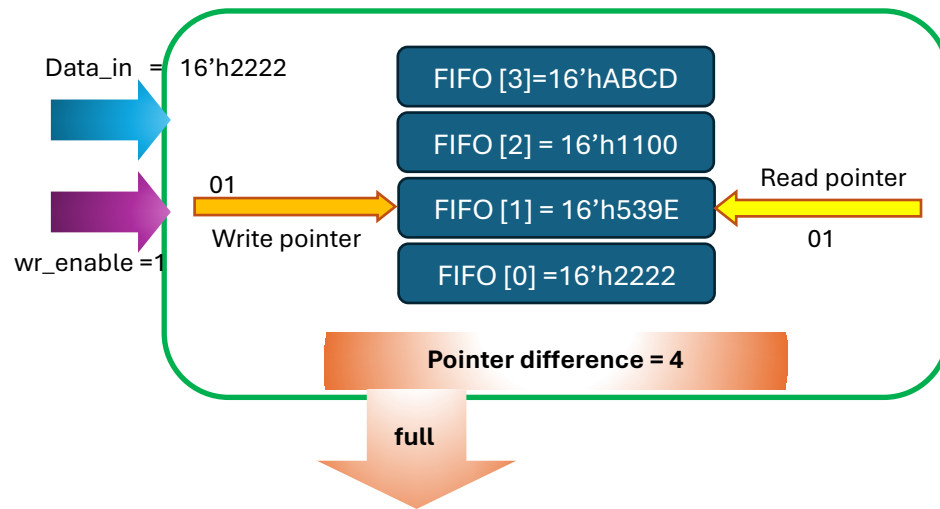
The pointers and memory locations are updated by the assigned values at the positive clock edge.



If the wr_enable is active again, the value on the Data_in will be passed to the FIFO and written in the memory location pointed at by the write pointer. Then, the write pointer will be incremented by 1 (01+1=10 in binary), and the pointer difference will be incremented by 1 (011+1 = 100 in binary). The FIFO has now 4 values that were not read yet. 4 is the depth of the FIFO memory. This means that the FIFO is full. No more data can be written. One or more words need to be read before anymore data is accepted. The pointer difference register will be always wider by 1 bit compared to the read and write pointer registers.

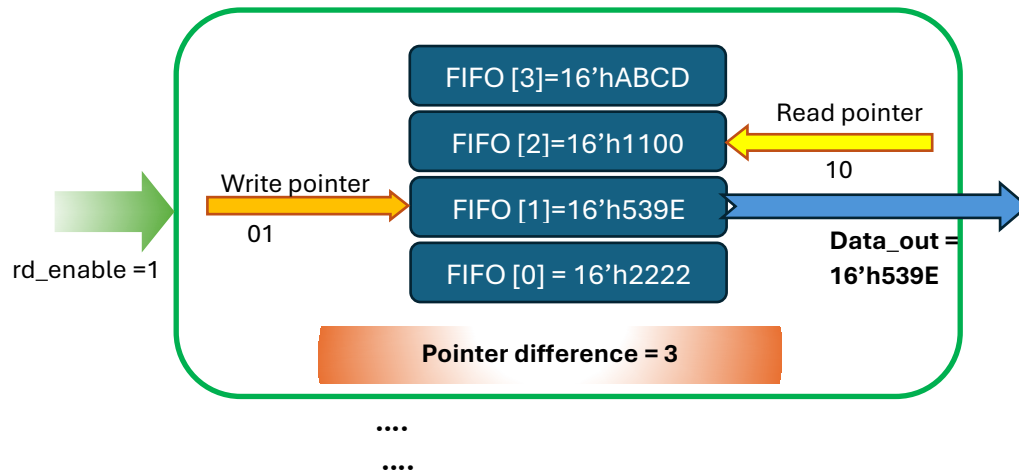

If the read enable is activated, then the data content saved in the memory location pointed at by the read pointer will be sent to the output data port. Then the Read pointer will be incremented by 1 (01+1=10 in binary). The pointer difference will be decremented by 1 (100 - 1 = 011 in binary) This indicates that there is exactly 3 data saved in the FIFO that was written and not read yet. Now the 16'h539E value saved in memory location 0 has been already, and it is fine to overwrite it! We will not delete it, but we can overwrite in when the memory space is needed for new incoming values. Now the FIFO is not completely full. Data can be accepted to be written

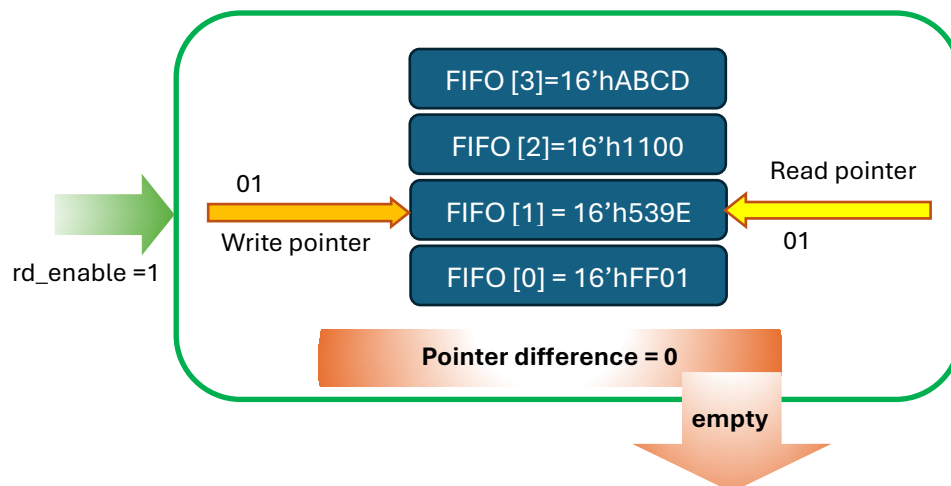

... If the rd_enable is active again over 3 more clock cycles, every time the data is read, the read pointer increments by 1 and the pointer difference decreases by 1. When the read pointer reaches the value on the write pointer (01) in this case, the pointer difference would have reached 0 indicating that there is no unread data in the FIFO anymore. The FIFO is empty.

```

module FIFO (    Data_out,          // Data path from FIFO
                empty,             // Flag asserted high for empty stack
                full,              // Flag asserted high for full stack
                Data_in,          // Data path into FIFO
                wr_enable,        // Input controlling a write to FIFO memory stack
                rd_enable,        // Input controlling a read to stack
                clk,              // clock
                rst               // reset
            );

parameter FIFO_width  = 16;      // width of stack and data paths
parameter FIFO_height = 4;      // height of stack (# of words)
parameter ptr_width   = 2;      // width of read and write pointers to address the FIFO words

output reg [FIFO_width-1 : 0] Data_out;
output      empty, full;
input [FIFO_width-1 : 0] Data_in;
input clk, rst;
input wr_enable, rd_enable;

// Pointers for reading and writing
reg [ptr_width-1 : 0] read_ptr, write_ptr;
reg [ptr_width : 0] ptr_diff;

// Memory FIFO registers
reg [FIFO_width-1 : 0] FIFO_Mem [FIFO_height-1 : 0]; // memory array

// empty and full flags
assign empty = (ptr_diff == 0) ? 1'b1 : 1'b0;
assign full  = (ptr_diff == FIFO_height) ? 1'b1 : 1'b0;

always @ (posedge clk or posedge rst)
begin
    if (rst) begin
        Data_out    <= 0;
        read_ptr    <= 0;
        write_ptr   <= 0;
        ptr_diff    <= 0;
    end
    else if ( (rd_enable) && (!empty) ) // read request and FIFO not empty
        begin
            Data_out    <= FIFO_Mem [read_ptr];
            read_ptr    <= read_ptr + 1;
            ptr_diff    <= ptr_diff - 1;
        end
    else if ( (wr_enable) && (!full) ) // write request and FIFO not full
        begin
            FIFO_Mem [write_ptr] <= Data_in;
            write_ptr    <= write_ptr + 1;
            ptr_diff    <= ptr_diff + 1;
        end
    end
endmodule

```



```

module FIFO_tb ();
    parameter FIFO_width = 16;           // width of stack and data paths
    parameter FIFO_height = 4;           // height of stack (# of words)
    parameter ptr_width = 2;             // width of pointer to address stack

    wire [FIFO_width -1 : 0] Data_out;
    wire empty, full;
    reg [FIFO_width -1 : 0] Data_in;
    reg clk, rst;
    reg wr_enable, rd_enable;

    wire [FIFO_width-1: 0] fifo_0, fifo_1, fifo_2, fifo_3;

    FIFO UUT ( Data_out, empty, full, Data_in, wr_enable, rd_enable, clk, rst );

    assign fifo_0 = UUT.FIFO_Mem [0];
    assign fifo_1 = UUT.FIFO_Mem [1];
    assign fifo_2 = UUT.FIFO_Mem [2];
    assign fifo_3 = UUT.FIFO_Mem [3];


    initial
    begin
        clk = 0;
        rst = 1;
        rd_enable = 0;
        wr_enable = 0;
        Data_in = 16'h1111;
        #350 $stop;
    end

    initial
    begin forever
        #5 clk = ~clk;    end

    initial
    fork
        #40  rst      = 1'b0;
        #50  Data_in   = 16'hFF01;
        #60  rd_enable = 1'b1;
        #80  rd_enable = 1'b0;
        #100 wr_enable = 1'b1;
        #110 Data_in   = 16'h539E;
        #120 wr_enable = 1'b0;
        #130 rd_enable = 1'b1;
        #140 rd_enable = 1'b0;
        #150 Data_in   = 16'h1100;
        #160 wr_enable = 1'b1;
        #170 Data_in   = 16'hABCD;
        #180 Data_in   = 16'h2222;
        #200 Data_in   = 16'h5050;
        #240 wr_enable = 1'b0;
        #260 rd_enable = 1'b1;
    join

endmodule

```

 

If the FIFO is empty, a read enable signal will not result in accessing any memory value. When empty, the Data_out will keep its value.