

DataPath Controller - Design Example - NRZ to PAM8 Serial Code Line Conversion

Consider the following datapath module.

1. Draw the internal structure of the module showing the registers and explaining the idea of operation.
2. Design a controller module that would control the conversion from NRZ to PAM8. The top module providing access to the host should have a reset that would reset the output to zero and should have an enable input to start the conversion and transmission process.

If the module is disabled during the construction of one 3-bit symbol, the controller should ignore the request until the symbol is completed.

Draw a State Graph for the controller FSM.

3. Design the top module and sketch the block diagram for it.
4. Create a testbench that verifies the functionality of your design.

Bonus: Modify your designs (datapath and/or controller) to down-sample the symbol rate by 2.

This means that you would receive 3 bits to build one symbol and hold it while skipping the following three bits.

```
module PAM8_Datapath (data_out, data_in, clock, reset, start, load);
output [2:0] data_out;
input      data_in, clock, reset, start, load;
reg [2:0] shift_reg, out_reg;
assign data_out = out_reg;
always @ (posedge clock)
    if (reset) begin
        shift_reg <= 3'b0;
        out_reg <= 3'b0; end
    else if (start) begin
        shift_reg <= {data_in, shift_reg[1:0]};
        out_reg <= 3'b0; end
    else if (load) begin
        shift_reg <= {data_in, shift_reg[2:1]};
        out_reg <= shift_reg; end
    else
        shift_reg <= {data_in, shift_reg[2:1]};
endmodule
```

```

module PAM8_Datapath_controller (data_in, data_out, reset, clock, enable);
input      data_in, reset, clock, enable;
output [2:0] data_out;

wire start, load;

PAM8_Datapath m1 (data_out, data_in, clock, reset, start, load);
PAM8_Controller m2 (start, load, enable, reset, clock);

endmodule

```

```

module PAM8_Controller (start, load, enable, reset, clock);

output reg start, load;
input enable, reset, clock;

reg [2:0] state, next_state;

parameter idle = 3'b000;
parameter starting = 3'b100;
parameter shift1 = 3'b001;
parameter shift2 = 3'b010;
parameter loading = 3'b011;

always @ (posedge clock)
if (reset) state <= idle;
else state <= next_state;

always @ *
case (state)
idle : begin
start = 1'b0;
load = 1'b0;
if (enable) next_state = starting;
else next_state = idle; end
starting : begin
start = 1'b1; // The LSB of the first symbol is loaded,
load = 1'b0; // the output remains 0.
next_state = shift1; end
shift1 : begin
start = 1'b0; // The 2nd bit is received
load = 1'b0;
next_state = shift2; end
shift2 : begin
start = 1'b0; // The MSB is received
load = 1'b0;
next_state = loading; end
loading : begin // The symbol is loaded to the output
start = 1'b0; // and the next LSB is loaded
load = 1'b1;
if(enable) next_state = shift1;
else next_state = idle; end
endcase
endmodule

```

```

module PAM8_tb ();

reg clock, reset, enable;
reg data_in;

wire [2:0] data_out;

reg [2:0] data_counter;

PAM8_Datapath_controller UUT (data_in, data_out, reset, clock, enable);

initial
begin
clock      = 1'b0;
reset      = 1'b1;
enable     = 1'b0;
data_in    = 1'b0;
end

always
#10 clock = ~clock;


initial
begin
#20 data_counter = 3'b101;
forever
#60 data_counter = data_counter + 1'b1;
end

always
begin
#20 data_in = data_counter [0];
#20 data_in = data_counter [1];
#20 data_in = data_counter [2];
end

initial
begin
#40 reset  = 1'b0;
#80 enable = 1'b1;
#180 enable = 1'b0;
#240 enable = 1'b1;
end

endmodule

```


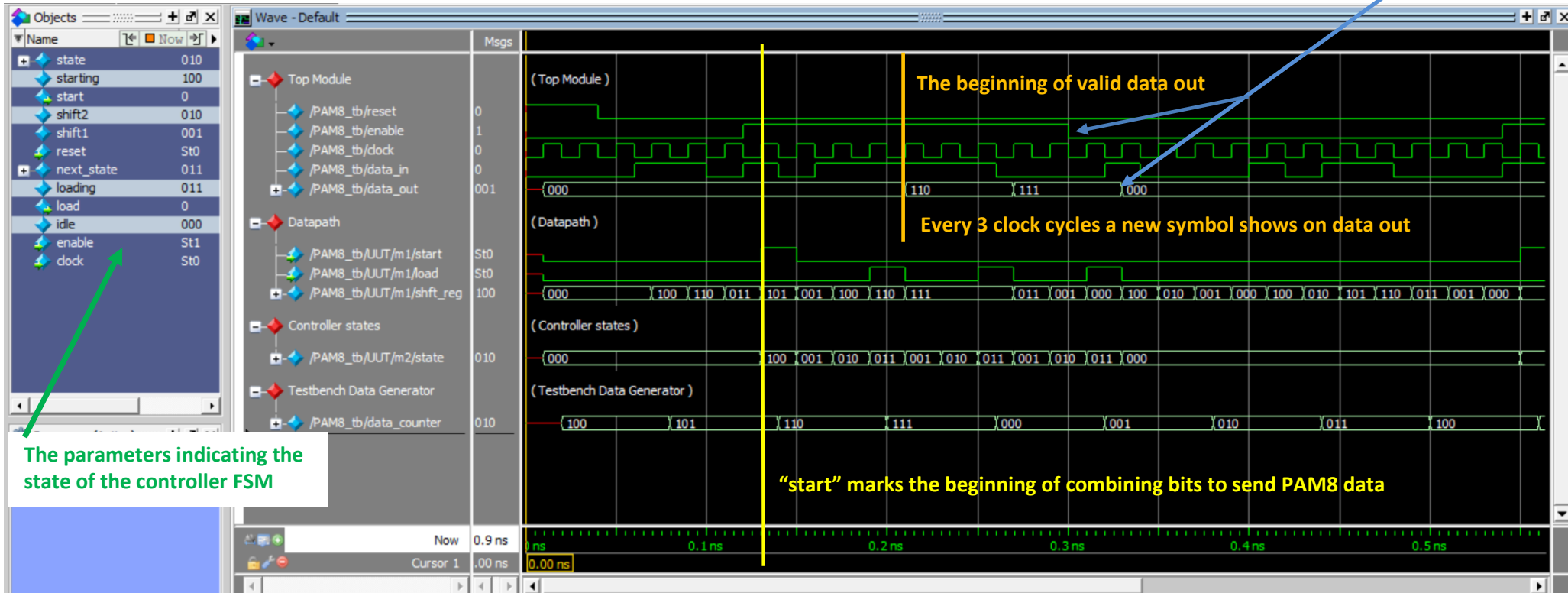


Although the enable signal went low, the module completed 3 clock cycles to finish building the started symbol.



The parameters indicating the state of the controller FSM

When the reset is active, the output and the shift register are both equal to zero. The reset has direct control over the datapath of the PAM8 module. When the reset is deactivated, while the enable is zero, the datapath load the data_in to the MSB of the shift register and load the data in the shift register to the right. The output register remains unchanged, and holds its value. The output register would only update with the value passed from the shift register when it receives a "load" command from the controller.

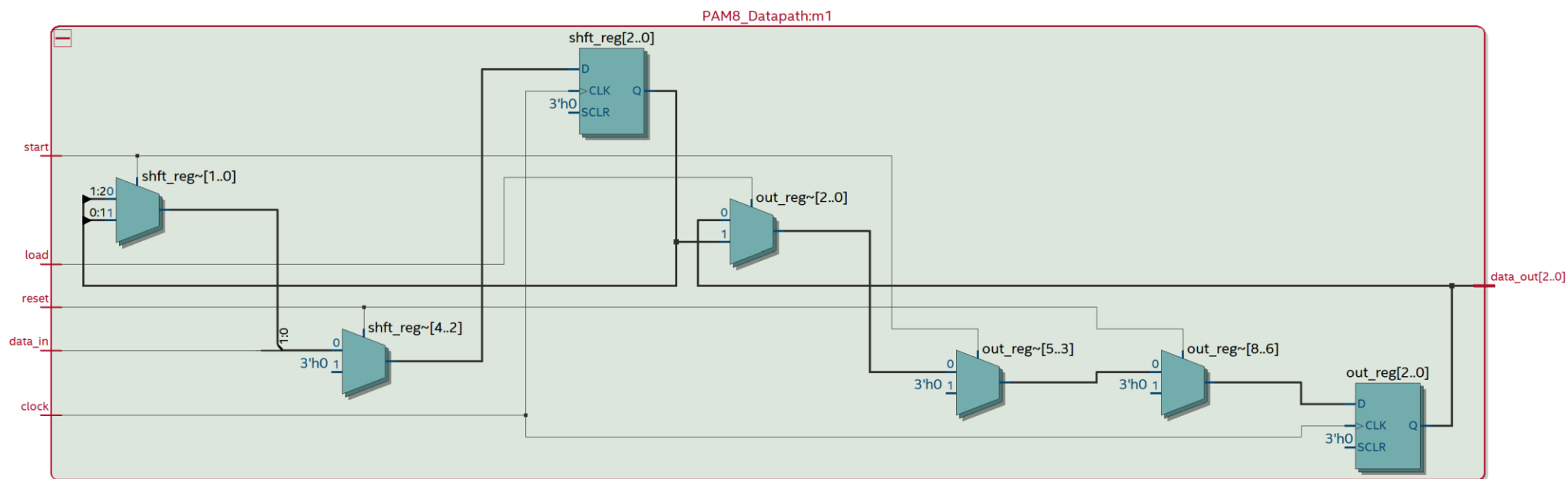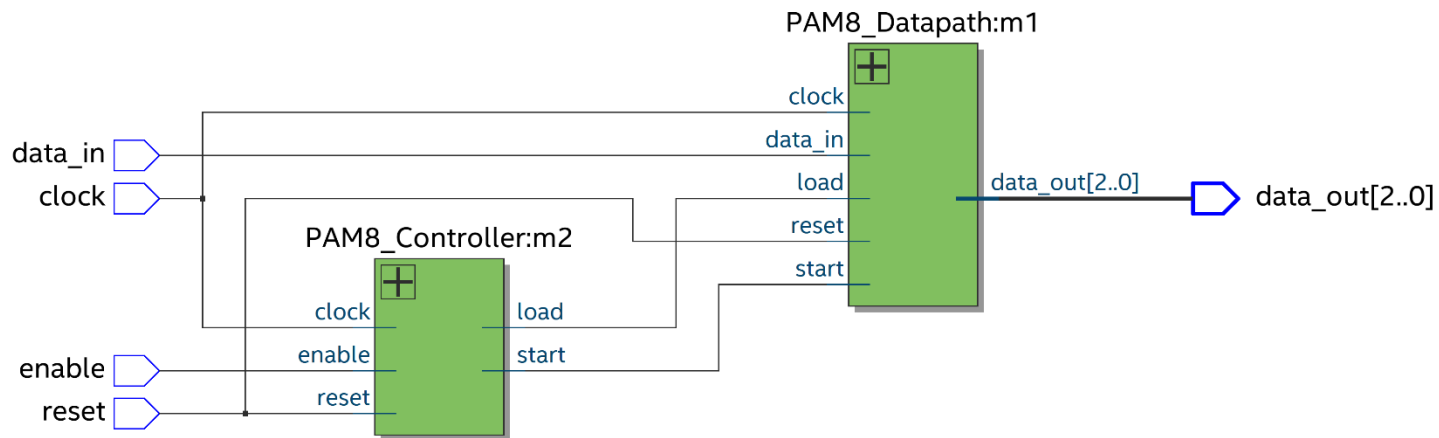At the first positive clock edge, that has the reset inactive and the enable active, the FSM of the controller exits the idle state and enters the "starting" state, where the "start" signal is set to high and the data_in is copied to the MSB of the shift register, while holding the old value of the output register.



PAM8_Controller:m2

 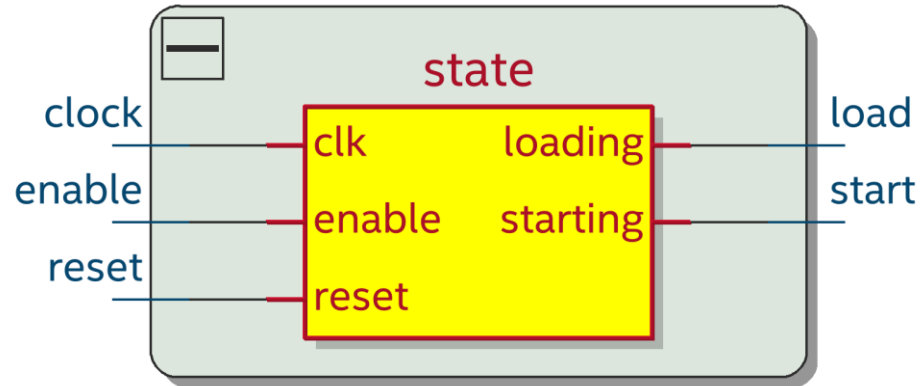

Bonus Question:

```
/*-----
Bonus Question:
-----*/
Modify your designs (datapath and/or controller) to down-sample the symbol rate by 2.
This means that you would receive 3 bits to build one symbol and hold it while skipping the
following three bits.
-----*/

module PAM8_Datapath_controller_Bonus (data_in, data_out, reset, clock, enable);
input    data_in, reset, clock, enable;
output [2:0] data_out;
wire start, load;
PAM8_Datapath_Bonus  m1  (data_out, data_in, clock, reset, start, load, hold);
PAM8_Controller_Bonus m2  (start, load, enable, reset, clock, hold);
endmodule

module PAM8_Datapath_Bonus  (data_out, data_in, clock, reset, start, load, hold);
output [2:0] data_out;
input    data_in, clock, reset, start, load;
input    hold;
reg [2:0] shft_reg, out_reg;
assign data_out = out_reg;
always @ (posedge clock)
    if (reset) begin
        shft_reg <= 3'b0;
        out_reg  <= 3'b0; end
    else if (start) begin
        shft_reg <= {data_in, shft_reg[1:0]};
        out_reg  <= 3'b0; end
    else if (load) begin
        shft_reg <= {data_in, shft_reg[2:1]};
        out_reg  <= shft_reg; end
    else if (hold) begin
        out_reg  <= out_reg;
        shft_reg <= 3'b0; end
    else
        shft_reg <= {data_in, shft_reg[2:1]};
endmodule

module PAM8_Controller_Bonus (start, load, enable, reset, clock, hold);
output reg start, load, hold;
input    enable, reset, clock;
reg [2:0] state, next_state;
parameter idle      = 3'b000;
parameter starting  = 3'b100;
parameter shift1    = 3'b001;
parameter shift2    = 3'b010;
parameter loading   = 3'b011;
parameter skip1     = 3'b111;
parameter skip2     = 3'b110;
parameter skip3     = 3'b101;
always @ (posedge clock)
    if (reset) state <= idle;
    else state <= next_state;
```

```

always @ *

begin
start = 1'b0;
load  = 1'b0;
hold  = 1'b0;

case (state)
idle   : begin
        if (enable) next_state = starting;
        else next_state = idle;      end
starting : begin
        start = 1'b1;                // The LSB of the first symbol is loaded,
        next_state = shift1;         end
shift1   : next_state = shift2;
shift2   : next_state = loading;
loading  : begin                        // The symbol is loaded to the output
        load = 1'b1;
        if(enable) next_state = skip1;
        else next_state = idle;      end
skip1    : begin
        hold = 1'b1;
        next_state = skip2; end
skip2    : begin
        hold = 1'b1;
        next_state = skip3; end
skip3    : begin
        hold = 1'b1;
        if(enable) next_state = shift1;
        else next_state = idle;      end
default  : next_state = idle;

        endcase
end
endmodule

module PAM8_Bonus_tb ();
reg clock, reset, enable;
reg data_in;

wire [2:0] data_out;
reg [2:0] data_counter;

PAM8_Datapath_controller_Bonus UUT (data_in, data_out, reset, clock, enable);

initial
begin
clock      = 1'b0;
reset      = 1'b1;
enable     = 1'b0;
data_in    = 1'b0;
end

always
#10 clock = ~clock;

initial
begin
#20 data_counter = 3'b101;
forever
#60 data_counter = data_counter + 1'b1;
end

always
begin
#20 data_in = data_counter [0];
#20 data_in = data_counter [1];
#20 data_in = data_counter [2];
end

initial
begin
#40 reset = 1'b0;
#80 enable = 1'b1;
#180 enable = 1'b0;
#240 enable = 1'b1;
end
endmodule

```