

## A few points to think about:

PAM4 combines two NRZ bits, which means 4 Manchester bits.

Manchester 0101 = 00 NRZ = 0 PAM4

Manchester 0110 = 01 NRZ = 1 PAM4

Manchester 1001 = 10 NRZ = 2 PAM4

Manchester 1010 = 11 NRZ = 3 PAM4

## This means that:


- PAM4 will change its value every 4 clock cycles from the Manchester clk.
- Some sequences are not possible if we go from Manchester to PAM4. (For example, 1111 is not possible, 0000 is not possible.. Only the ones given above are possible) So, some states will only have one outward arrow representing only one possible input. (either 0 or 1). If I start with a 0, we are 100% sure the next bit will be 1; if we start the sequence with 1, then 100% the following bit will be a 0.
- The PAM4 level output is always given using two output bits to give you the 4
  possible levels.

In the simulation of the Manchester to PAM4 code line converter, the PAM4 value will be delayed by 4 clock cycles (not perfectly aligned as in the timing diagram shared) because we need to wait for the serially incoming bit to figure out what the PAM4 level will be.

We did a 4Bit sequence detector as one of the examples for the FSM. We had one output that went high when a sequence was detected and was zero otherwise. The main difference here is that we need to latch the PAM4 output over 4 clock cycles, until we receive the next 4 bits of Manchester sequence. This will increase the number of states that we need significantly. (36 states)

This will require that we develop a strategy to keep our code readable, organized, parametrized to be able to troubleshoot and debug as needed.

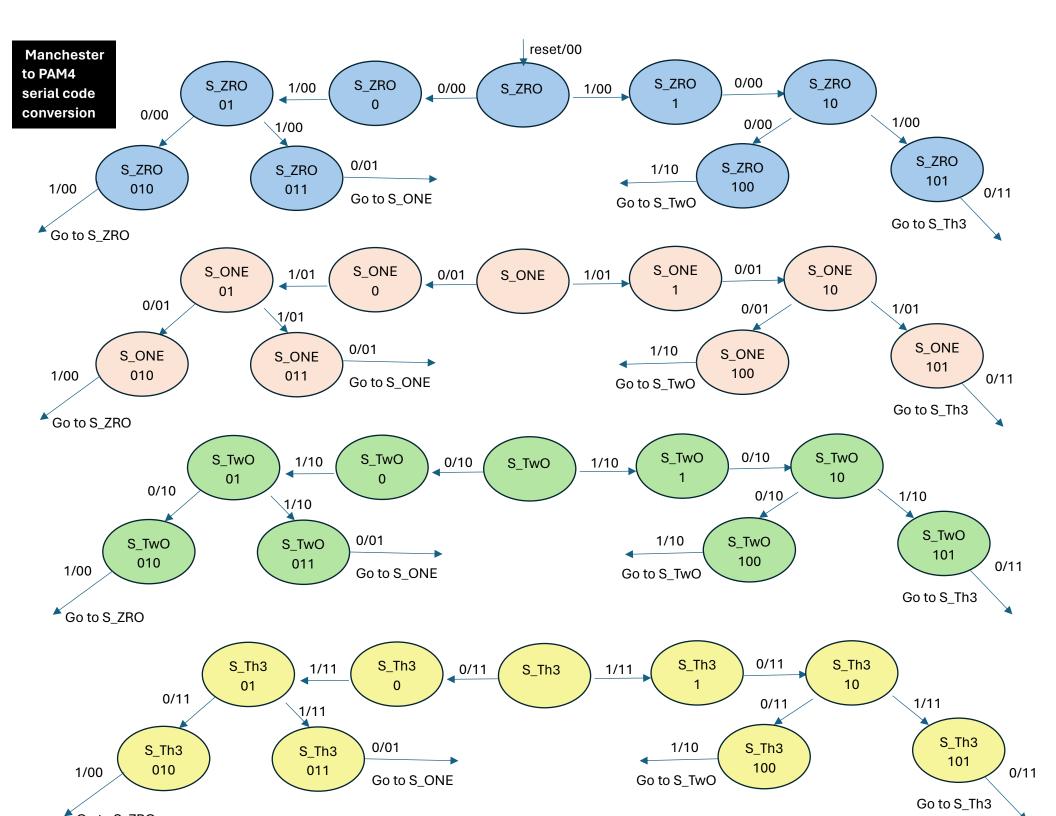We will learn later how we can use registers and split the design into datapath and controller to have an efficient converter design with serial input.



For assigning numbers to the states, you can choose numbers that make it easy to track and verify in the simulation results. For example:

// parameter state\_name = 8'b\_PAM4level\_ManchesterCodeReceived

parameter S\_TwO = 8'b0010\_1001;

```
parameter S ZRO
                         = 8'b 0000 0101;
                                            // HEX 05 the last bit of the Manchester 0101 has
                                                         been received and the output is at 00 level,
                                            // HEX 00 the first bit of a new Manchester code is 0
            S ZRO xxx0 = 8'b 0000 0000;
                                                         and the last output is latched at 00 level.
           S ZRO xx01 = 8'b 0000 0001; // HEX 01 Two bits of a new Manchester code are 01
                                                         and the output is latched at 00 level.
            S ZRO \times 010 = 8'b 0000 \ 0010;
                                           // HEX 02 3 bits of a new Manchester code are 010
                                                         and the output is latched at 00 level.
parameter S ZRO x011 = 8'b 0000 0011; // HEX 03 3 bits of a new Manchester code are 011
                                                         and the output is latched at 00 level.
                                             // HEX 0F the first bit of a new Manchester code is 1
           S_{ZRO_{xxx1}} = 8'b_{0000_{1111}};
parameter
                                                          and the output is latched at 00 level.
           S_{ZRO_{XX10}} = 8'b_{0000_{1110}};
                                             // HEX 0E Two bits of a new Manchester code is 10
parameter
                                             //
                                                          and the output is latched at 00 level.
parameter
            S_ZRO_x101 = 8'b_0000_1101;
                                             // HEX 0D 3 bits of a new Manchester code is 101
                                                          and the output is latched at 00 level.
parameter S_ZRO_x100 = 8'b_0000_1100;
                                             // HEX 0C 3 bits of a new Manchester code is 100
                                             //
                                                          and the output is latched at 00 level.
parameter S_ONE
                         = 8'b_0000_0110;
                                            // HEX 16 the last bit of the Manchester 0101 has
                                                         been received and the output is at 01 level,
parameter
           S_ONE_xxx0 = 8'b_0001_0000;
                                            // HEX 10 the first bit of a new Manchester code is 0
                                                         and the last output is latched at 01 level.
           S_ONE_xx01 = 8'b_0001_0001; // HEX_11 Two bits of a new Manchester code are 01
parameter
                                                         and the output is latched at 01 level.
           S_ONE_x010 = 8'b_0001_0010;
                                            // HEX 12 3 bits of a new Manchester code are 010
parameter
                                                         and the output is latched at 01 level.
parameter
           S_ONE_x011 = 8'b_0001_0011; // HEX 13 3 bits of a new Manchester code are 011
                                                         and the output is latched at 01 level.
                                             // HEX 1F the first bit of a new Manchester code is 1
parameter
           S_ONE_xxx1 = 8'b_0001_1111;
                                             //
                                                          and the output is latched at 01 level.
           S_ONE_xx10 = 8'b_0001_1110;
                                             // HEX 1E Two bits of a new Manchester code is 10
parameter
                                             //
                                                          and the output is latched at 01 level.
parameter S_ONE_x101 = 8'b_0001_1101;
                                             // HEX 1D 3 bits of a new Manchester code is 101
                                                          and the output is latched at 01 level.
parameter S_ONE_x100 = 8'b_0001_1100;
                                             // HEX 1C 3 bits of a new Manchester code is 100
                                             //
                                                          and the output is latched at 01 level.
```

parameter S\_Th3 = 8'b0011\_1010;

... and so on