

```
1 // ee417 lesson 9 Assignment 1 L9A1
2 // Name: Ron Kalin, Date: 07-10-24 Group: Kalin/Jammeh
3 // Design: moving average FIR filter of overlapping windows of 4 input samples
4 // FIR order will be a power of 2, parameterized with word_size
5 // top level module
6 module moving_average_filter #(parameter word_size=8, order=4, n=2)(
7     output reg [2*word_size-1:0] filtered_sample,
8     input [word_size-1:0] sample_in,
9     input enable, clk, reset
10 );
11 // Coefficient values for a 4-tap moving average filter
12 //reg [word_size-1:0] coeff [0:order] = {16'h1000, 16'h1000, 16'h1000, 16'h1000};
13 reg [word_size-1:0] coeff0 = 4'd1; //coefficients of one were selected
14 reg [word_size-1:0] coeff1 = 4'd1; //because for moving average they aren't needed
15 reg [word_size-1:0] coeff2 = 4'd1;
16 reg [word_size-1:0] coeff3 = 4'd1;
17 reg [word_size-1:0] tap_outputs [0:3];
18
19 // Circular buffer to store input samples
20 reg [word_size-1:0] buffer0, buffer1, buffer2, buffer3;
21 reg [word_size-1:0] buffer [0:order-1];
22 always @(posedge clk) begin
23     if (reset || ~enable) begin
24         buffer0 = 0;
25         buffer1 = 0;
26         buffer2 = 0;
27         buffer3 = 0;
28     end else if (enable) begin
29         buffer3 = buffer2;
30         buffer2 = buffer1;
31         buffer1 = buffer0;
32         buffer0 = sample_in;
33     end
34     // Multipliers and accumulator
35     tap_outputs[0] = buffer0 * coeff0; //coeff[0];
36     tap_outputs[1] = buffer1 * coeff1; //coeff[1];
37     tap_outputs[2] = buffer2 * coeff2; //coeff[2];
38     tap_outputs[3] = buffer3 * coeff3; //coeff[3];
39
40     filtered_sample = (buffer0 + buffer1 + buffer2 + buffer3); // >> 2;
41     //filtered_sample = buffer[0] + buffer[1] + buffer[2] + buffer[3];
42     //filtered_sample <= (tap_outputs[0] + tap_outputs[1] + tap_outputs[2] + tap_outputs[3])
43     // Right shift by 2 bits to approximate division by 4
44     filtered_sample = (filtered_sample >> n); //shift n places to divide by 2^n
45     //shift n places requires 2^n samples (buffers and coefficients)
46 end
47 endmodule
48
49
```