

FIR Filter Design

PROJECT 1 CE6325 VLSI DESIGN: VERILOG HDL

LAMIN JAMMEH NET-ID: DAL852207

Project Description:

A Finite Impulse Response (FIR) filter was designed with pre-determined specifications. The filter order, and the Data_in size were parameterized to allow the design to be scalable. The filter takes in a sample input, processes the sample input and passes it to an output register

Design Specifications

Filter order: 5

Filter coefficients: [7, 8, 9, 12, 4]

Data_in size: 4

Data_out size: 16

Data flow of the design

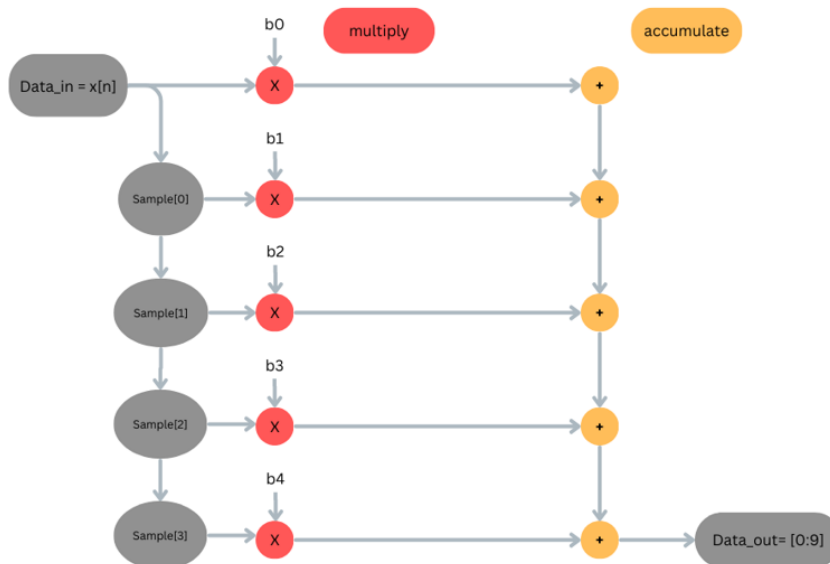


Figure1: Finite Impulse Response (FIR) Filter using Multiply and Accumulate

Design Netlist

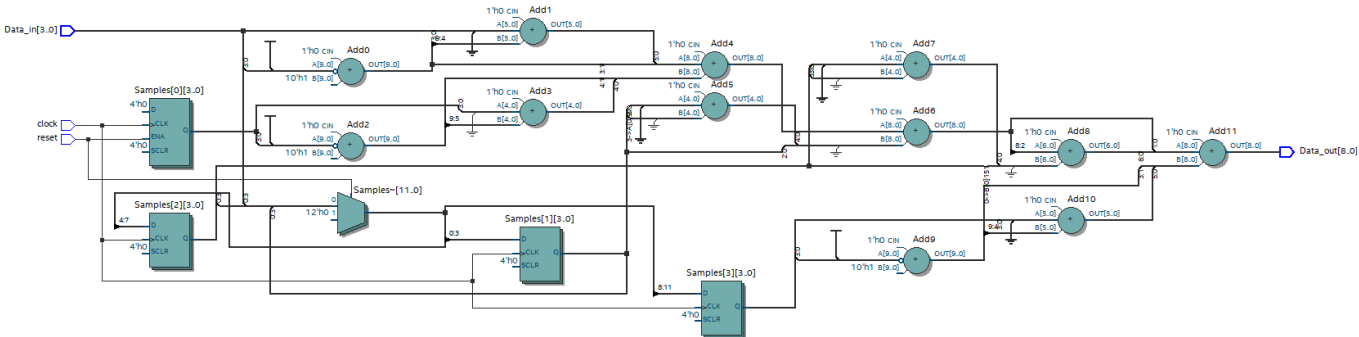


Figure 2: Netlist for the FIR filter

Testbench Process Flow

 


Figure 3: Shows the Testbench Process flow

Table 1 showing Filter out with when Data_in = decimal (6)

Data_in		Sample[k]	Filter Coefficient (bn)		bn * Sample[k]		Acc @ filter stage
6	Data_in →	6	7	bn * Sample[k] →	42	acc0	42
		6	8		48	acc1	90
		6	9		54	acc2	144
		6	12		72	acc3	216
		6	4		24	Data_out/acc4	240

Table 1 shows that Data_in will go shift through all of Sample[k] when enough time is allowed before changing the value at the input. The value in each register of Sample[k] is multiplied by the filter

coefficient (b_n). The values of the multiply is accumulated or summed to form the output of the filter.

$$Mux = b_n * Sample[k]$$

$$acc = \sum_n^0 Mux_n$$

Register Transistor Logic (RTL) Simulation Result

Table3 shows the observed values from the simulation results

```
# run -all
# Time: 0 | Data_in: 0 | Data_out: x | reset: 1
# Time: 5 | Data_in: 0 | Data_out: 0 | reset: 1
# Time: 10 | Data_in: 0 | Data_out: 0 | reset: 0
# Time: 110 | Data_in: 6 | Data_out: 0 | reset: 0
# Time: 115 | Data_in: 6 | Data_out: 42 | reset: 0
# Time: 125 | Data_in: 6 | Data_out: 90 | reset: 0
# Time: 135 | Data_in: 6 | Data_out: 144 | reset: 0
# Time: 145 | Data_in: 6 | Data_out: 216 | reset: 0
# Time: 155 | Data_in: 6 | Data_out: 240 | reset: 0
# Time: 210 | Data_in: 3 | Data_out: 240 | reset: 0
# Time: 215 | Data_in: 3 | Data_out: 219 | reset: 0
# Time: 225 | Data_in: 3 | Data_out: 195 | reset: 0
# Time: 235 | Data_in: 3 | Data_out: 168 | reset: 0
# Time: 245 | Data_in: 3 | Data_out: 132 | reset: 0
# Time: 255 | Data_in: 3 | Data_out: 120 | reset: 0
# Time: 310 | Data_in: 2 | Data_out: 120 | reset: 0
# Time: 315 | Data_in: 2 | Data_out: 113 | reset: 0
# Time: 325 | Data_in: 2 | Data_out: 105 | reset: 0
# Time: 335 | Data_in: 2 | Data_out: 96 | reset: 0
# Time: 345 | Data_in: 2 | Data_out: 84 | reset: 0
# Time: 355 | Data_in: 2 | Data_out: 80 | reset: 0
# Time: 410 | Data_in: 5 | Data_out: 80 | reset: 0
# Time: 415 | Data_in: 5 | Data_out: 101 | reset: 0
# Time: 420 | Data_in: 5 | Data_out: 101 | reset: 1
# Time: 425 | Data_in: 5 | Data_out: 0 | reset: 1
# Time: 430 | Data_in: 5 | Data_out: 0 | reset: 0
# Time: 435 | Data_in: 5 | Data_out: 35 | reset: 0
# Time: 445 | Data_in: 5 | Data_out: 75 | reset: 0
# Time: 455 | Data_in: 5 | Data_out: 120 | reset: 0
# Time: 465 | Data_in: 5 | Data_out: 180 | reset: 0
# Time: 475 | Data_in: 5 | Data_out: 200 | reset: 0
# Time: 530 | Data_in: 2 | Data_out: 200 | reset: 0
# Time: 535 | Data_in: 2 | Data_out: 179 | reset: 0
# Time: 545 | Data_in: 2 | Data_out: 155 | reset: 0
# Time: 555 | Data_in: 2 | Data_out: 128 | reset: 0
# Time: 565 | Data_in: 2 | Data_out: 92 | reset: 0
# Time: 575 | Data_in: 2 | Data_out: 80 | reset: 0
# Time: 630 | Data_in: 0 | Data_out: 80 | reset: 0
# Time: 635 | Data_in: 0 | Data_out: 66 | reset: 0
# Time: 645 | Data_in: 0 | Data_out: 50 | reset: 0
# Time: 655 | Data_in: 0 | Data_out: 32 | reset: 0
# Time: 665 | Data_in: 0 | Data_out: 8 | reset: 0
# Time: 675 | Data_in: 0 | Data_out: 0 | reset: 0
# Time: 730 | Data_in: 2 | Data_out: 0 | reset: 0
# Time: 735 | Data_in: 2 | Data_out: 14 | reset: 0
# Time: 745 | Data_in: 2 | Data_out: 30 | reset: 0
# Time: 755 | Data_in: 2 | Data_out: 48 | reset: 0
# Time: 765 | Data_in: 2 | Data_out: 72 | reset: 0
# Time: 775 | Data_in: 2 | Data_out: 80 | reset: 0
# Time: 830 | Data_in: 4 | Data_out: 80 | reset: 0
# Time: 835 | Data_in: 4 | Data_out: 94 | reset: 0
# Time: 845 | Data_in: 4 | Data_out: 110 | reset: 0
# Time: 855 | Data_in: 4 | Data_out: 128 | reset: 0
# Time: 865 | Data_in: 4 | Data_out: 152 | reset: 0
# Time: 875 | Data_in: 4 | Data_out: 160 | reset: 0
# ** Note: $stop : C:/Users/lmnm/OneDrive/Documents/Grad School/UTD/Fall 2024/EEDG 6325/Projects/Project 1/FIR_Filter_Project1_tb.v(66)
# Time: 930 ps Iteration: 0 Instance: /FIR_Filter_Project1_tb
```

When Data_in =6 Data_out=240 @ next rising clock after Data_in goes through all the filter taps or stages

@ reset = 1 Data_out = 0 since the Sample register is cleared @reset high. This happens @ next rising clock

Simulation Wave form

