

The simulation summary shows the following

- Output z1 is high after the S_reset is low, and when the present state=2 or b010
- Output z2 is high after the S_reset is low, and when the present state=4 or b100
 - After z2 is high z1 cannot occur until S_reset gets toggle high and then low