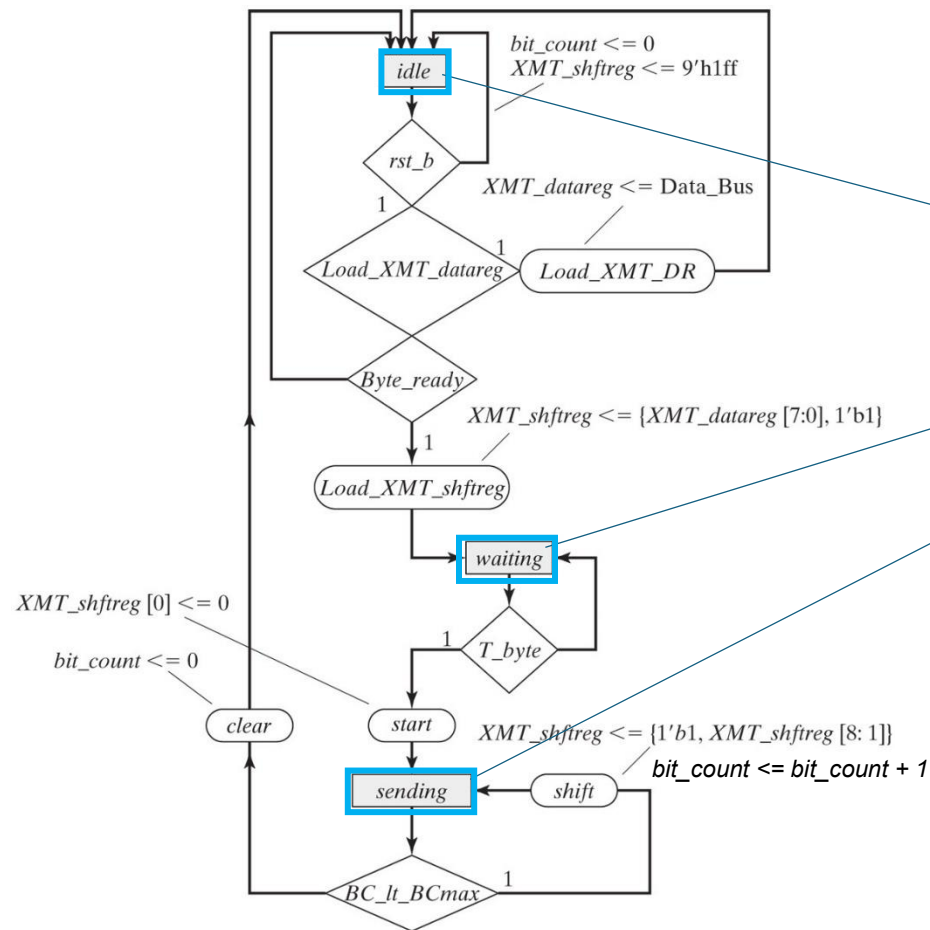


Explaining the ASMD (Algorithmic State Machine and DataPath) for the UART transmitter: **Controller States**




States of the controller are enclosed in the rectangular (shaded) box. The controller has 3 states: idle, waiting, and sending.

Note: Only the branch corresponding to a true decision is annotated at a decision diamond; signals that are de-asserted are not shown explicitly de-asserted. Conditional assertions are indicated by the name of the asserted signal.

Note: *BC_lt_BCmax* asserts if *Bit_count* < *word_size* + 1.

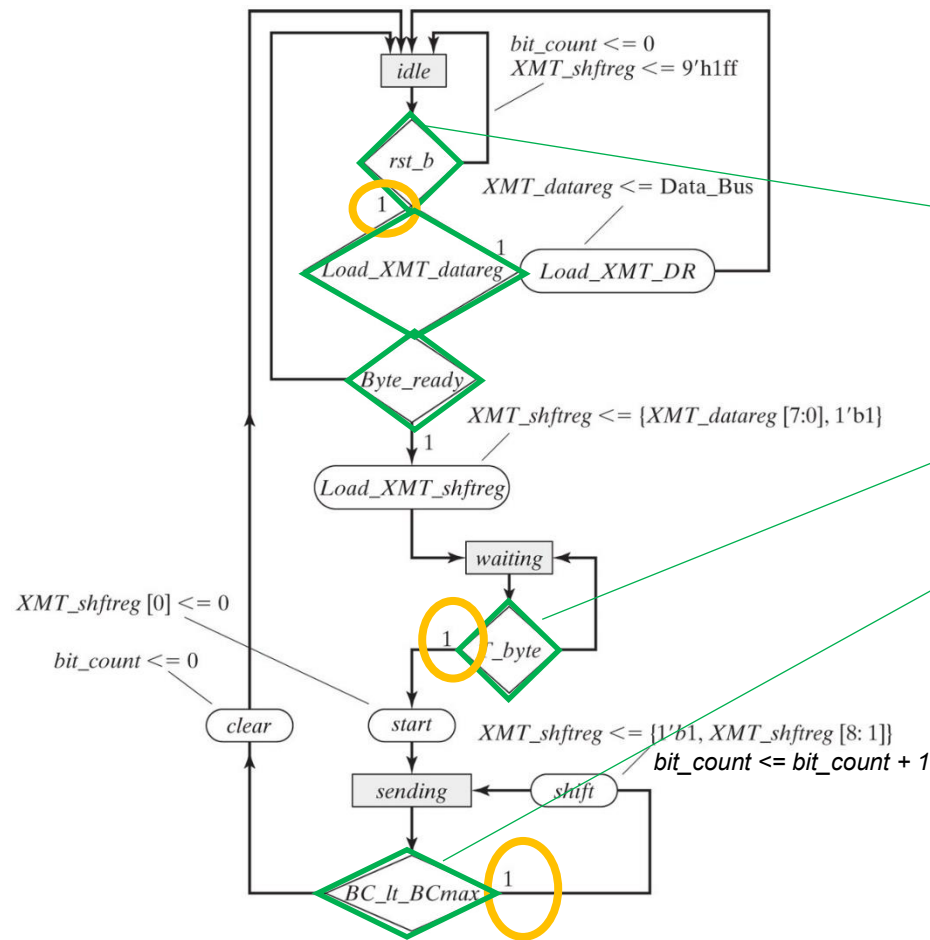Explaining the ASMD (Algorithmic State Machine and DataPath) for the UART transmitter: **Controller Inputs**




Diamond shapes are used for checking the value of a controller **input**. Controller inputs are always single bits signals, so they can be either '1' or '0'. Based on their logic value the transition arrow destination state and controller outputs are determined. The path followed in case the input is a logic '1' is annotated with a **1**. Otherwise the path has no label.

The inputs to the controller can be coming from the user as an overall input to the top module (Byte_ready), or they can be internal signals generated by the DataPath (BC_lt_BCMax).

Note: Only the branch corresponding to a true decision is annotated at a decision diamond; signals that are de-asserted are not shown explicitly de-asserted. Conditional assertions are indicated by the name of the asserted signal.

Note: BC_lt_BCmax asserts if $Bit_count < word_size + 1$.

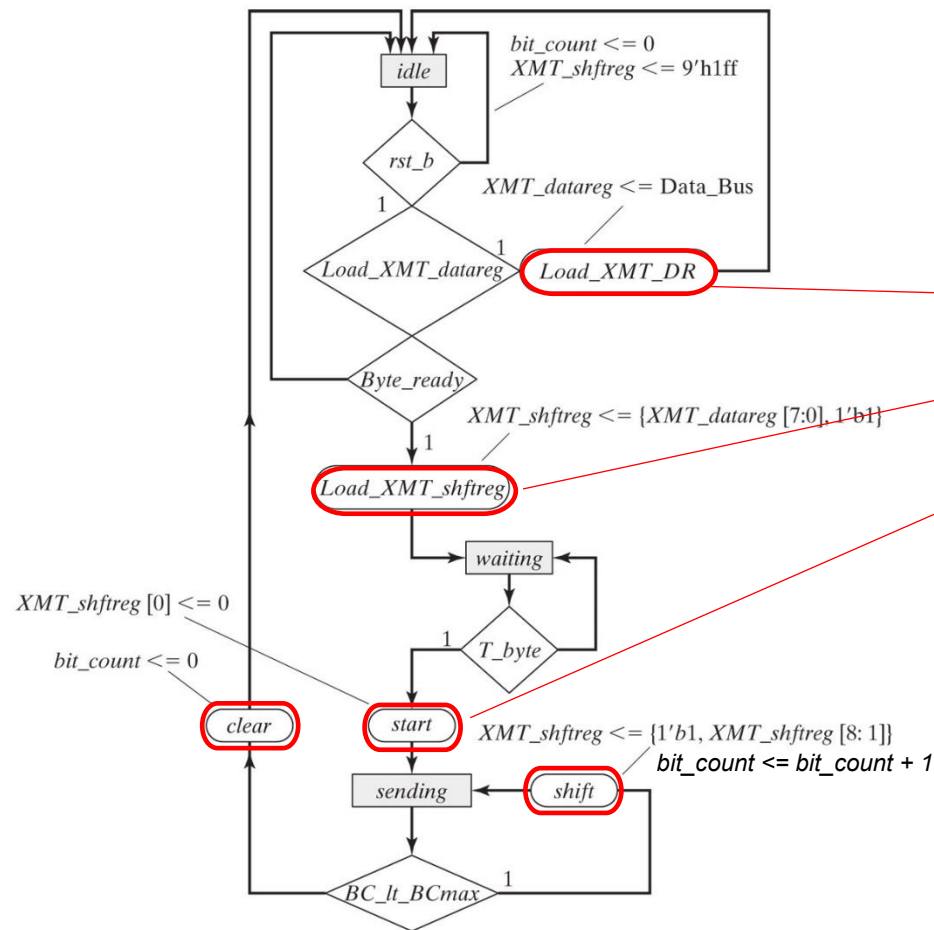Explaining the ASMD (Algorithmic State Machine and DataPath) for the UART transmitter: **Controller Outputs**



Controller outputs are single bit signals. They appear on the transition arrows if they will be set to a logic '1'.


They are enclosed in a rectangular shape with two rounded sides.

Output signals not featured on the transition line are just kept inactive (0 level).


Note: Only the branch corresponding to a true decision is annotated at a decision diamond; signals that are de-asserted are not shown explicitly de-asserted. Conditional assertions are indicated by the name of the asserted signal.

Note: *BC_lt_BCmax* asserts if *Bit_count* < *word_size* + 1.

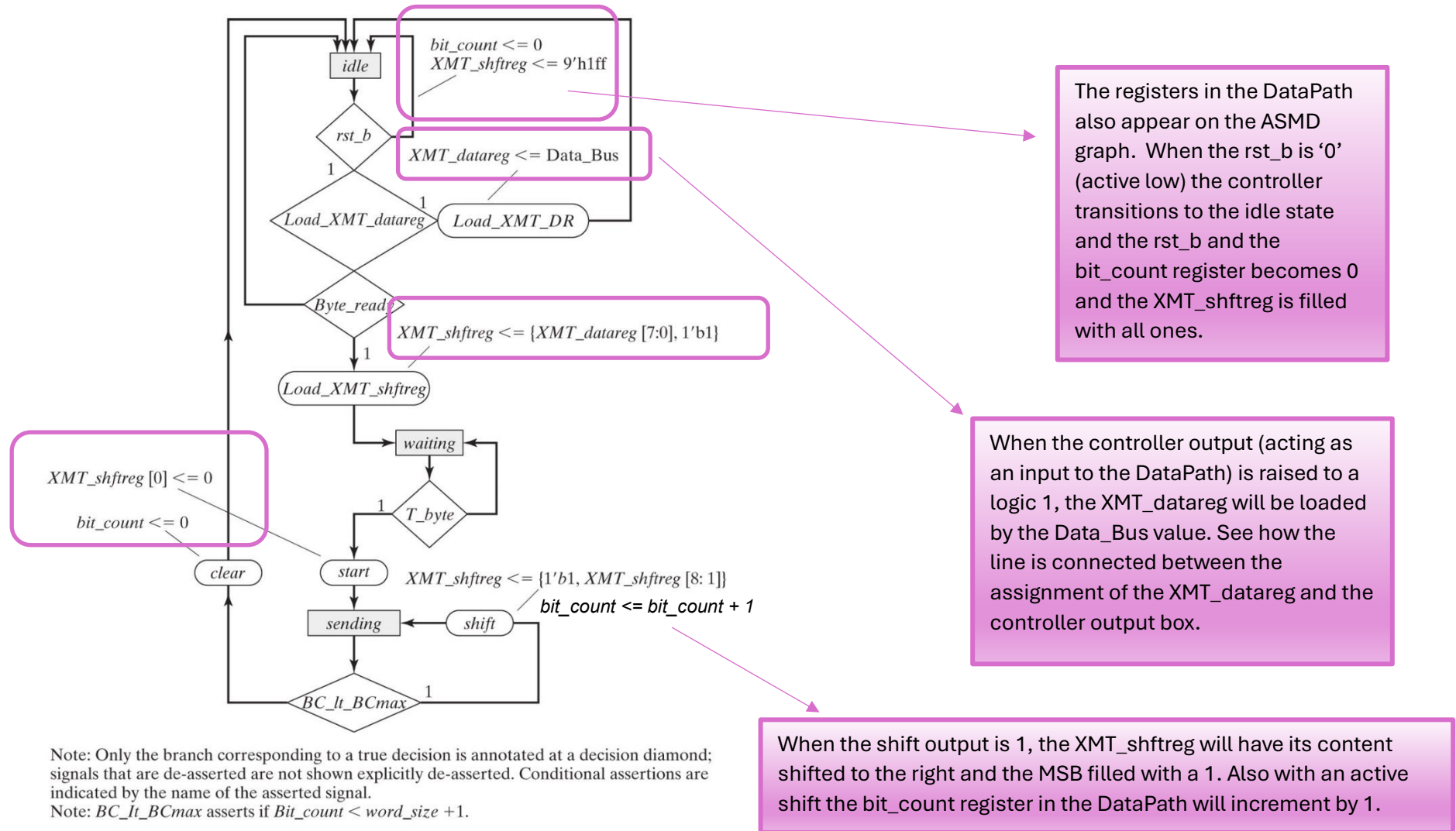Explaining the ASMD (Algorithmic State Machine and DataPath) for the UART transmitter: DataPath Registers



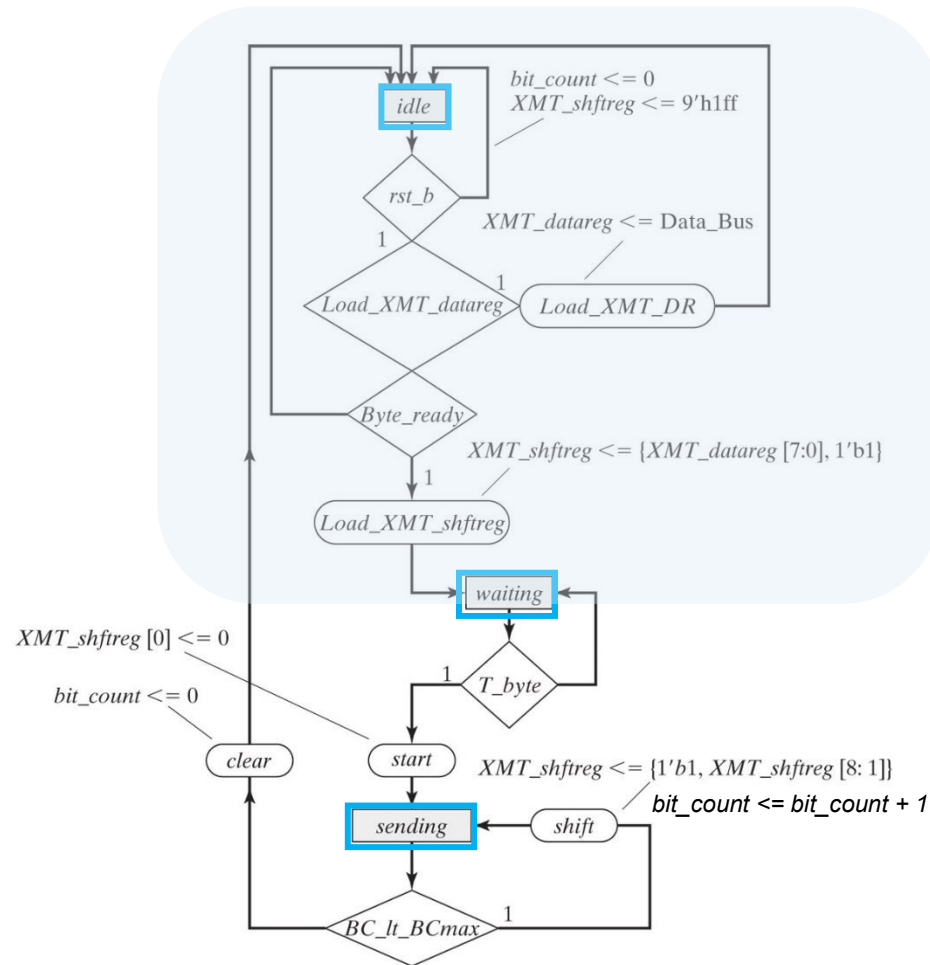
Explaining the ASMD (Algorithmic State Machine and DataPath) for the UART transmitter: **Generating the FSM**




Note: Only the branch corresponding to a true decision is annotated at a decision diamond; signals that are de-asserted are not shown explicitly de-asserted. Conditional assertions are indicated by the name of the asserted signal.

Note: BC_lt_BCmax asserts if $Bit_count < word_size + 1$.

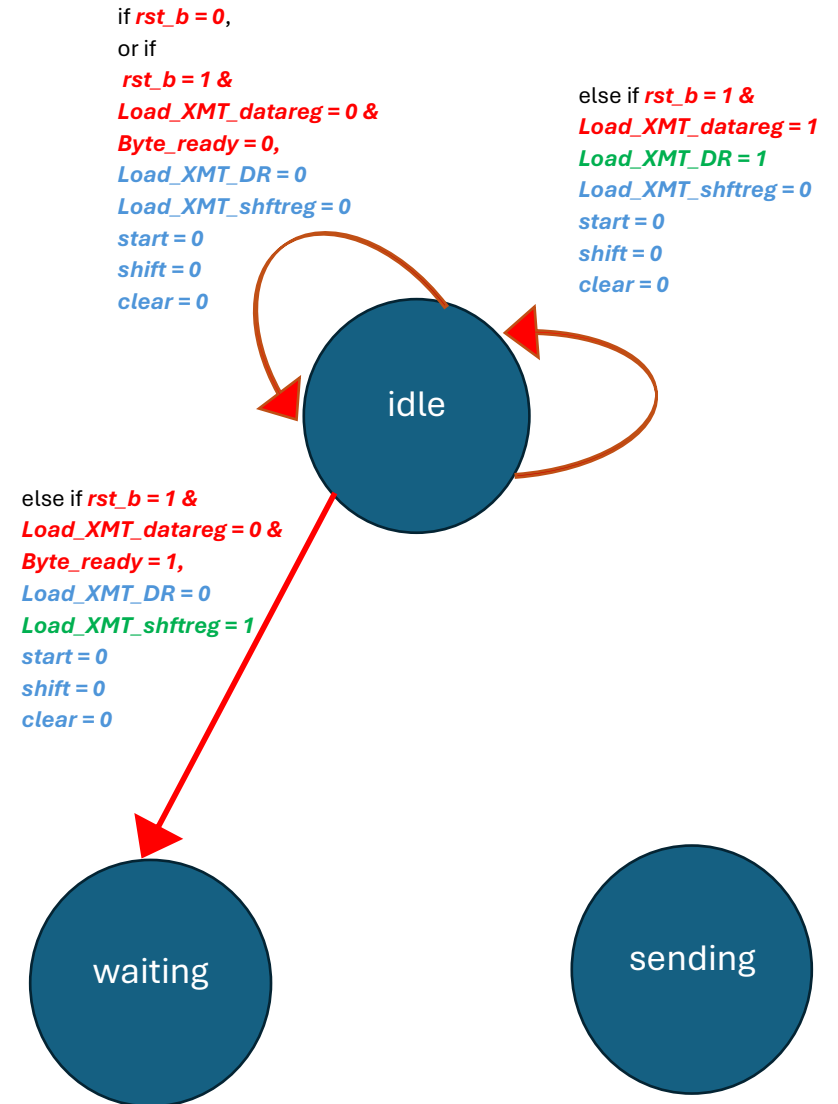Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall



 
Explaining the ASMD (Algorithmic State Machine and DataPath) for the UART transmitter: [Generating the FSM](#)




Note: Only the branch corresponding to a true decision is annotated at a decision diamond; signals that are de-asserted are not shown explicitly de-asserted. Conditional assertions are indicated by the name of the asserted signal.

Note: BC_lt_BCmax asserts if $Bit_count < word_size + 1$.

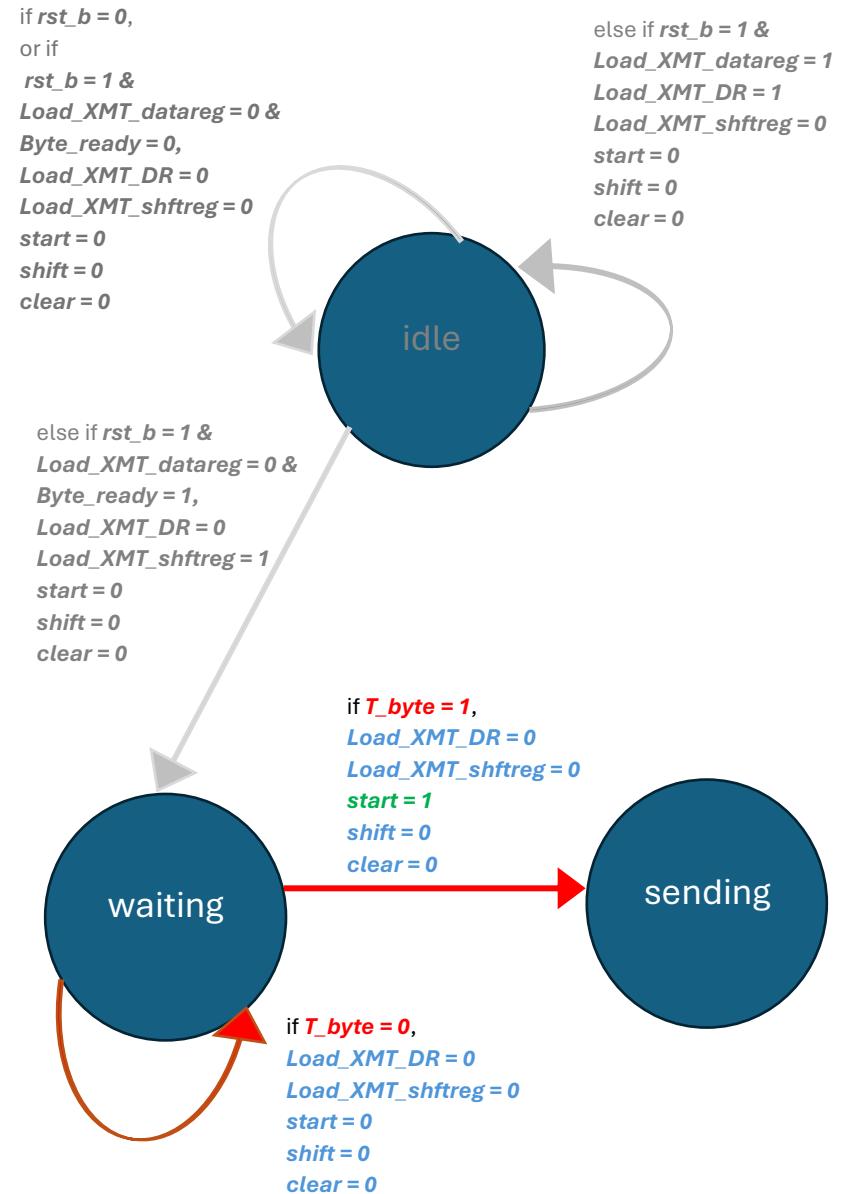Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall



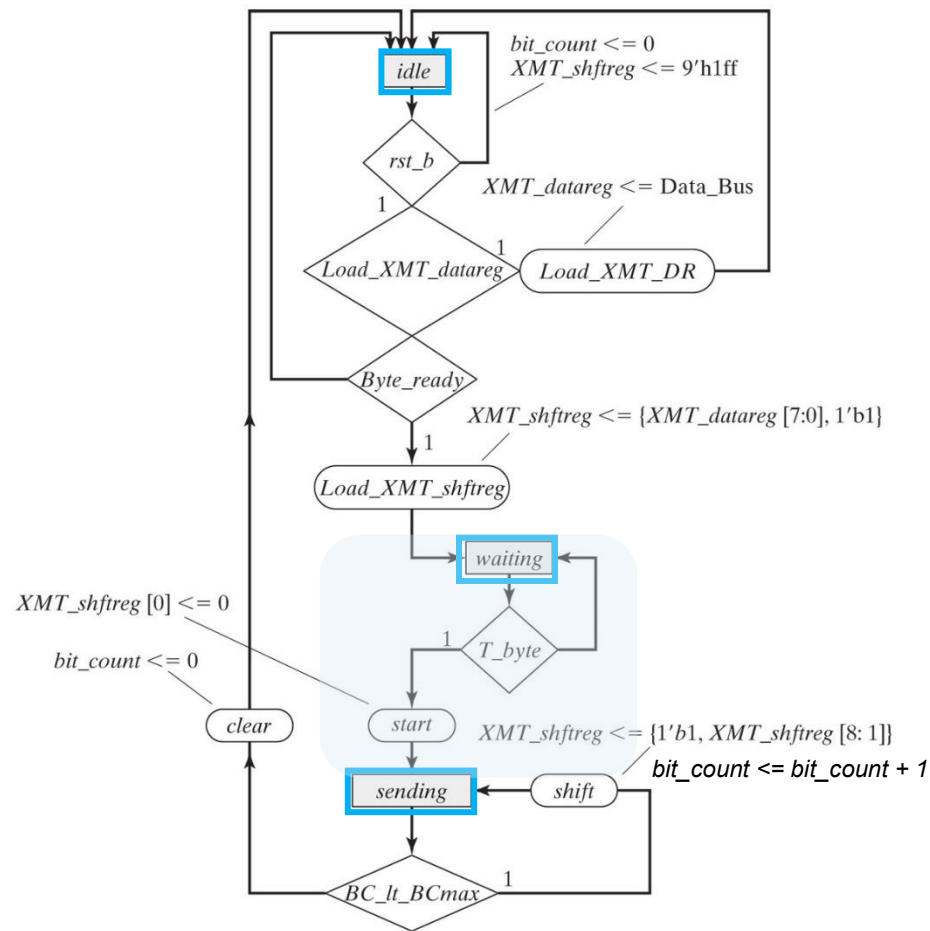Explaining the ASMD (Algorithmic State Machine and DataPath) for the UART transmitter: [Generating the FSM](#)



Note: Only the branch corresponding to a true decision is annotated at a decision diamond; signals that are de-asserted are not shown explicitly de-asserted. Conditional assertions are indicated by the name of the asserted signal.

Note: BC_lt_BCmax asserts if $Bit_count < word_size + 1$.

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


if $rst_b = 0$,
or if
 $rst_b = 1$ &
 $Load_XMT_datareg = 0$ &
 $Byte_ready = 0$,
 $Load_XMT_DR = 0$
 $Load_XMT_shftreg = 0$
 $start = 0$
 $shift = 0$
 $clear = 0$

else if $rst_b = 1$ &
 $Load_XMT_datareg = 1$
 $Load_XMT_DR = 1$
 $Load_XMT_shftreg = 0$
 $start = 0$
 $shift = 0$
 $clear = 0$


else if $rst_b = 1$ &
 $Load_XMT_datareg = 0$ &
 $Byte_ready = 1$,
 $Load_XMT_DR = 0$
 $Load_XMT_shftreg = 1$
 $start = 0$
 $shift = 0$
 $clear = 0$

if $T_byte = 1$,
 $Load_XMT_DR = 0$
 $Load_XMT_shftreg = 0$
 $start = 1$
 $shift = 0$
 $clear = 0$

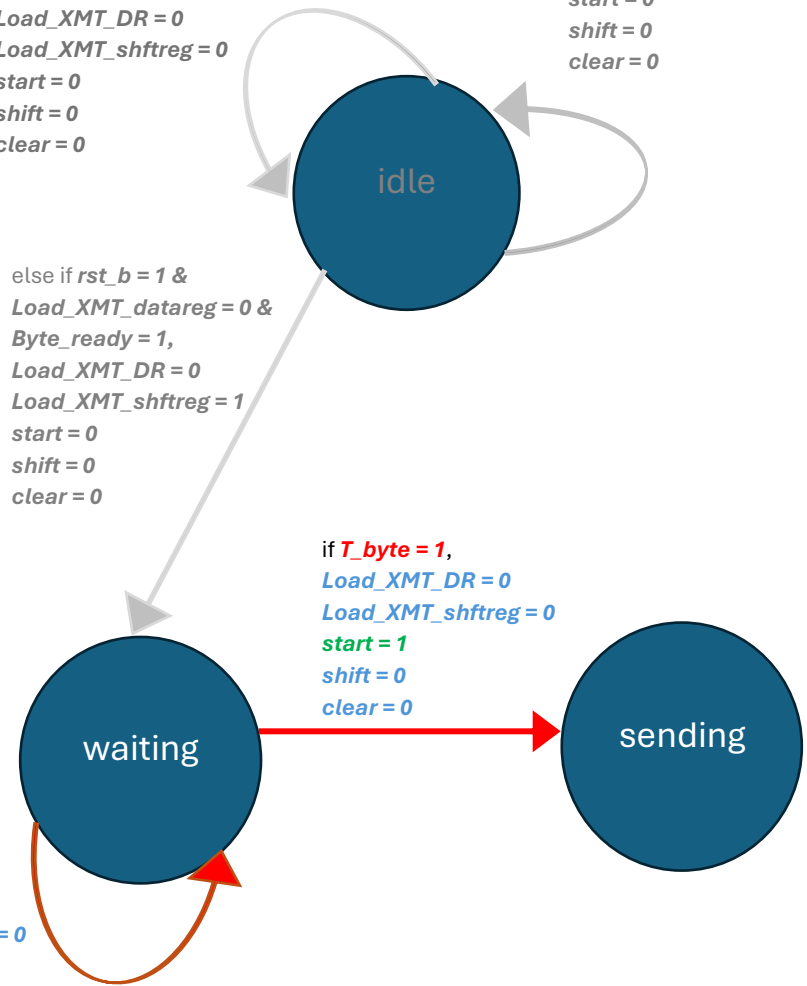if $T_byte = 0$,
 $Load_XMT_DR = 0$
 $Load_XMT_shftreg = 0$
 $start = 0$
 $shift = 0$
 $clear = 0$



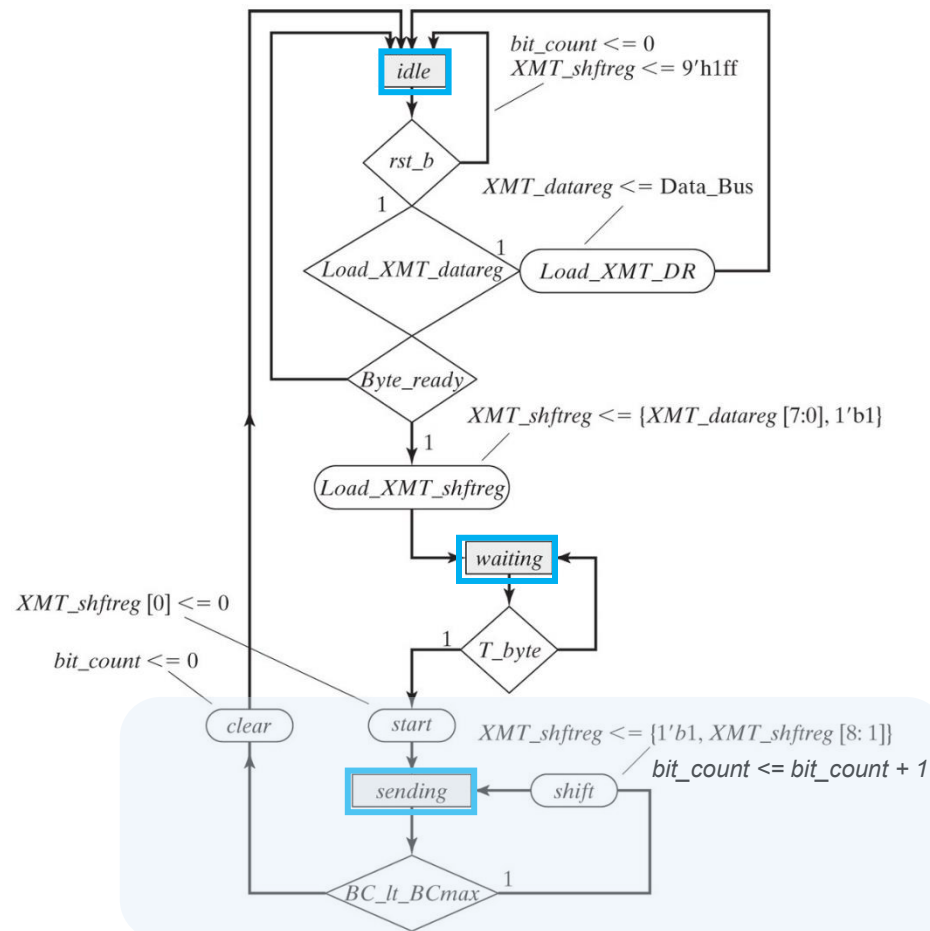
Explaining the ASMD (Algorithmic State Machine and DataPath) for the UART transmitter: [Generating the FSM](#)




Note: Only the branch corresponding to a true decision is annotated at a decision diamond; signals that are de-asserted are not shown explicitly de-asserted. Conditional assertions are indicated by the name of the asserted signal.

Note: BC_lt_BCmax asserts if $Bit_count < word_size + 1$.

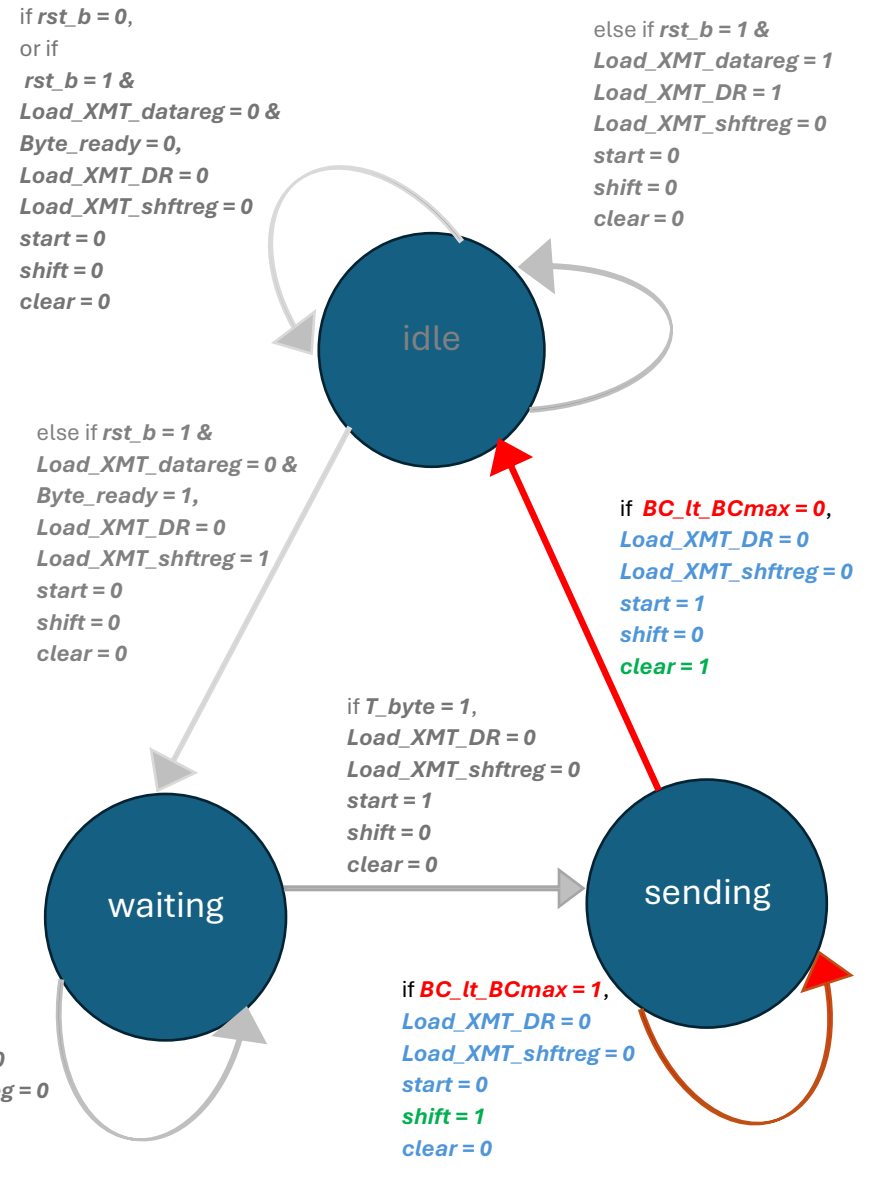Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall



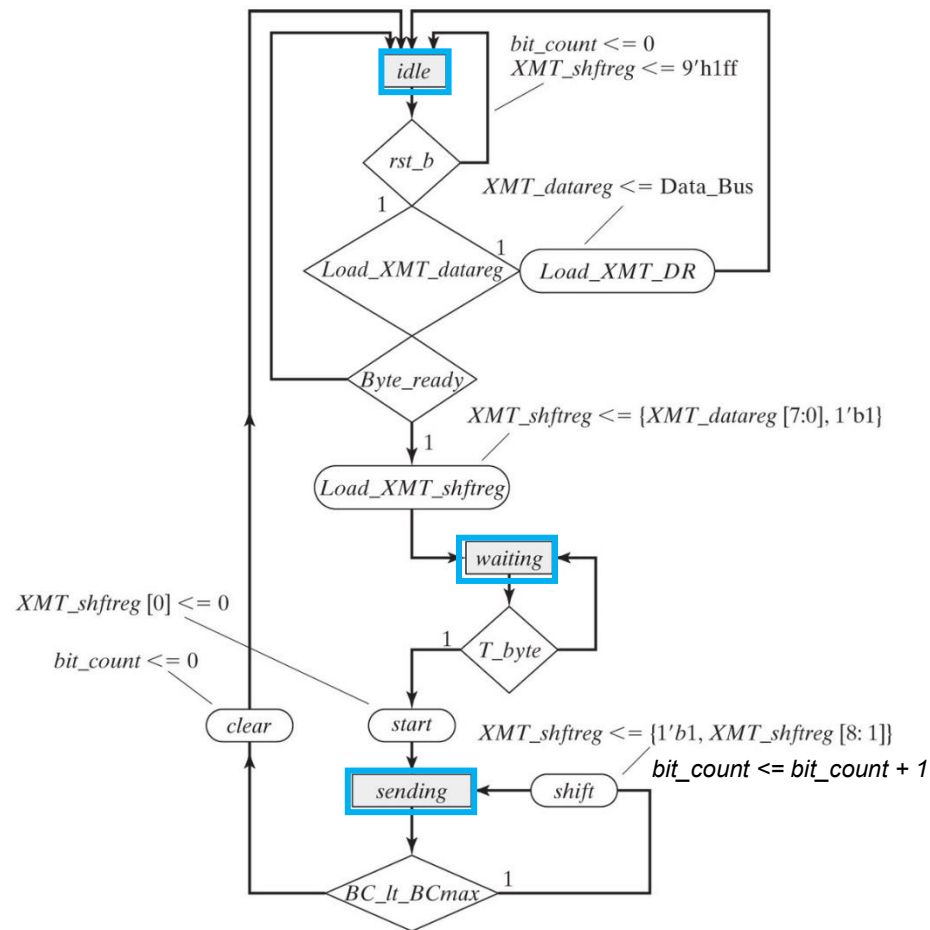Explaining the ASMD (Algorithmic State Machine and DataPath) for the UART transmitter: [Controller Verilog code](#)



Note: Only the branch corresponding to a true decision is annotated at a decision diamond; signals that are de-asserted are not shown explicitly de-asserted. Conditional assertions are indicated by the name of the asserted signal.

Note: BC_lt_BCmax asserts if $Bit_count < word_size + 1$.

```

always @ (posedge clock, negedge rst_b)
begin: State_transition
    if (rst_b == 1'b0)
        state <= idle;
    else
        state <= next_state;
    end

always @ (state, Load_Tx_datareg, Byte_ready, T_byte, BC_lt_BCmax)
begin: Output_and_next_state
    Load_XMT_DR = 0;
    start = 0;
    clear = 0;
    Load_XMT_shftreg = 0;
    shift = 0;
    next_state = idle;


    case (state)
        idle: if (Load_Tx_datareg == 1'b1) begin
                    Load_XMT_DR = 1;
                    next_state = idle;
                end
            else if (Byte_ready == 1'b1) begin
                    Load_XMT_shftreg = 1;
                    next_state = waiting;
                end

        waiting: if (T_byte == 1'b1) begin
                    start = 1;
                    next_state = sending;
                end
            else
                next_state = waiting;

        sending: if (BC_lt_BCmax) begin
                    shift = 1;
                    next_state = sending;
                end
            else begin
                    clear = 1;
                    next_state = idle;
                end

        default: next_state = idle;
    endcase
end
    
```

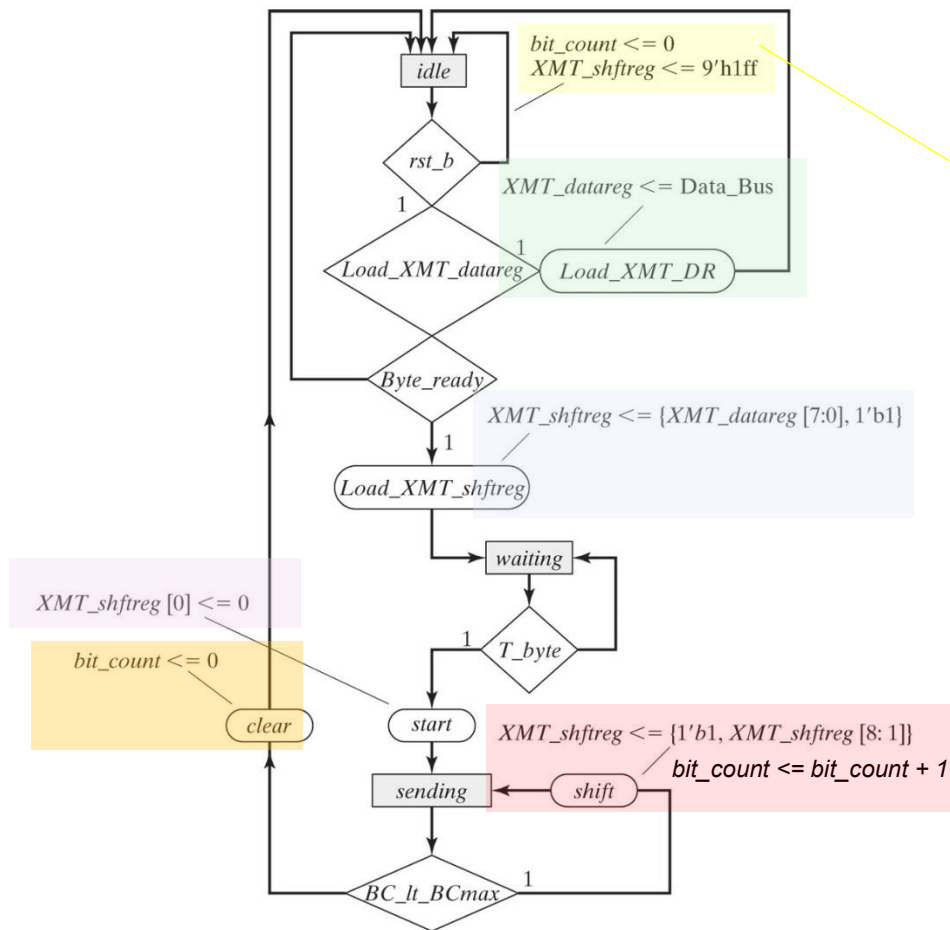Explaining the ASMD (Algorithmic State Machine and DataPath) for the UART transmitter: **DataPath Verilog code**



Note: Only the branch corresponding to a true decision is annotated at a decision diamond; signals that are de-asserted are not shown explicitly de-asserted. Conditional assertions are indicated by the name of the asserted signal.

Note: BC_lt_BCmax asserts if $Bit_count < word_size + 1$.

```

assign Serial_out = XMT_shftreg[0];
assign BC_lt_BCmax = (bit_count < word_size+1);

```

always @ (posedge clock, negedge rst_b)

```

if (rst_b == 0) begin
    XMT_shftreg <= 9'h1FF;
    bit_count <= 0;
end

```

else begin: Register Transfers

```

if (Load_XMT_DR == 1'b1)
    XMT_datareg <= Data_Bus; // get the data word from data bus

```

```

if (Load_Tx_SR == 1'b1)
    XMT_shftreg <= {XMT_datareg, 1'b1}; // load shftreg & insert start bit

```

```

if (start == 1'b1)
    XMT_shftreg[0] <= 0; // signal start of transmission

```

```

if (clear == 1'b1)
    bit_count <= 0;

```

```

if (shift == 1'b1) begin // shift Shift_Register right and fill with 1's
    XMT_shftreg <= {1'b1, XMT_shftreg[word_size : 1]};
    bit_count <= bit_count + 1; end

```

end

